


LECTURE 5

- Integration Property
 - s domain interpretation of charged C/L
- Solution of Integro-Differential Equations using Laplace Transform

Reference: Decatlo/Lin pp 580-581, 585-590

Example: A second s-domain interpretation of a charged capacitor by way of integration property

Time-domain

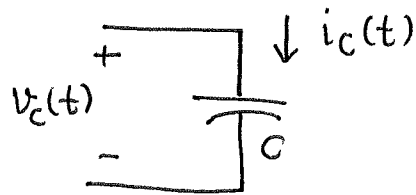

$$v_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(q) dq \quad t > 0$$


s-domain

Laplace transform the above equation

$$\begin{aligned} V_c(s) &= \frac{1}{C} \left[\frac{I_c(s)}{s} + \frac{\int_{-\infty}^{0^-} i_c(q) dq}{s} \right] \\ &= \frac{I_c(s)}{Cs} + \frac{\frac{1}{C} \int_{-\infty}^{0^-} i_c(q) dq}{s} \end{aligned}$$

$$V_c(s) = \frac{I_c(s)}{Cs} + \frac{v_c(0^-)}{s}$$


Circuit Interpretation
 voltages

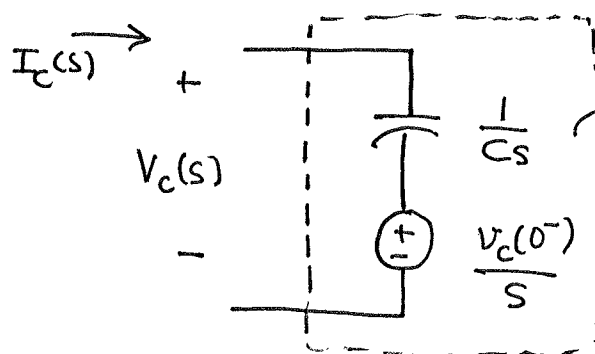

Equivalent circuit in s-domain

Example: A frequency domain interpretation of the inductor with $i_L(0^-) \neq 0$

Time-domain

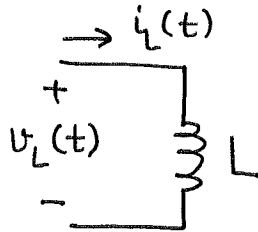


$$\Leftrightarrow i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(\tau) d\tau$$

s-domain


Laplace transform the above equation

$$\begin{aligned} I_L(s) &= \frac{1}{L} \left[\frac{V_L(s)}{s} + \frac{\int_{-\infty}^{0^-} v_L(\tau) d\tau}{s} \right] \\ &= \frac{V_L(s)}{Ls} + \frac{\frac{1}{L} \int_{-\infty}^{0^-} v_L(\tau) d\tau}{s} \end{aligned}$$
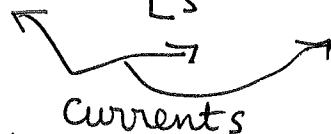
$$I_L(s) = \frac{V_L(s)}{Ls} + \frac{i_L(0^-)}{s}$$




circuit Interpretation

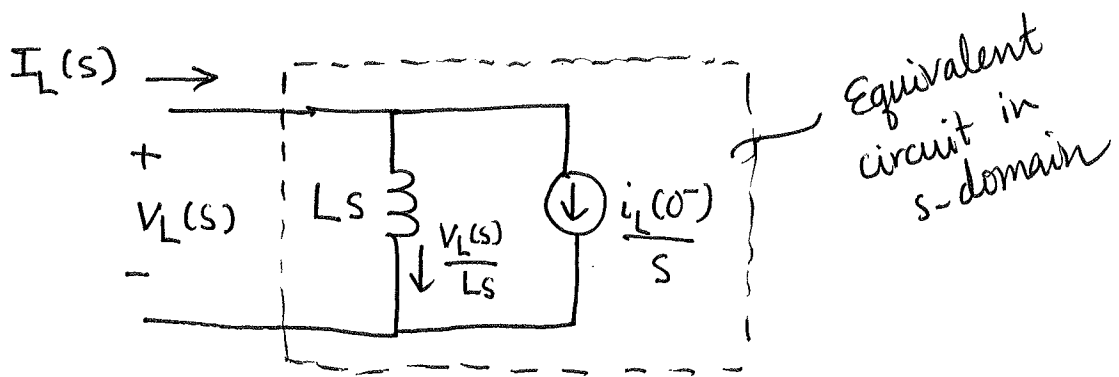

Solution of Integro-Differential Equations using Laplace Transform

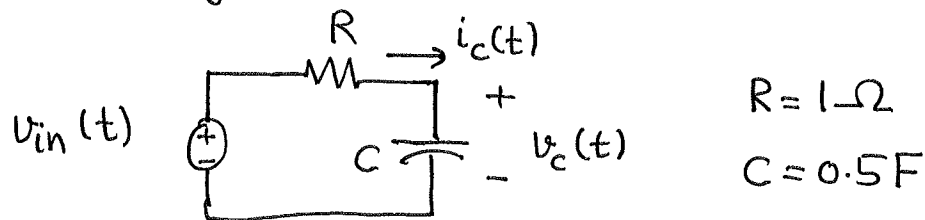Example: Find $v_c(t)$ for the series RC circuit
assuming $v_c(0^-) \neq 0$ and $v_{in}(t) = 10e^{-4t}u(t)$



Step 1: Construct differential equation in
terms of R and C , then plug in numbers.

$$(a) \quad i_c = C \frac{dv_c}{dt}$$

$$(b) \quad i_c = \frac{1}{R} [v_{in} - v_c]$$

$$(c) \quad \therefore C \frac{dv_c}{dt} = \frac{1}{R} v_{in} - \frac{1}{R} v_c$$

$$\frac{dv_c}{dt} = \frac{1}{RC} v_{in} - \frac{1}{RC} v_c$$

$$\frac{dv_c}{dt} + \frac{1}{RC} v_c = \frac{1}{RC} v_{in}$$

Plugging in R and C values, we get

$$\frac{dv_c}{dt} + 2 v_c = 2 v_{in}$$

Step 2: Take Laplace Transform on both sides of the differential equation

$$s V_C(s) - v_C(0^-) + \frac{1}{RC} V_C(s) = \frac{1}{RC} V_{in}(s)$$

$$(s+2) V_C(s) = 2 V_{in}(s) + v_C(0^-)$$

$$V_C(s) = \frac{2}{s+2} V_{in}(s) + \frac{v_C(0^-)}{s+2}$$

$$V_C(s) = \frac{2}{s+2} \cdot \frac{10}{s+4} + \frac{v_C(0^-)}{s+2}$$


$$V_C(s) = \frac{20}{(s+2)(s+4)} + \frac{v_C(0^-)}{s+2}$$

$$V_C(s) = \frac{10}{s+2} - \frac{10}{s+4} + \frac{v_C(0^-)}{s+2}$$

Step 3 : Find $v_C(t)$ by taking inverse Laplace transform

$$v_C(t) = \underbrace{10 e^{-2t} u(t) - 10 e^{-4t} u(t)}_{\text{due only to input "zero-state response"}} + \underbrace{v_C(0^-) e^{-2t} u(t)}_{\text{due only to IC "zero-input response"}}$$

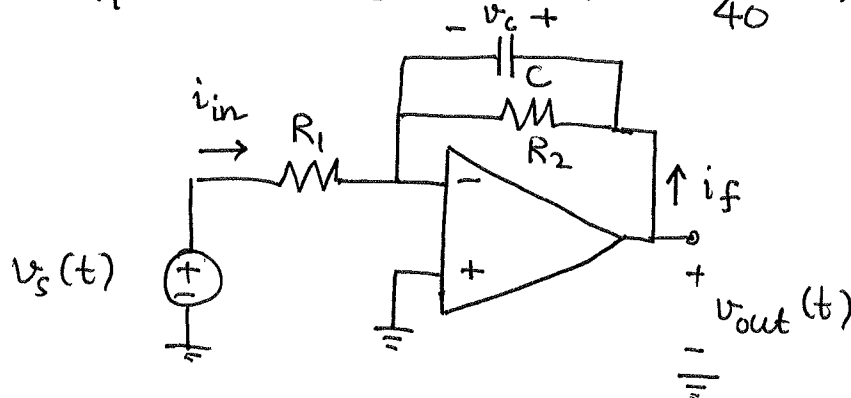Example: Find $v_{out}(t)$ for the op-amp circuit below when $v_s(t) = e^{-4t} \cos(2t) u(t) V$, $R_1 = 5 \Omega$, $R_2 = 10 \Omega$, $C = \frac{1}{40} F$, $v_c(0^-) \neq 0$



Step 1: Construct a differential equation

$$(a) \quad i_{in} = -i_f$$

$$(b) \quad i_{in} = \frac{v_s}{R_1}$$

$$(c) \quad i_f = C \frac{dv_c}{dt} + \frac{v_c}{R_2}$$

$$(d) \quad v_c = v_{out}$$

$$(e) \quad \therefore -C \frac{dv_c}{dt} - \frac{v_c}{R_2} = \frac{v_s}{R_1}$$

$$\frac{dv_c}{dt} + \frac{v_c}{R_2 C} = -\frac{v_s}{R_1 C}$$

Step 2: Take Laplace transform on both sides of the differential equation

$$s V_c(s) - v_c(0^-) + \frac{1}{R_2 C} V_c(s) = -\frac{1}{R_1 C} V_s(s)$$

$$\left(s + \frac{1}{R_2 C}\right) V_C(s) = -\frac{1}{R_1 C} V_S(s) + v_C(0^-)$$

$$V_C(s) = \frac{-\frac{1}{R_1 C}}{s + \frac{1}{R_2 C}} V_S(s) + \frac{v_C(0^-)}{s + \frac{1}{R_2 C}}$$

$$V_C(s) = -\frac{8}{\cancel{s+4}} \cdot \frac{\cancel{s+4}}{(s+4)^2 + 4} + \frac{v_C(0^-)}{s+4}$$

$$V_C(s) = \frac{-8}{(s+4)^2 + 4} + \frac{v_C(0^-)}{s+4}$$

Step 3: Find $v_{out}(t) = v_C(t)$ by taking inverse Laplace transform

$$v_{out}(t) = \underbrace{-4 e^{-4t} \sin(2t) u(t)}_{\substack{\text{due only to input} \\ \text{"zero-state response"}}} + \underbrace{v_C(0^-) e^{-4t} u(t)}_{\substack{\text{due only to IC} \\ \text{"zero-input response"}}$$