

Aung Kyi San  
Summer 2012

ECE 20200 : Linear Circuit Analysis II  
School of ECE, Purdue University

## LECTURE 11

- Switched Capacitors Circuits

- Reference: Decarlo/Lin

pp 645-652

Switched Capacitor Networks



- Resistorless, inductorless
- only sources, switches, capacitors and op-amps

Example 1: Consider the circuit as shown below.

The switch 'S' is closed at  $t=0$ .  $v_{c_1}(0^-) = 1V$   
 $v_{c_2}(0^-) = 0$ . Compute  $v_{c_1}(t)$  and  $v_{c_2}(t)$  for  $t > 0$ .

Method 1

For  $t > 0$ ,

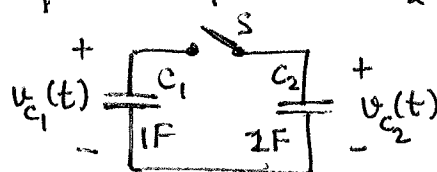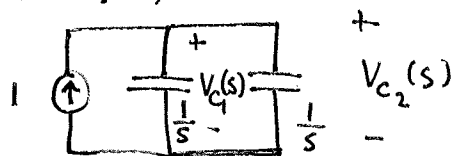

$$V_{C_1}(s) = V_{C_2}(s) = \frac{\frac{1}{s} \cdot \frac{1}{s}}{\frac{1}{s} + \frac{1}{s}} \cdot 1 = \frac{\frac{1}{s^2}}{\frac{2}{s}} = \frac{0.5}{s}$$

$$v_{c_1}(t) = v_{c_2}(t) = 0.5 u(t)$$

Method 2 - Conservation-of-charge approach

For  $t < 0$ ,  $q_{\text{total}} = C_1 v_{c_1}(0^-) + C_2 v_{c_2}(0^-)$   
 $= (1)(1) + (1)(0) = 1$



For  $t > 0$ ,  $q_{\text{total}} = C_1 v_{c_1}(0^+) + C_2 v_{c_2}(0^+)$   
 $= (1 + 1) v_{c_1}(0^+) \quad (\because v_{c_1}(0^+) = v_{c_2}(0^+))$





By conservation-of-charge

$$1 = 2 v_{c_1}(0^+) \Rightarrow v_{c_1}(0^+) = \frac{1}{2} = v_{c_2}(0^+)$$

For  $t > 0$ ,  $v_{c_1}(t) = v_{c_2}(t) = 0.5 V$  (or)  $v_{c_1}(t) = v_{c_2}(t) = 0.5 u(t)$

Example 2:

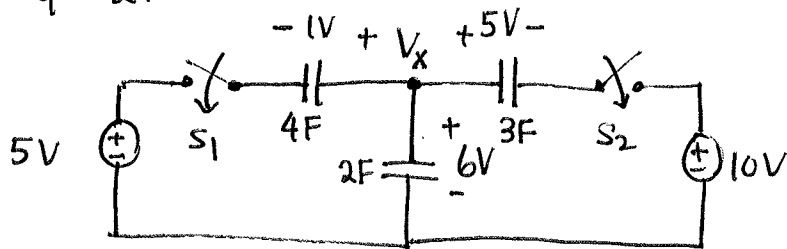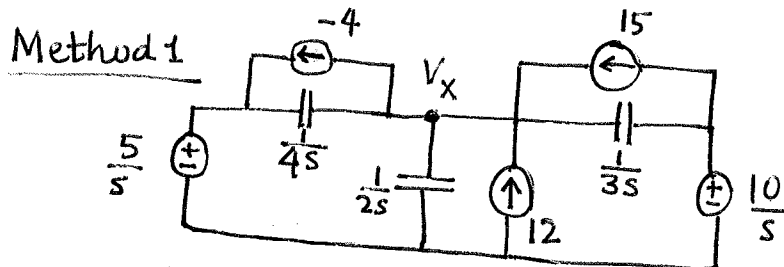Initial conditions shown in figure at  $t=0^-$ .Switches - closed at  $t=0$ Find the node voltage  $V_x$  for  $t > 0$ Nodal Eqn. at node  $V_x$ 

$$\left(V_x - \frac{5}{s}\right)4s + (-4) + V_x(2s) - 12 - 15 + \left(V_x - \frac{10}{s}\right)3s = 0$$

$$V_x = \frac{9}{s}$$

$$v_x(t) = 9 u(t) \text{ V}$$

Method 2 - conservation-of-charge approach

For  $t < 0$ ,  $q_{\text{total}} = (4)(1) + (3)(5) + (2)(6) = 31$

For  $t > 0$ ,  $q_{\text{total}} = (4)(V_x - 5) + 2V_x + 3(V_x - 10)$   
 $= 9V_x - 50$

 $\therefore$  By conservation-of-charge

$$31 = 9V_x - 50$$


$$V_x = \frac{81}{9} = 9 \text{ V}$$

$$\therefore v_x(t) = 9 \text{ V for } t > 0 \text{ (or) } v_x(t) = 9 u(t) \text{ V.}$$




Example 3. Given  $v_2(t) = 10V$ ,  $v_3(t) = v_4(t) = 0V$  for  $t < 0$ .

Find  $v_2(t)$ ,  $v_3(t)$  and  $v_4(t)$  for  $t > 0$

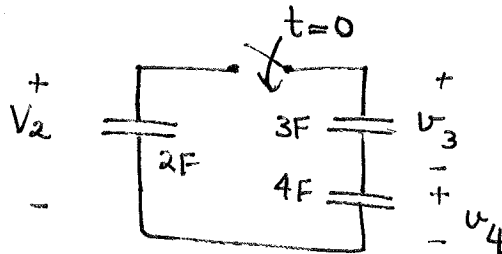

Method 1.

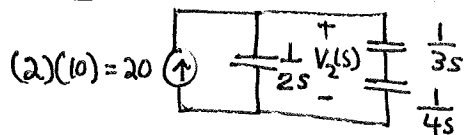

$$V_2(s) = \frac{7}{26s} \cdot 20 = \frac{70}{13s}$$

$$v_2(t) = \frac{70}{13} u(t) \leftarrow$$

$$V_3(s) = V_2(s) \cdot \frac{1}{\frac{3s}{7}} = \frac{70}{13s} \cdot \frac{4}{7} = \frac{40}{13s}$$

$$v_3(t) = \frac{40}{13} u(t) \leftarrow$$

$$V_4(s) = V_2(s) \cdot \frac{1}{\frac{4s}{7}} = \frac{70}{13s} \cdot \frac{3}{7} = \frac{30}{13s}$$

$$v_4(t) = \frac{30}{13} u(t) \leftarrow$$

$$\frac{1}{\frac{1}{3s} + \frac{1}{4s}} = \frac{1}{\frac{1}{3s} + \frac{1}{4s}} = \frac{7}{12s}$$

$$\frac{1}{2s} \cdot \frac{7}{12s} = \frac{1}{\frac{12s}{7} + 2s} = \frac{7}{26s}$$


Method 2

$$t < 0 \quad q_{\text{total}} = 2(10) = 20$$

$$t > 0 \quad q_{\text{total}} = 2v_2 + 3v_3$$

$$\therefore 20 = 2v_2 + 3v_3$$

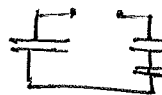But  $3 \frac{1}{3} v_3 = 4v_4$  and  $v_2 = v_3 + v_4$   
 $4 \frac{1}{4} v_4 = \frac{4}{3} v_3$



$$\begin{aligned}
 \therefore 20 &= 2v_2 + 3v_3 \\
 &= 2(v_3 + v_4) + 3v_3 \\
 &= 5v_3 + 2v_4 \\
 &= 5 \frac{4}{3} v_4 + 2v_4
 \end{aligned}$$


$$20 = \frac{26}{3} v_4$$

$$v_4 = \frac{60}{26} = \frac{30}{13} \text{ V} \leftarrow$$

$$v_3 = \frac{4}{3} v_4 = \frac{4}{3} \cdot \frac{30}{13} = \frac{40}{13} \text{ V} \leftarrow$$

$$v_2 = v_3 + v_4 = \frac{70}{13} \text{ V} \leftarrow$$


Example 4.

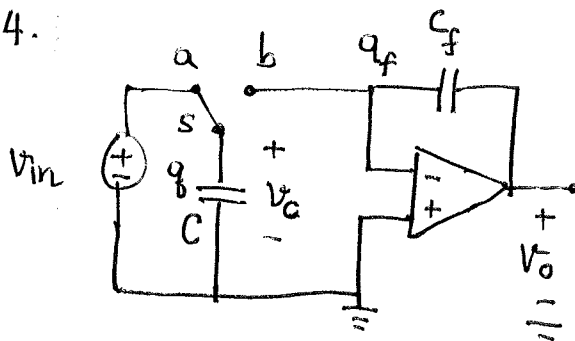

S is operated in the following manner.

1. At  $t=0$ , S is at position a, has been there for a long time.
2. At  $t=T$ , S is moved to position b.
3. At  $t=2T$ , S is moved to position a.
4. At  $t=3T$ , S is moved to position b.
5. :


Determine  $v_o$  and sketch the output waveform.

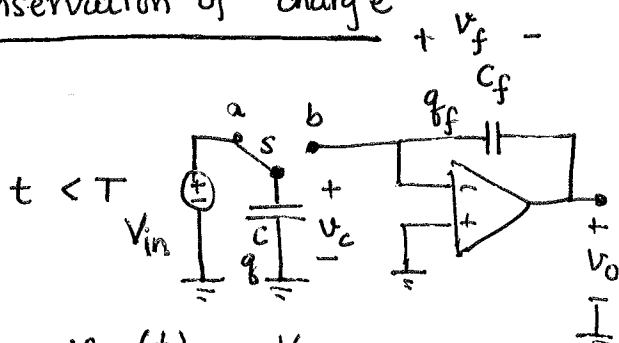Conservation of charge

$$v_c(t) = V_{in}$$

$$v_f(t) = 0 \Rightarrow v_o = -v_f = 0 \leftarrow$$

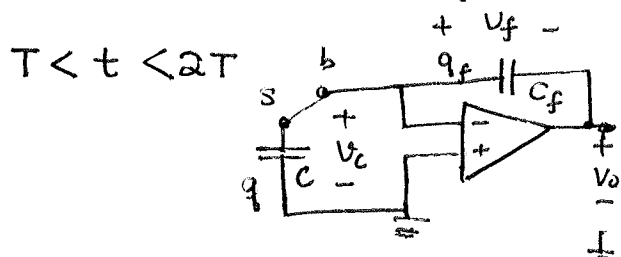
$$q = C V_{in}, \quad q_f = 0 \quad \therefore q_{total} = C V_{in}$$



$$v_c = v_- = v_+ = 0$$

$$q = 0, \quad q_f = q_{total} = C V_{in}$$
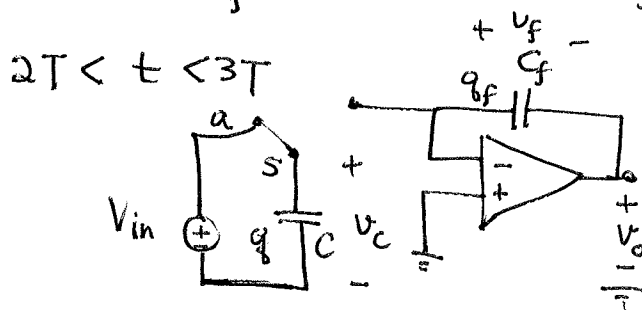
$$v_f = \frac{C}{C_f} V_{in} \Rightarrow v_o = -\frac{C}{C_f} V_{in} \leftarrow$$



$$v_c(t) = V_{in}$$

$$q = C V_{in}, \quad q_f = C V_{in} \quad \therefore q_{total} = 2C V_{in}$$

$$v_o = -\frac{C}{C_f} V_{in} \leftarrow$$

$$3T < t < 4T$$

$$v_c = v_- = v_+ = 0$$

$$q = 0, \quad q_f = q_{\text{total}} = 2Cv_{\text{in}}$$

$$v_f = \frac{2Cv_{\text{in}}}{C_f} \Rightarrow v_o = -\frac{2Cv_{\text{in}}}{C_f} \quad \leftarrow$$

$$4T < t < 5T$$

$$v_c(t) = v_{\text{in}}, \quad v_f(t) = \frac{2Cv_{\text{in}}}{C_f}$$

$$q = Cv_{\text{in}}, \quad q_f = 2Cv_{\text{in}}$$

$$q_{\text{total}} = 3Cv_{\text{in}}$$

$$v_o = -\frac{2Cv_{\text{in}}}{C_f} \quad \leftarrow$$

$$5T < t < 6T$$

$$v_c = v_- = v_+ = 0$$

$$q = 0, \quad q_f = q_{\text{total}} = 3Cv_{\text{in}}$$

$$v_f = \frac{3Cv_{\text{in}}}{C_f} \Rightarrow v_o = -\frac{3Cv_{\text{in}}}{C_f} \quad \leftarrow$$

⋮

$$v_o(t) = \begin{cases} 0 & t < T \\ -Cv_{\text{in}}/C_f & T < t < 3T \\ -2Cv_{\text{in}}/C_f & 3T < t < 5T \\ -3Cv_{\text{in}}/C_f & 5T < t < 7T \end{cases}$$

Let all the parameters have units of 1.

