

Key Ideas in Chapter 19: Electric Circuits



- **Surface charges make the electric field that drives the current in a circuit.**
 - Transient effects precede the steady state.
 - A battery maintains a charge separation and a potential difference.
- **How to analyze circuits:**
 - Current-node rule: Current into a node equals current out of the node.
 - Voltage-loop rule: The total potential difference around a loop is zero.

Last Time


- Electron Spin
- Bar Magnet
- Equilibrium vs. Steady State in a Circuit
- What is "used up" in a circuit?
- Kirchhoff's Current Node Law
- **E**-field inside a wire

Microscopic View of E in the wire:

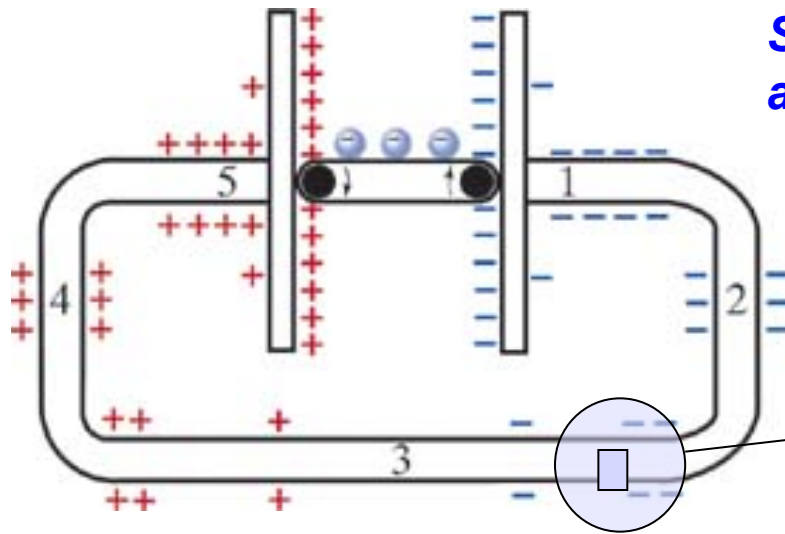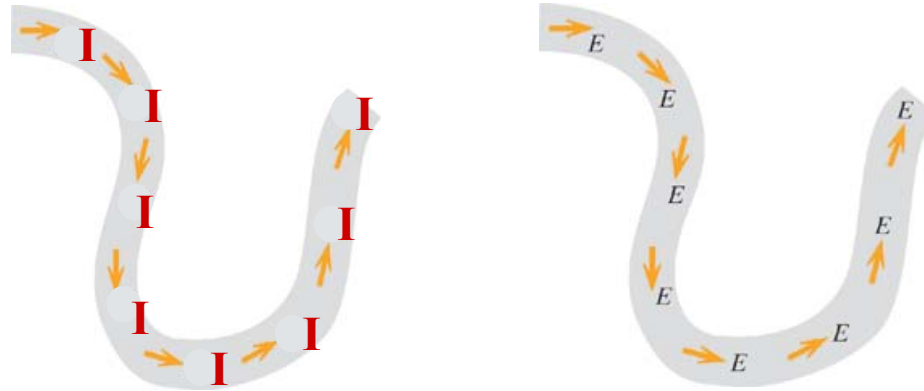Constant current in the wire \rightarrow Constant E in the wire.



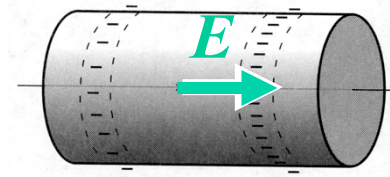Surface charges on wire automatically adjust so as to maintain constant E in the wire.




Today

- Transient response when connecting a circuit
- How long until steady state is reached?
- Introduction to Resistors
- Energy conservation in a circuit
- Kirchhoff's Voltage Loop Law
- Batteries

Connecting a Circuit

What happens just before and just after a circuit is connected?

Before the circuit is connected:

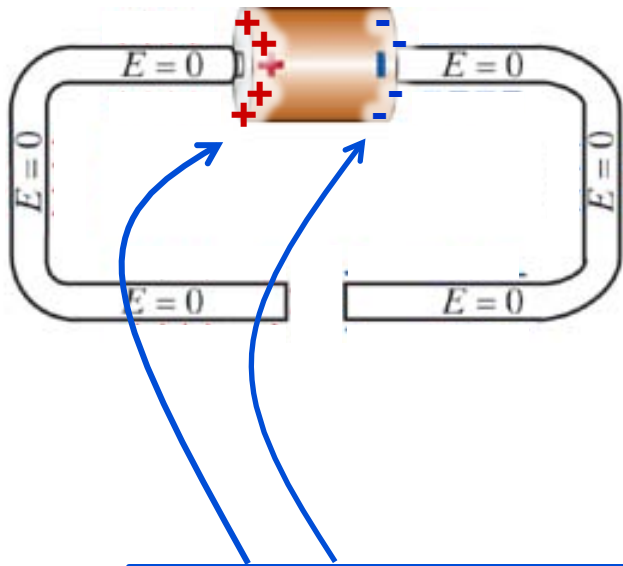

- No current flows $I = |q|nAu|\vec{E}| = 0$
- System is in **equilibrium**:

$$\vec{E} = 0$$

$$\vec{v} = u|\vec{E}| = 0$$


How is $|\vec{E}| = 0$ maintained when there are charges here?

There must be surface charges on the wire to prevent current from flowing before we connect the circuit.

Connecting a Circuit

What happens just before and just after a circuit is connected?


Before the circuit is connected:

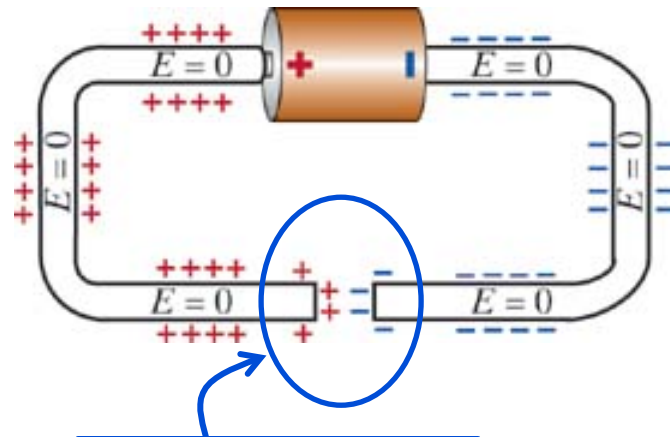

- No current flows $I = |q|nAu|\vec{E}| = 0$
- System is in **equilibrium**:

$$\vec{E} = 0$$

$$\bar{v} = u|\vec{E}| = 0$$

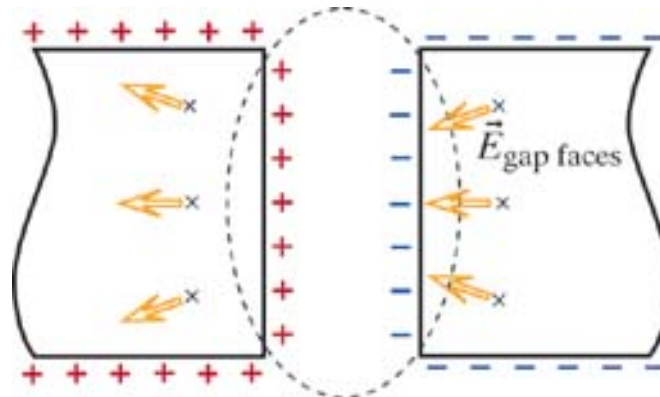


E due only to gap faces

Connecting a Circuit

What happens just before and just after a circuit is connected?


Before the circuit is connected:

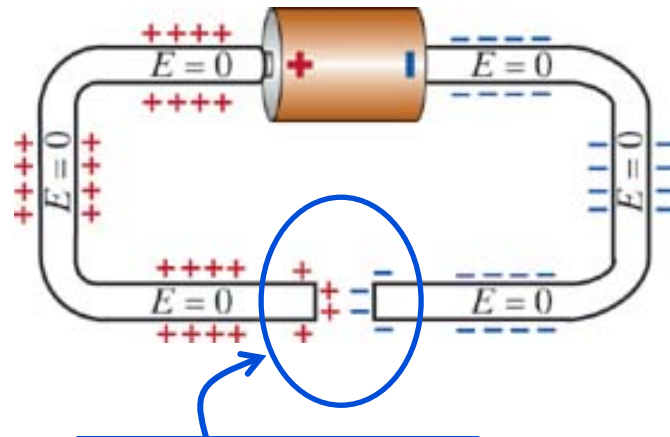

- No current flows $I = |q|nAu|\vec{E}| = 0$
- System is in **equilibrium**:

$$\vec{E} = 0$$

$$\bar{v} = u|\vec{E}| = 0$$

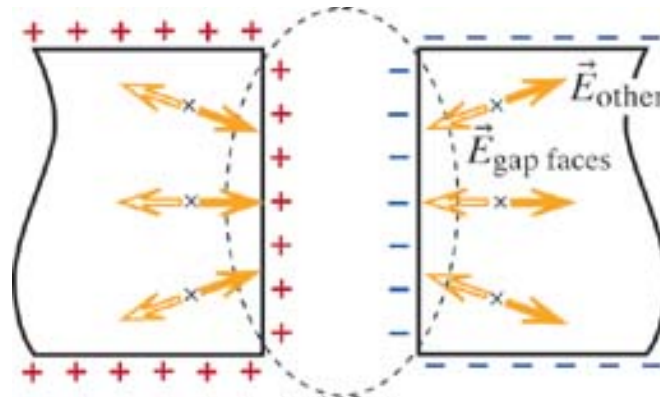


E due to everything else cancels \vec{E}_{gap}

Connecting a Circuit



What happens just before and just after a circuit is connected?

Before the circuit is connected:

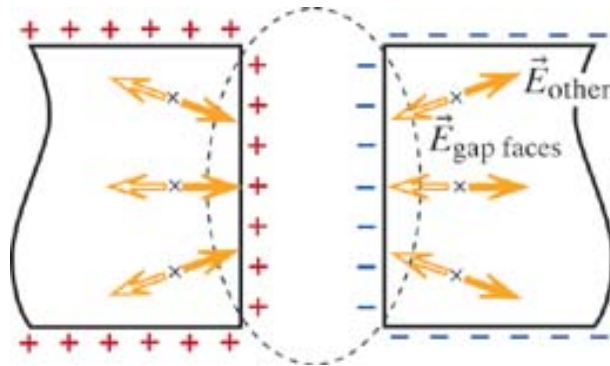

E due to everything else cancels \vec{E}_{gap}

Now close the gap ...

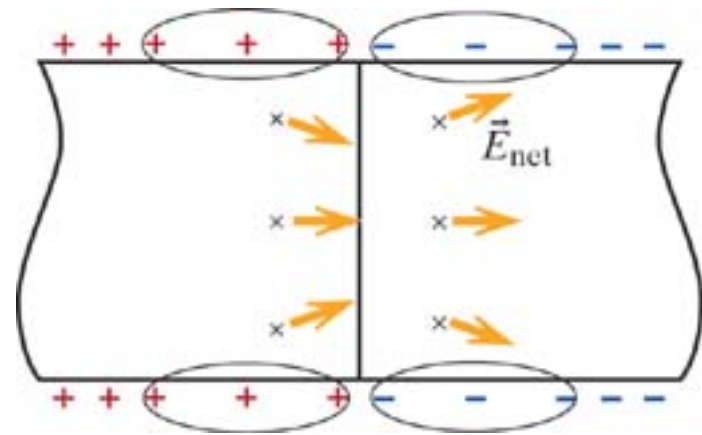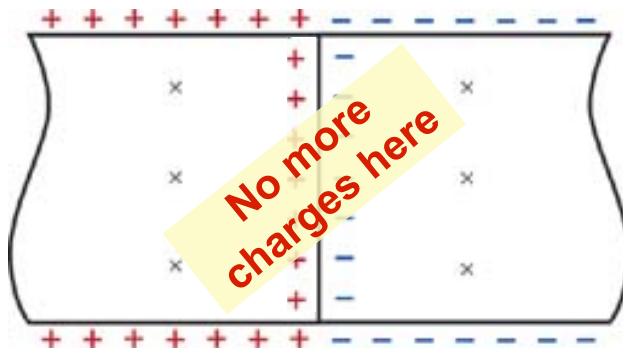


The gap face charge $\rightarrow 0$, and so does \vec{E}_{gap}

Connecting a Circuit

What happens just before and just after a circuit is connected?

Just after the circuit is connected:

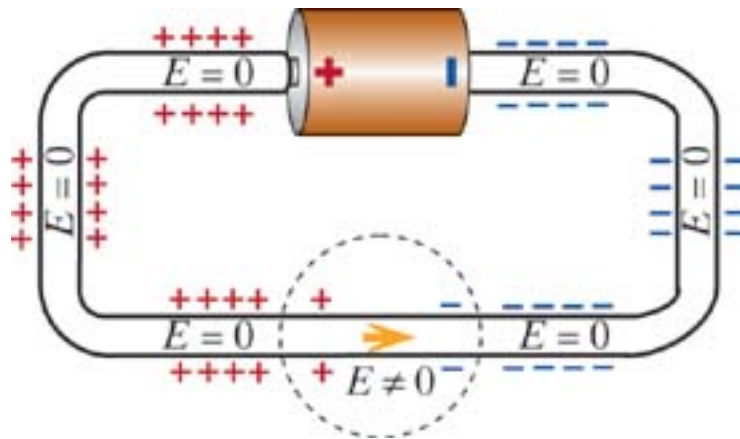

There is a **disturbance** in the previous (equilibrium) E-field.

Now the region next to the disturbance updates its E-field, and the next region...

How fast does this disturbance propagate?

At the drift speed of the electrons? $\bar{v} \approx 5 \times 10^{-5} m/s$

At the speed of light? $c \approx 3 \times 10^8 m/s$

iClicker – Reality Physics!

$\bar{v} \approx 5 \times 10^{-5} m/s$ Drift speed of electrons

$c \approx 3 \times 10^8 m/s$ Speed of light

iClicker – Reality Physics!

$\bar{v} \approx 5 \times 10^{-5} m/s$ Drift speed of electrons

$c \approx 3 \times 10^8 m/s$ Speed of light

Reality Physics!

$\bar{v} \approx 5 \times 10^{-5} m/s$ Drift speed of electrons

$c \approx 3 \times 10^8 m/s$ Speed of light



Flip Light Switch On.

How long until information about the change in E-field reaches the light bulb?



← L = 5 m →

≈ 1 day for electrons to travel from light switch to bulb.


≈ 16 nanoseconds for the change in E-field to travel from light switch to bulb.

Because there are sooooo many electrons in the wire, they don't have to move far to create a large current.

Connecting a Circuit


What happens just before and just after a circuit is connected?

Just after the circuit is connected:

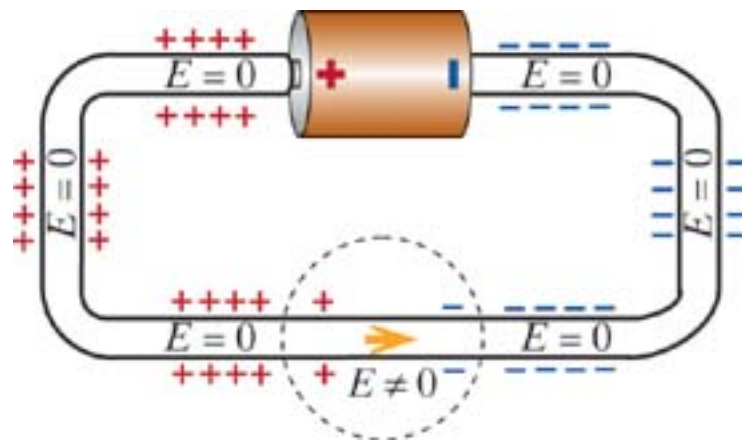


There is a **disturbance** in the previous (equilibrium) E-field.

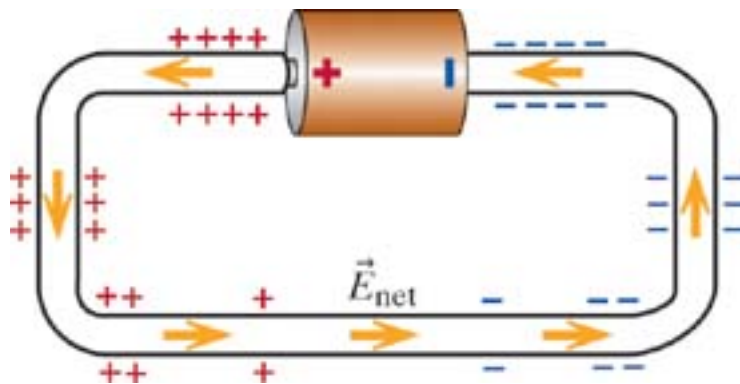Now the region next to the disturbance updates its E-field, and the next region...



The disturbance travels at the speed of light, and within a few **nanoseconds**, **steady state** is established.

Surface Charge and Resistors

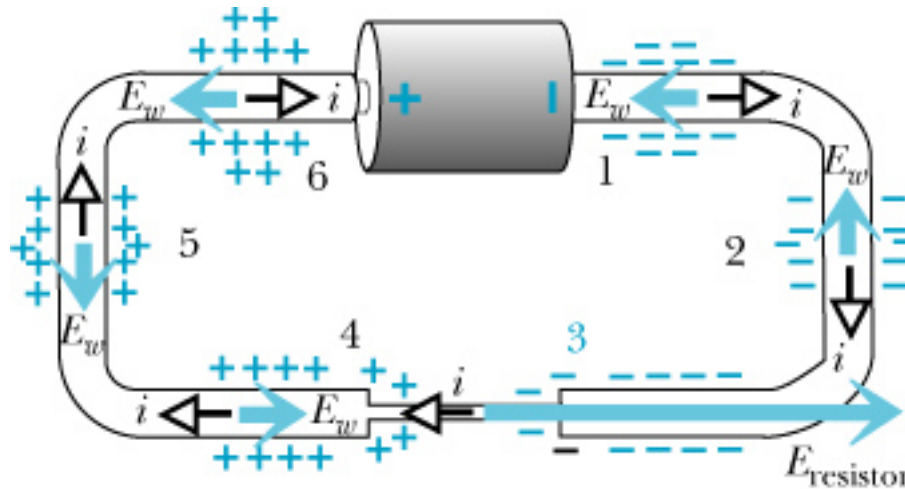

After steady state is reached:


$$i_{thin} = i_{thick} \longrightarrow$$

$$i_{thin} = nA_{thin}uE_{thin}$$


$$i_{thick} = nA_{thick}uE_{thick}$$

$$E_{thin} = \frac{A_{thick}}{A_{thin}} E_{thick}$$

A Wide Resistor

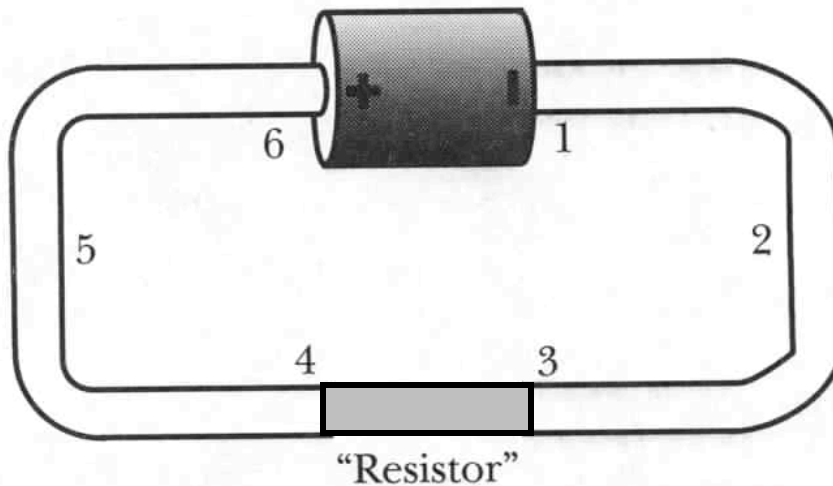

low mobility

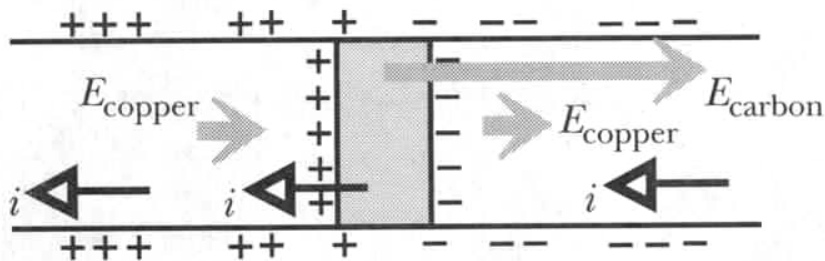


$$i = nA\bar{v} = nAuE$$

$$i_{\text{thin}} = nAu_{\text{thin}}E_{\text{thin}}$$

$$i_{\text{thick}} = nAu_{\text{thick}}E_{\text{thick}}$$

$$E_{\text{thin}} = \frac{u_{\text{thick}}}{u_{\text{thin}}} E_{\text{thick}}$$

Energy in a Circuit

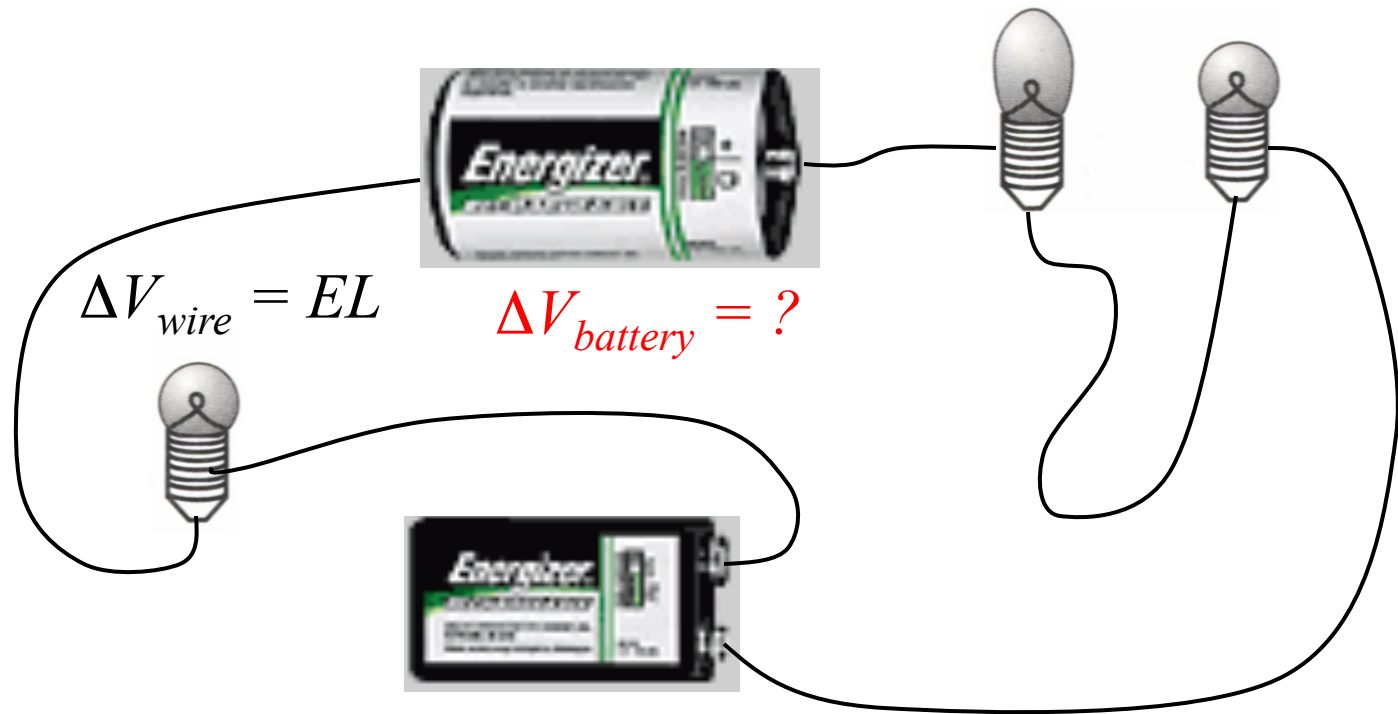


Energy conservation (the Kirchhoff loop rule [2nd law]):


$$\Delta V_1 + \Delta V_2 + \Delta V_3 + \dots = 0 \quad \text{along any closed path in a circuit}$$

$$\Delta V = \Delta U/q \quad \leftarrow \text{energy per unit charge}$$

General Use of the Loop Rule

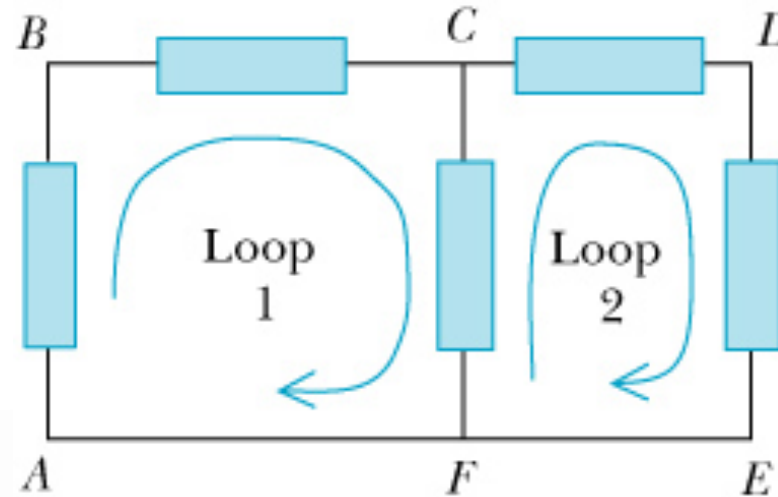

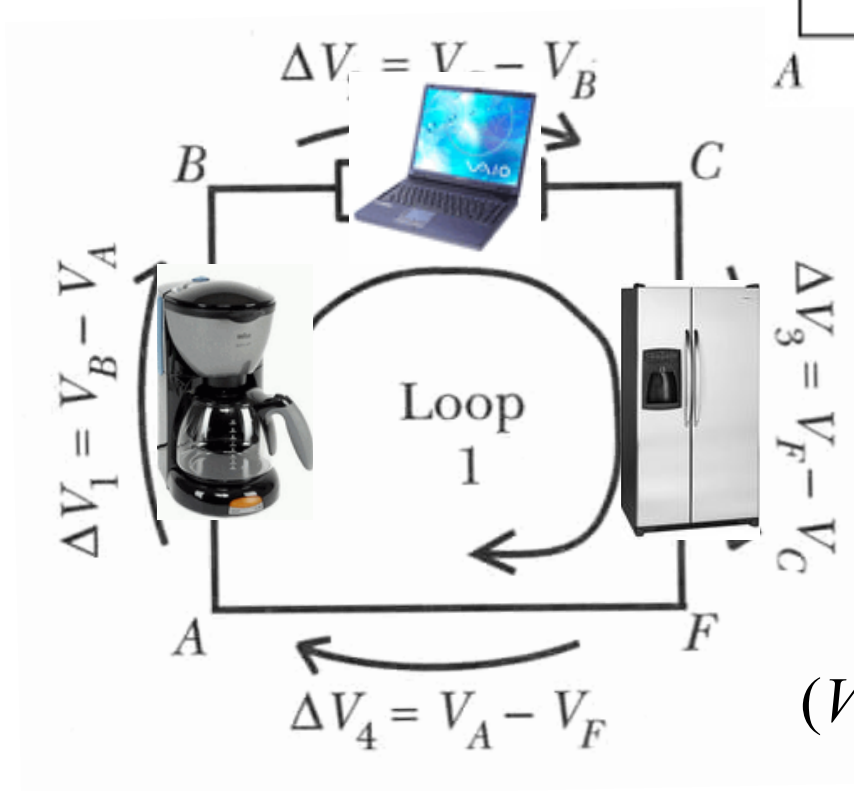
$$\Delta V_1 + \Delta V_2 + \Delta V_3 + \Delta V_4 = 0$$




$$(V_B - V_A) + (V_C - V_B) + (V_F - V_C) + (V_A - V_F) = 0$$

Two Batteries in Series

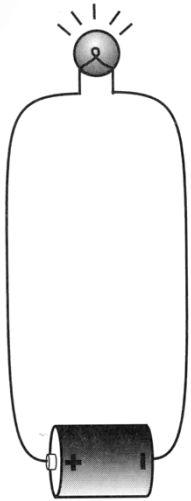

Why light bulb is brighter with two batteries?

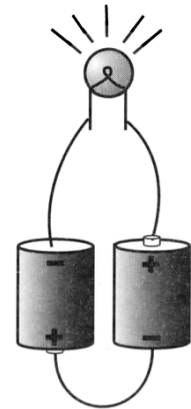Two batteries in series can drive more current:
Potential difference across two batteries in series is $2emf \rightarrow$ doubles electric field everywhere in the circuit \rightarrow doubles drift speed \rightarrow doubles current.



$$emf - EL = 0$$

$$E = \frac{emf}{L}$$

$$i = nAuE = nAu \frac{emf}{L}$$

$$P_{1batt} = eLnAu \left(\frac{emf}{L} \right)^2$$

Work per second:

$$P = (q / T)EL = ieEL$$

$$P = nAueLE^2$$

$$2emf - EL = 0$$

$$E = \frac{2emf}{L}$$

$$i = nAu \frac{2emf}{L}$$

$$P_{2batt} = eLnAu \left(\frac{2emf}{L} \right)^2$$

$$P_{2batt} = 4 \times P_{1batt}$$

Potential Difference Across the Battery

Coulomb force on each e

non-Coulomb force on each e

1. $a = F_{NC}/m$
2. $F_C = eE_C \longrightarrow E_C = \frac{F_C}{e}$
3. $F_C = F_{NC}$

$$|\Delta V_{batt}| = E_C s = \frac{F_C s}{e} = \frac{F_{NC} s}{e}$$

Energy input per unit charge
emf – electromotive force


The function of a battery is to produce and maintain a charge separation.

The *emf* is measured in Volts, but it is not a potential difference!

The *emf* is the energy input per unit charge.

chemical, nuclear, gravitational...

Twice the Length

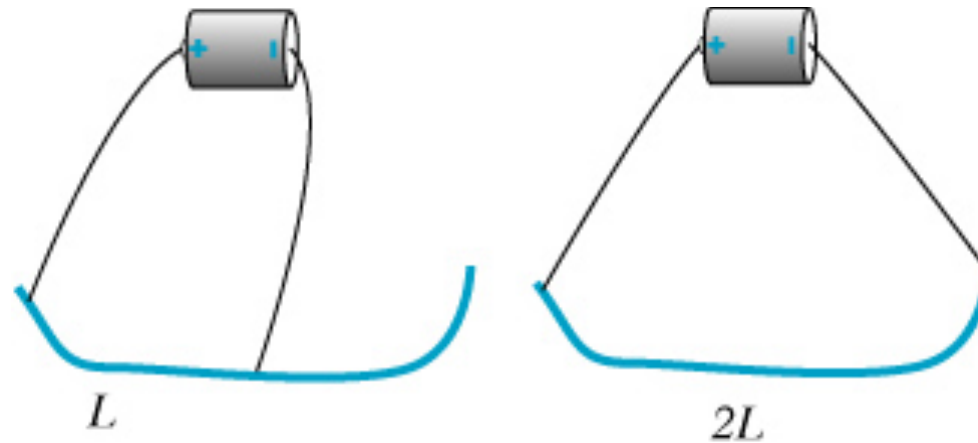


Nichrome wire (resistive)

Quantitative measurement of current with a compass


$$i = nAuE = nAu \frac{\Delta V}{L} \longrightarrow i_{2L} = nAu \frac{\Delta V}{2L} = \frac{1}{2} i_L$$

Current is halved when increasing the length of the wire by a factor of 2.

Doubling the Cross-Sectional Area

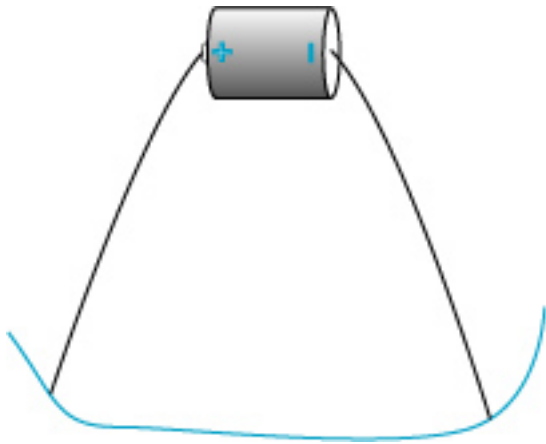

$$i_A = nAu|E|$$

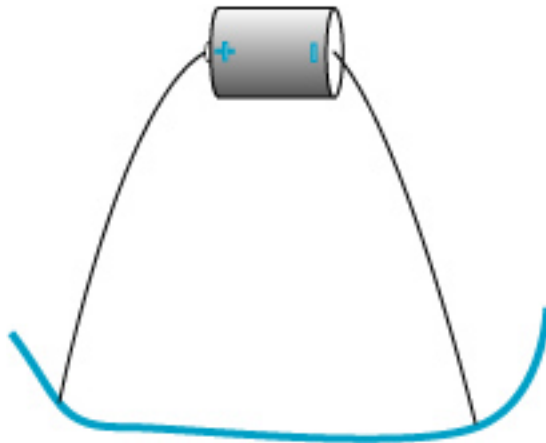


$$i_{2A} = n(2A)u|E| = 2i_A$$

If A doubles, the current doubles.


Nichrome wire

Two Batteries in Series

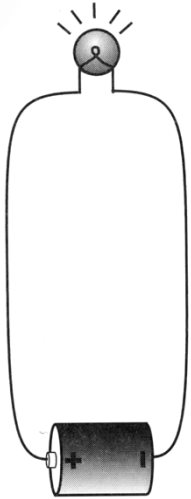

Why light bulb is brighter with two batteries?

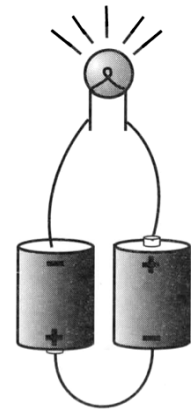Two batteries in series can drive more current:
 Potential difference across two batteries in series is $2emf \rightarrow$ doubles electric field everywhere in the circuit \rightarrow doubles drift speed \rightarrow doubles current.



$$emf - EL = 0$$

$$E = \frac{emf}{L}$$

$$i = nAuE = nAu \frac{emf}{L}$$

$$P_{1batt} = eLnAu \left(\frac{emf}{L} \right)^2$$

Work per second:

$$P = (q / T)EL = ieEL$$

$$P = nAueLE^2$$

$$2emf - EL = 0$$


$$E = \frac{2emf}{L}$$

$$i = nAu \frac{2emf}{L}$$

$$P_{2batt} = eLnAu \left(\frac{2emf}{L} \right)^2$$

$$P_{2batt} = 4 \times P_{1batt}$$

How Do the Currents Know How to Divide?

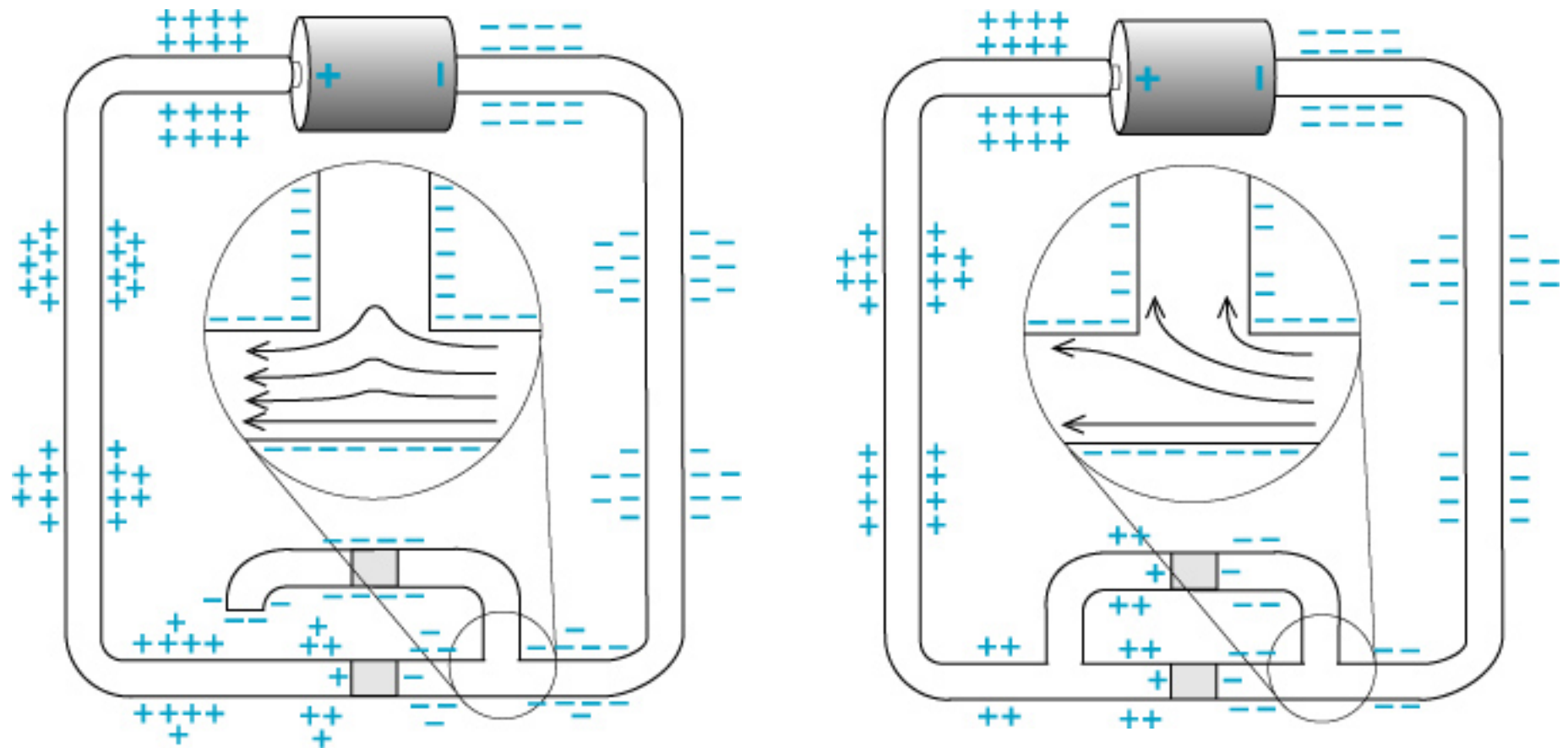

Today

- Transient response when connecting a circuit
- How long until steady state is reached?
- Introduction to Resistors
- Energy conservation in a circuit
- Kirchhoff's Voltage Loop Law
- Batteries