

Aung Kyi San
Summer 2012

ECE 20200 : Linear Circuit Analysis II
School of ECE, Purdue University


LECTURE 8

- Transfer Functions $H(s)$
- Impulse/ Step Responses
- Initial/ Final Value Theorems

Reference: Decarlo/Lin

PP 626-634

PP 726-729

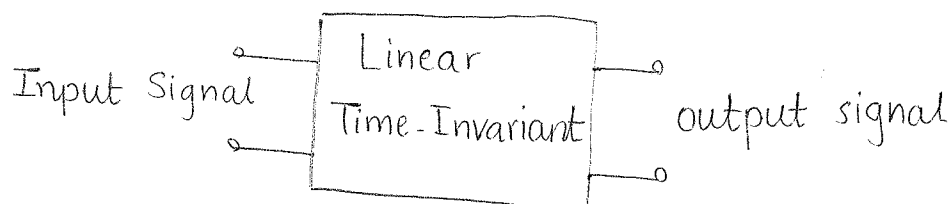Transfer Functions


Transfer Function $H(s) = \frac{\mathcal{L}[\text{output signal}]}{\mathcal{L}[\text{input signal}]}$

Interpretation: $H(s)$ denotes the Laplace transform of the circuit or more generally the Laplace transform of some linear, time-invariant physical process having input stimuli and observable responses.

Remark: $Z(s) = \frac{V_{out}(s)}{I_{in}(s)}$ and $Y(s) = \frac{I_{out}(s)}{V_{in}(s)}$

are special types of transfer functions.

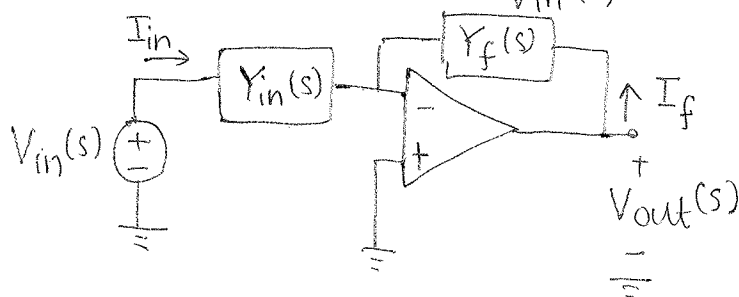Example 1: Show that $\frac{V_{out}(s)}{V_{in}(s)} = H(s) = \frac{-Y_{in}(s)}{Y_f(s)}$



$$I_{in}(s) = -I_f(s)$$

$$Y_{in}(s) V_{in}(s) = -Y_f(s) V_{out}(s)$$

$$\therefore \frac{V_{out}(s)}{V_{in}(s)} = -\frac{Y_{in}(s)}{Y_f(s)} = H(s)$$


Check!

$$H(s) = -\frac{Z_f(s)}{Z_{in}(s)}$$

Example 2: Find R_1, R_2, C_1 and R_3, R_4, C_2 so that

$$H(s) = \frac{30}{(s+5)(s+6)}$$

(Note: The solution is not unique)

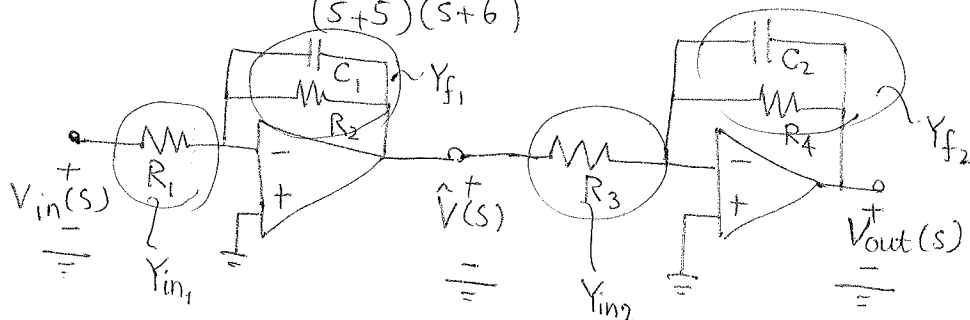

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{V_{out}(s)}{\hat{V}(s)} \cdot \frac{\hat{V}(s)}{V_{in}(s)} = \frac{30}{(s+5)(s+6)}$$

$$H_1(s) \cdot H_2(s) = \frac{30}{(s+5)(s+6)}$$

Using the result from example 1,

$$\begin{aligned} \left(-\frac{Y_{in1}(s)}{Y_{f1}(s)} \right) \left(-\frac{Y_{in2}(s)}{Y_{f2}(s)} \right) &= \frac{30}{(s+5)(s+6)} \\ &= \left(\frac{-5}{s+5} \right) \left(\frac{-6}{s+6} \right) \end{aligned}$$

Admittance formulas

$$Y_{in1}(s) = \frac{1}{R_1} = G_1$$

$$Y_{f1}(s) = C_1 s + G_2$$

$$\therefore H_1(s) = \frac{-Y_{in1}(s)}{Y_{f1}(s)}$$

$$= -\frac{G_1}{C_1 s + G_2}$$

$$= \frac{-5}{s+5}$$

$$\therefore G_1 = G_2 = 5 \text{ S}$$

$$C_1 = 1 \text{ F}$$

$$R_1 = R_2 = 0.2 \text{ } \Omega$$

$$Y_{in2}(s) = \frac{1}{R_3} = G_3$$

$$Y_{f2}(s) = C_2 s + G_4$$

$$H_2(s) = \frac{-Y_{in2}(s)}{Y_{f2}(s)}$$

$$= \frac{-G_3}{C_2 s + G_4}$$

$$= \frac{-6}{s+6}$$

$$G_3 = G_4 = 6 \text{ S}$$

$$C_2 = 1 \text{ F}$$

$$R_3 = R_4 = \frac{1}{6} \text{ } \Omega$$

Impulse and Step ResponsesSome Definitions

1. Impulse Response : Response of circuit to an impulse.

$$\delta(t) \longrightarrow \boxed{H(s)} \longrightarrow ?$$

$$\text{output} = h(t) = \mathcal{L}^{-1} [H(s) \cdot \mathcal{L}[\delta(t)]] = \mathcal{L}^{-1} [H(s)]$$

2. Step Response : Response of circuit to a step input

$$u(t) \longrightarrow \boxed{H(s)} \longrightarrow ?$$

$$\text{output} = s(t) = \mathcal{L}^{-1} [H(s) \cdot \mathcal{L}[u(t)]] = \mathcal{L}^{-1} [H(s) \cdot \frac{1}{s}]$$

3. Relationship between impulse response and step response

$$h(t) = \mathcal{L}^{-1}[H(s)] = \mathcal{L}^{-1}\left[s \frac{H(s)}{s}\right] = \frac{d}{dt} [s(t)]$$

$$\therefore \text{impulse response} = \frac{d}{dt} [\text{step response}]$$

Example 2 - continued.

$$\text{Recall } H(s) = \frac{30}{(s+5)(s+6)}$$

(a) Find the impulse response.

$$H(s) = \frac{30}{(s+5)(s+6)} = \frac{30}{s+5} - \frac{30}{s+6}$$

$$\therefore h(t) = \mathcal{L}^{-1}[H(s)] = 30e^{-5t}u(t) - 30e^{-6t}u(t)$$

(b) Find the step response.


$$\frac{H(s)}{s} = \frac{30}{s(s+5)(s+6)} = \frac{1}{s} - \frac{6}{s+5} + \frac{5}{s+6}$$

$$\therefore s(t) = \mathcal{L}^{-1}\left[\frac{H(s)}{s}\right] = u(t) - 6e^{-5t}u(t) + 5e^{-6t}u(t)$$

(c) Check the relationship.

$$\begin{aligned} \frac{d}{dt}(s(t)) &= \frac{d}{dt} \left[(1 - 6e^{-5t} + 5e^{-6t})u(t) \right] \\ &= (1 - 6e^{-5t} + 5e^{-6t}) \frac{d}{dt}(u(t)) + \frac{d}{dt}(1 - 6e^{-5t} + 5e^{-6t}) \cdot u(t) \\ &= (1 - 6e^{-5t} + 5e^{-6t})\delta(t) + (30e^{-5t} - 30e^{-6t})u(t) \\ &= (1 - 6 + 5)\delta(t) + 30e^{-5t}u(t) - 30e^{-6t}u(t) \\ &= 30e^{-5t}u(t) - 30e^{-6t}u(t) = h(t) \quad \checkmark \end{aligned}$$

Example 3.

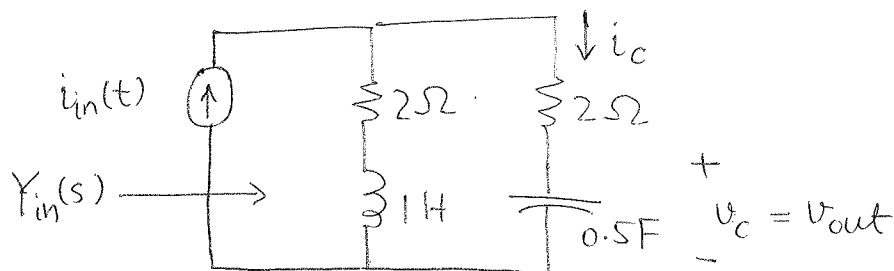(a) Find $H(s) = \frac{V_{out}(s)}{I_{in}(s)}$ Compute $Y_{in}(s)$ first.

$$Y_{in}(s) = \frac{1}{s+2} + \frac{1}{2+\frac{2}{s}} = \frac{1}{s+2} + \frac{0.5s}{s+1}$$

Then get $I_c(s)$ using current division

$$I_c(s) = \frac{\frac{0.5s}{s+1}}{\frac{0.5s}{s+1} + \frac{1}{s+2}} \quad I_{in}(s) = \frac{2s(s+2)}{s^2+4s+2} I_{in}(s)$$

$$\therefore V_c(s) = \frac{2}{s} \cdot I_c(s) = \frac{4(s+2)}{s^2+4s+2} I_{in}(s) = V_{out}(s)$$

$$\therefore \frac{V_{out}(s)}{I_{in}(s)} = \frac{4(s+2)}{s^2+4s+2} = H(s)$$

(b) Find the impulse response $h(t)$.

$$h(t) = \mathcal{L}^{-1}[H(s)] = (2e^{-3.4142t} + 2e^{-0.58579t})u(t)$$

(c) Find the step response $s(t)$

$$s(t) = \mathcal{L}^{-1}\left[\frac{H(s)}{s}\right] = (4 - 0.58579e^{-3.4142t} - 3.4142e^{-0.58579t})u(t)$$

* solutions to parts (b) and (c) are obtained using MATLAB

Initial/Final Value TheoremsFinal Value Theorem

Suppose $F(s) = \mathcal{L}[f(t)]$ only has poles in OLHCP except possibly a single pole at the origin (i.e., $s=0$). Then

$$\lim_{s \rightarrow 0} s F(s) = \lim_{t \rightarrow \infty} f(t) = f(\infty)$$

Example 1. Find $f(\infty)$ when $F(s) = \frac{(s+2)(s-1)}{s(s+1)(s+3)}$

$$f(\infty) = \lim_{s \rightarrow 0} s F(s) = \lim_{s \rightarrow 0} s \frac{(s+2)(s-1)}{s(s+1)(s+3)} = \frac{2(-1)}{(1)(3)} = -\frac{2}{3}$$

Example 2. Find $f(\infty)$ when $F(s) = \frac{1}{s^2+1}$

$$f(\infty) = \lim_{s \rightarrow 0} s F(s) = \lim_{s \rightarrow 0} s \frac{1}{s^2+1} = 0 \quad ?$$

$f(t) = \mathcal{L}^{-1}\left[\frac{1}{s^2+1}\right] = \sin(t)u(t)$ which does not have a limit
 \therefore Final value Theorem does not work here! ($\because s^2+1=0 \Rightarrow s=\pm j$ poles)

Initial Value Theorem

$\mathcal{L}[f(t)] = F(s) = \frac{n(s)}{d(s)}$ with $\deg(n(s)) < \deg(d(s))$. Then

$$\lim_{s \rightarrow \infty} s F(s) = f(0^+)$$

Example: Find $f(1^+)$ when $F(s) = \frac{e^{-s}}{s} \left[\frac{2.7183s+1}{s+3} \right]$

$$f(1^+) = \hat{f}(0^+) \text{ where } \hat{F}(s) = e^s F(s)$$

$$\begin{aligned} \hat{f}(0^+) &= \lim_{s \rightarrow \infty} s \hat{F}(s) = \lim_{s \rightarrow \infty} s e^s \frac{e^{-s}}{s} \left[\frac{2.7183s+1}{s+3} \right] \\ &= \lim_{s \rightarrow \infty} \left[\frac{2.7183s+1}{s+3} \right] \\ &= 2.7183 \end{aligned}$$