

Lec3

Wednesday, January 11, 2012
10:40 AM

HW2 due today.
HW3 is assigned. Due Monday.

Solution to Homework 1 is posted on the web
IMPORTANT: please check solution very carefully. The grader can only grade one question out of three. The rest is graded by effort. Hence, it is your responsibility to make sure your answer is correct.

Also, Please make sure you write your PUID on the upper-right corner of the first page!!! This saves enormous amount of time to sort the homework.

Review and Objectives

Wednesday, January 04, 2012



3:52 PM

Review:

- Charge Q
- Current I
 - o Rate at which charge is transported
- Voltage V
 - o Pressure caused by an electric field, making current flow
- Voltage source


$$I = \frac{\Delta Q}{\Delta t}$$

$$i(t) = \frac{dq(t)}{dt}$$

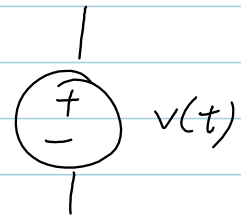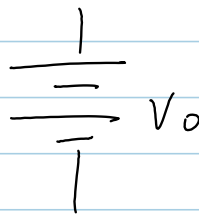

Very Important!

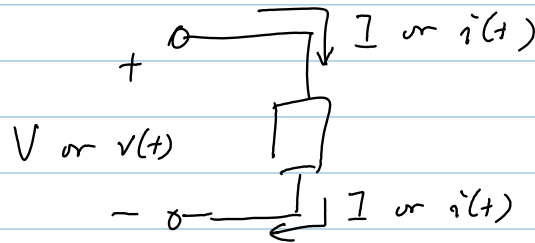- Passive sign convention: labeling of the reference directions of general two terminal circuit elements
 - o Current in = current out



- Ohm's Law with passive sign convention

$$V = IR$$

- Absorbed power with passive sign convention labelling

- o DC case:

$$P_{CE} = VI$$

$$P_{del}^S = VI \leftarrow \text{passive sign convention for the other parts (not the source)}$$

- o General case:

$$p_{ce}(t) = v(t) i(t) = v_{AB}(t) i(t) = -v_{BA}(t) i(t)$$

○ Energy/work:

$$W(t) = \int_{-\infty}^t p(\tau) d\tau = \int_{-\infty}^t v(\tau) i(\tau) d\tau$$

$$\text{or } \int_{t_0}^{t_1} p(\tau) d\tau$$

Objectives:

- Independent and dependent/controlled sources
- Ohm's Law

Wednesday, January 04, 2012
2:57 PM

Absorbed power

$$P_6 = 10 \times (-2) = -20 \text{ W} \quad (\text{probably a source too})$$

$$P_{del} = 14 \times 1 = 14 \text{ W}$$

11 "Conservation of power"

"Conservation of power"

- Actually $P_6 = -20\text{W} < 0$

Total delivered power from all sources
 $= P_{\text{del}} + (-P_6) = 34\text{W}$

Total absorbed power by all (other) circuit elements
 $= 34\text{W}$

$$\sum_{\text{over all sources}} P_{\text{delivered}} = \sum_{\text{over all CEs}} P_{\text{absorbed}}$$

- If we treat the absorbed power of the source
 $= (-P_{\text{del}})$

Then

$$-P_{\text{del}} + P_1 + P_2 + P_3 + P_5 + P_6 = 0$$

$$\sum_{\substack{\text{over} \\ \text{both sources} \\ \& \text{CEs}}} P_{\text{absorbed}} = 0$$

$$\sum P_{\text{delivered}} = 0$$


over both
sources &
CEs

2 terminal circuit element

Saturday, January 07, 2012

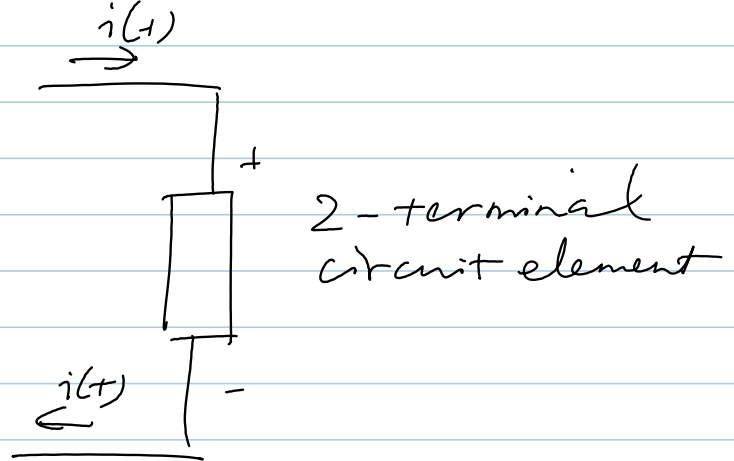10:39 AM

- Battery & resistors are ^{examples} of a 2-terminal circuit element




Current in = Current out

Analogy : Water into a pipe
= water out of a pipe

Current source

Thursday, January 05, 2012
4:16 PM

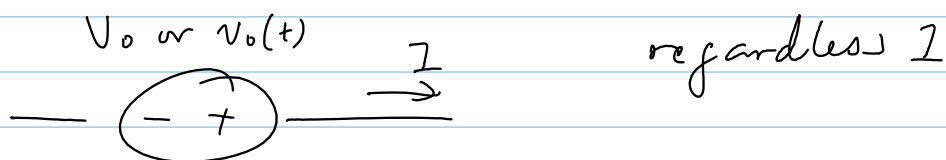
- We have seen the battery, which is a voltage source.
- An ideal/independent voltage source produces a constant voltage drop under all operating conditions, i.e., independent of load.




- Note that we often do not apply the passive-sign convention to the source


Current Source

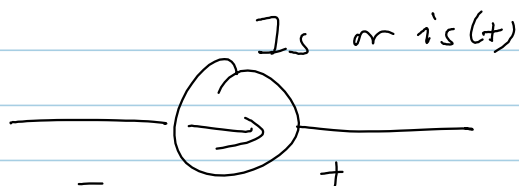- Similarly, an ^{ideal} current source provides a constant current I_s , or a time-varying current $i_s(t)$, to a circuit under all operating conditions.



Ex

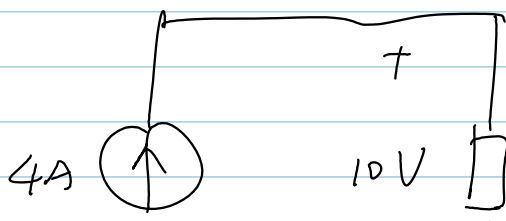

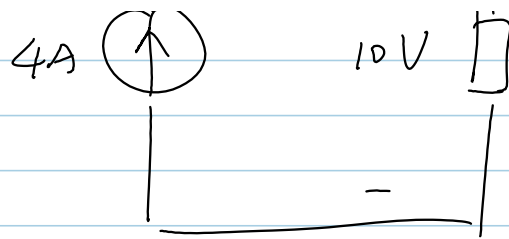



What is the power supplied by the current source?

$$10 \times 4 = 40 \text{ W}$$

Short circuit and open circuit - 10min

Monday, January 09, 2012
1:23 PM

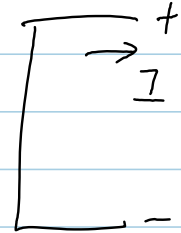
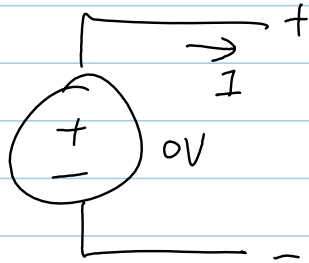
- What happens to a voltage source with a voltage of $0V$?



- No matter what current flows through, the voltage drop is zero

short circuit

- A current source with $0A$

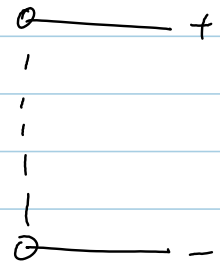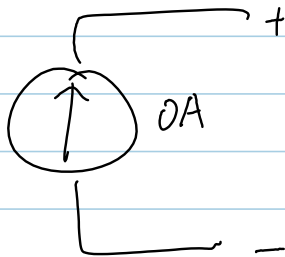

open circuit



Dependent/controlled sources-10min


Thursday, January 05, 2012
4:23 PM


- The voltage or current of the controlled sources depend explicitly on the voltage or current in some other part of the circuit


- e.g. an amplifier

- an analogy: the interest rate at which banks lend money to customers depends on the rate set by the Federal Reserve

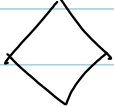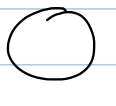-  : dependent source  : independent source

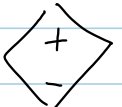
 : dependent voltage source


 : dependent current source

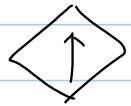$2V_a$  : dependent relationship

Four types

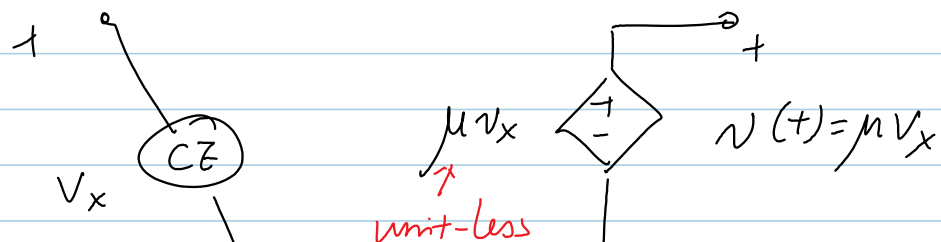- VCVS (voltage controlled voltage source)



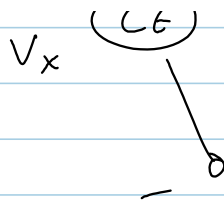


unit-less



- CCVS (current controlled voltage source)




$r_m i_x$
unit: Ω

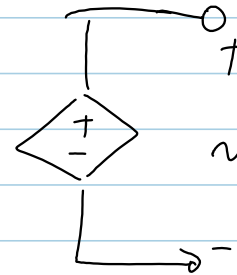


$$v(t) = r_m i_x$$

common mistake: thinking that this is a current source.

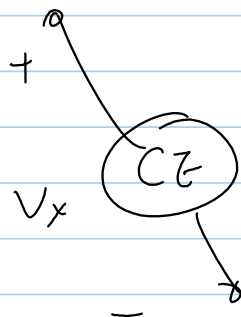- VCCS (Voltage controlled current source)





$g_m v_x$
unit: S

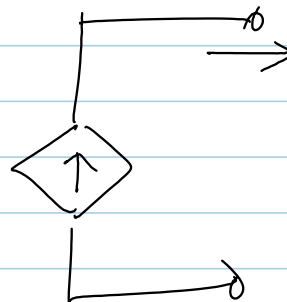


$$i(t) = g_m v_x$$

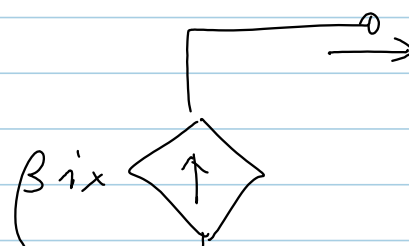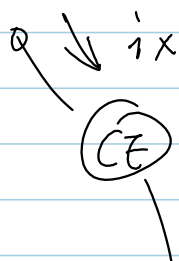- CCCS (current controlled current source)



$$i(t) = \beta i_x$$

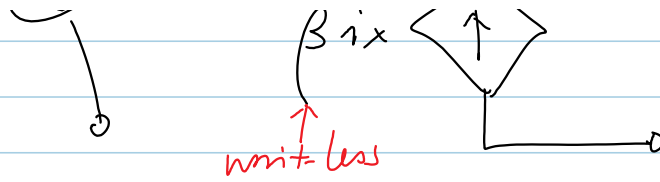

Examples-10min

Thursday, January 05, 2012
5:48 PM

- We have known a number of relationships

- Ohm's Law: $I = \frac{V}{R}$


- power: $P = VI$

- Conservation of power

$$P_{del} = P_{abs}$$

It turns out that with these we can already compute many interesting results.

Ex 3.1 (P34)

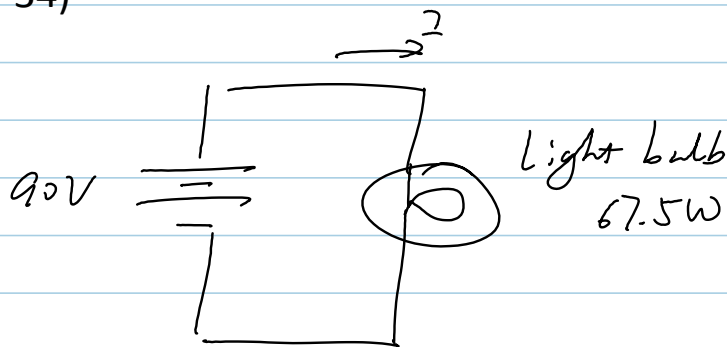

Find the current I and the "hot" resistance of the light bulb.

Solution:


Step 1: Find I using power relationship

$$I = \frac{P_{\text{bulb}}}{V_{\text{in}}} = \frac{67.5}{90} = 0.75 \text{ A}$$

Step 2: Find R using Ohm's Law

$$R = \frac{V_{\text{in}}}{I} = \frac{90}{0.75} = 120 \Omega$$

Ex 3.2

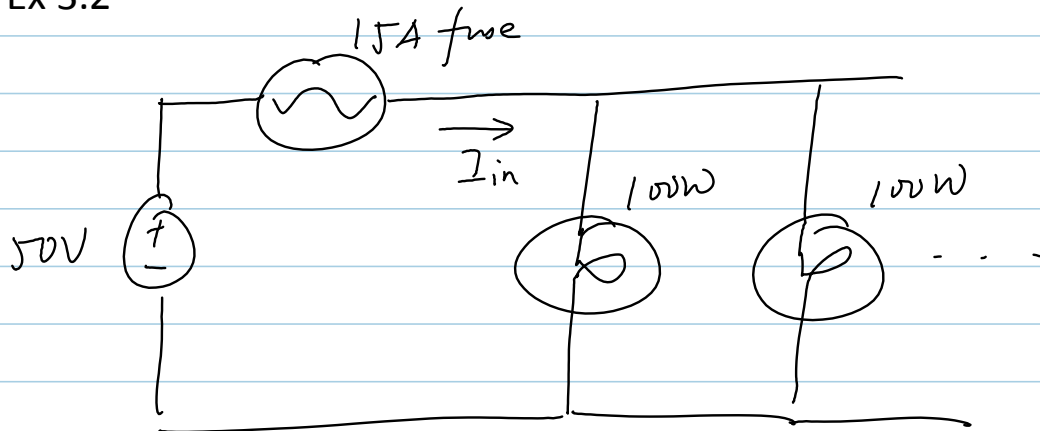

How many 100W bulbs can be connected in parallel before the fuse will blow?

Solution:

- Step 1: Compute the max power delivered by the source

$$P_{\text{max}} = 50 \times 15 = 750 \text{ Watts}$$

This is also the max power that the bulbs can absorb

- Step 2 : Find the max # of bulbs

$$N \times 100 \leq 750$$


$$N \leq 7.5$$

$$\Rightarrow N = 7$$

More examples-10min

Saturday, January 07, 2012
10:38 AM

Ex 3.3

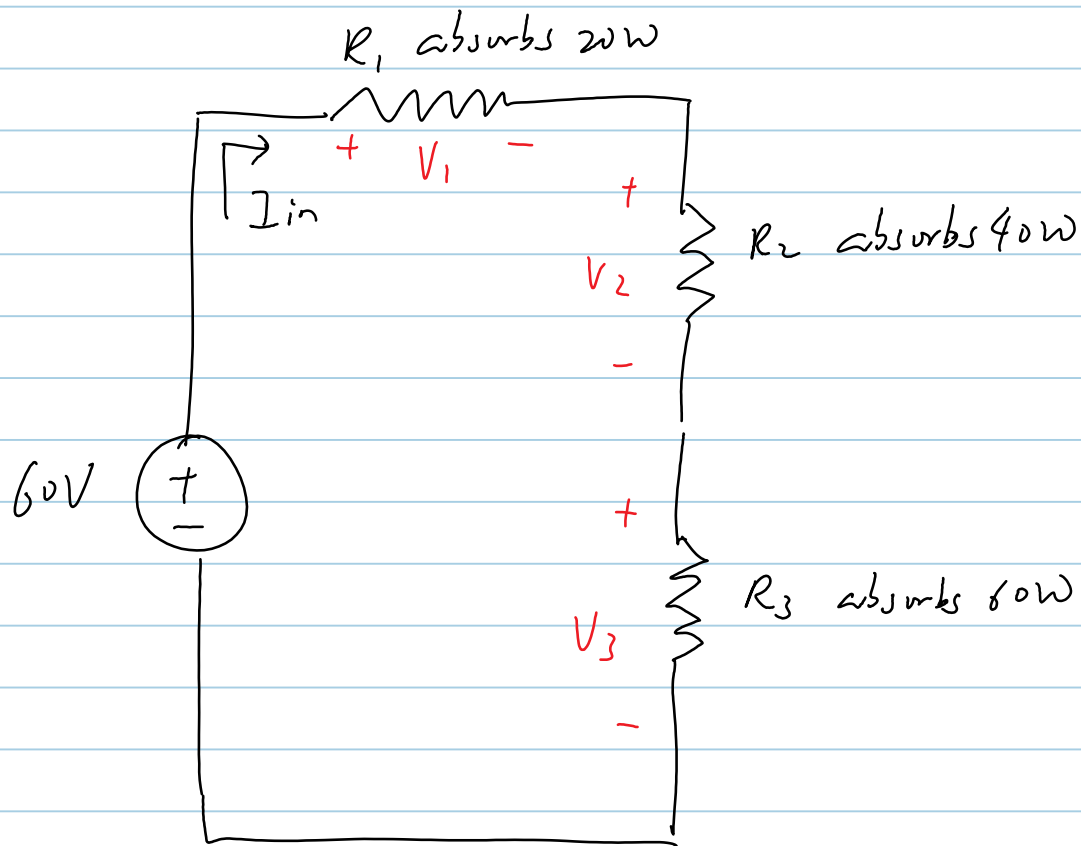

Find

- (i) I_{in}
- (ii) V_i , the voltage across each resistor
- (iii) Check that the source voltage is the sum of the resistor voltages
- (iv) Find the resistance of each resistor
- (v) Find the effective resistance seen by the source

Solution =

(i) Compute power delivered by the source using

Conservation

$$P_{del} = 20 + 40 + 60 = 120 \text{ Watts}$$

Compute I_{in} using power relationship

$$I_{in} = \frac{P_{del}}{V_{in}} = \frac{120}{60} = 2 \text{ A}$$

(ii) Since each element is a 2-terminal circuit element, the current entering equals the current leaving

Find voltage V_i using power relationship

$$V_1 = \frac{20}{2} = 10 \text{ V}$$

$$V_2 = \frac{40}{2} = 20 \text{ V}$$

$$V_3 = \frac{60}{2} = 30 \text{ V}$$

Note the passive-sign convention!

(iii) $V_{in} = V_1 + V_2 + V_3 = 60 \text{ V}$ ✓

This is known as KVL, which we will study in further details soon

(iv) Find resistance of each resistor using Ohm's Law.

$$R_1 = \frac{V_1}{I_{in}} = \frac{10}{2} = 5 \Omega$$

$$R_2 = \frac{V_2}{I_{in}} = \frac{20}{2} = 10\Omega$$

$$R_3 = \frac{V_3}{I_{in}} = \frac{30}{2} = 15\Omega$$

Alternately, note that

$$P = VI = \frac{V^2}{R} = I^2 R$$

Hence, you can also find R using these formulas

(v) Find the effective resistance seen by source using Ohm's Law

$$R_{eff} = \frac{V_{in}}{I_{in}} = \frac{60}{2} = 30\Omega$$


Note that

$$R_{eff} = R_1 + R_2 + R_3$$

This is a known property of series resistors, which we will also study in Ch. 4.

Take home

Saturday, January 07, 2012
10:52 AM

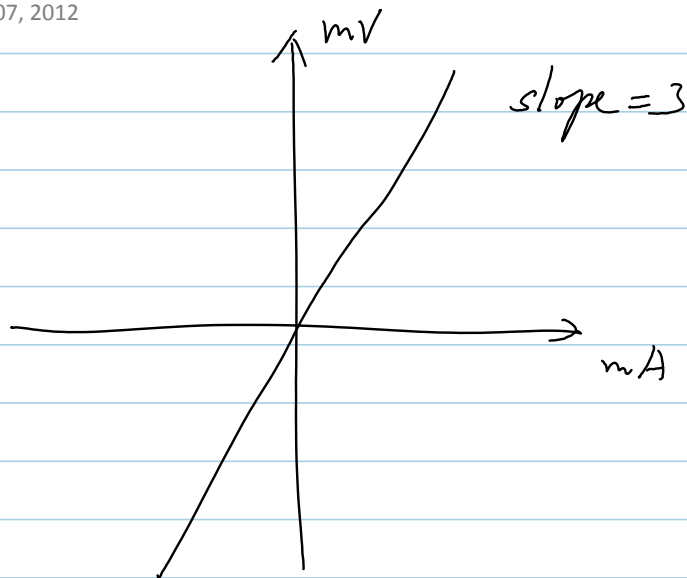

A circuit has the $v-i$ diagram above,
What is the equivalent circuit element that could
replace it?

— A resistor with $R = 3\Omega$.