

Lec2

Monday, January 09, 2012
2:21 PM

Homework set 1 is due today. (last problem should be prob.8)

Homework set 2 is assigned. Due on Friday.

TA office hours and location are available at the course homepage.

Review and objective

Tuesday, January 03, 2012
4:19 PM

Review:

- Electrical Charge Q
 - o Positive and negative charge
- Electrical current I
 - o Flow rate of charge
 - o Flow of negative charge viewed as flow of positive charge in the reverse direction
 - o Positive and negative current

Objective:

- Introduce the notion of voltage
- Introduce voltage source/battery
- Introduce the notion of 2-terminal circuit element
- Study absorbed and delivered power

$$I = \frac{\Delta Q}{\Delta t}$$

$$i = \frac{dq}{dt}$$

Charge revisited-10min

Tuesday, January 03, 2012
4:07 PM

- Conversely, the "sum" of the instantaneous currents through a cross-sectional area from $-\infty$ to t equals the net charge transported through the boundary

$$q(t) = \int_{-\infty}^t i(\tau) d\tau = \text{"Area below } i(t)\text{"}$$

Ex 1.4. Suppose that $i(t)$ is given as follows



Find $q(t)$

$$\begin{aligned} q(t) &= \int_{-\infty}^t i(\tau) d\tau = \int_{-\infty}^0 i(\tau) d\tau + \int_0^t i(\tau) d\tau \\ &= \int_0^t i(\tau) d\tau \end{aligned}$$

Case 1: $0 \leq t < 1$. Here $i(t) = 2t$


$$q(t) = \int_0^t 2\tau d\tau = \tau^2 \Big|_0^t = t^2 \text{ (C)}$$

Case 2: $1 \leq t < 2$. Here $i(t) = -2t + 4$

$$\begin{aligned} f(t) &= f(1) + \int_1^t i(\tau) d\tau \\ &= 1 + \int_1^t (-2\tau + 4) d\tau \\ &= 1 + \left[-\tau^2 + 4\tau \right]_1^t \\ &= 1 + \left[-t^2 + 4t - (-1 + 4) \right] \\ &= -2 + 4t - t^2 \quad (c) \end{aligned}$$


Case 3: $t \geq 2$

$$\begin{aligned} f(t) &= f(2) + \int_2^t i(\tau) d\tau \\ &= f(2) = 2 \quad (c) \end{aligned}$$

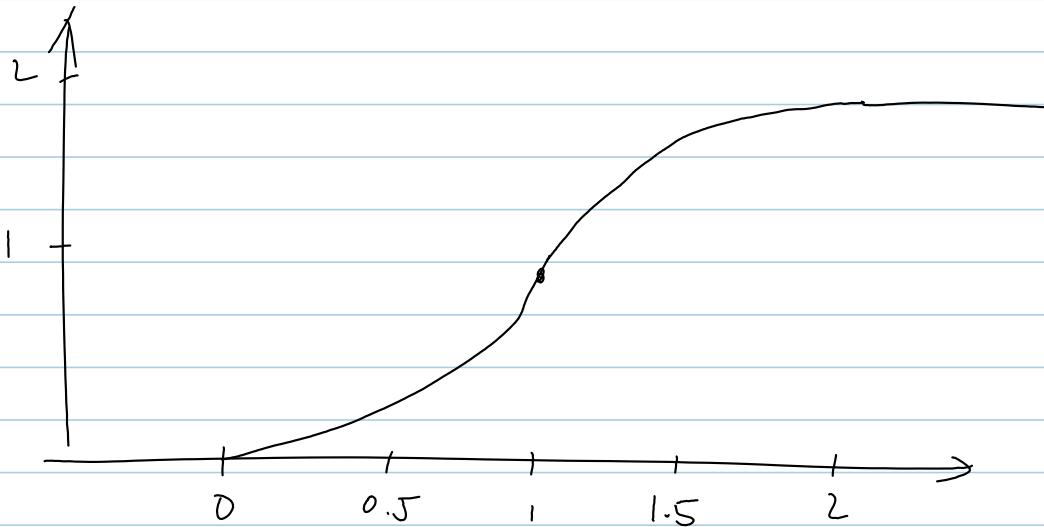

Ex 1.5 (P7)

May skip

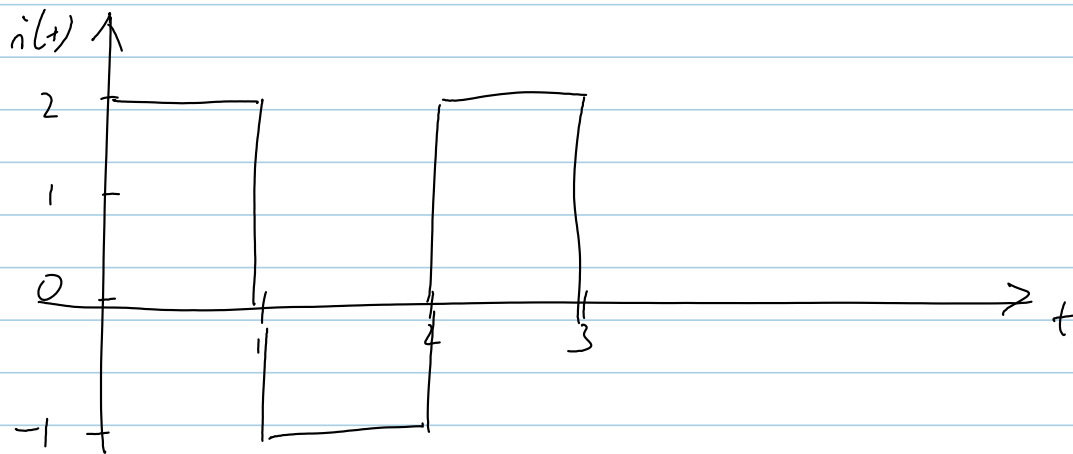

Find the total charge Q transported.


The total charge equals the total area beneath the curve.

$$= 2 - 1 + 2 = 3 \text{ (C)}$$

Voltage

Tuesday, January 03, 2012
4:19 PM

Recall the water analogy

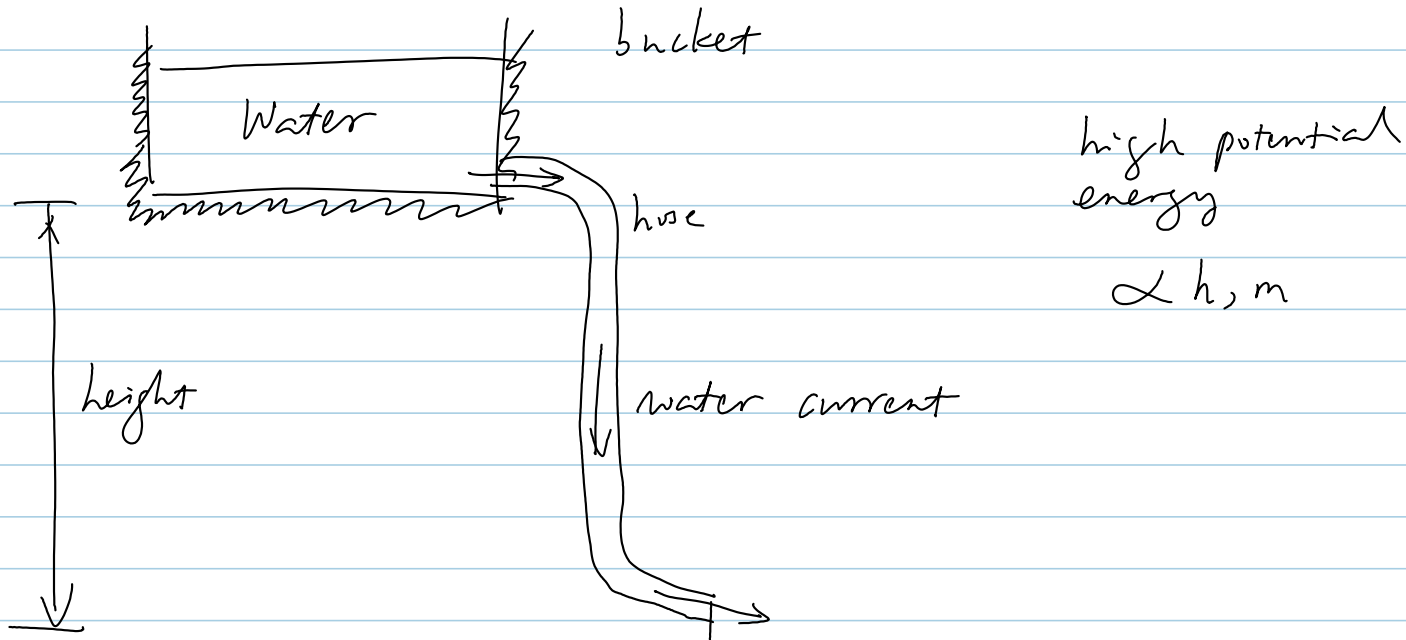

Water bucket / hose	Electrical Circuit
Water Mass	Electrical charge
Water current	Electrical current
Height	Voltage


What causes current to flow?

- Gravity forces water to flow from a higher elevation to a lower elevation.

- Water mass at higher altitude contains more potential energy $\propto h$ ($=mgh$)

- As water flows, potential energy is converted to kinetic energy

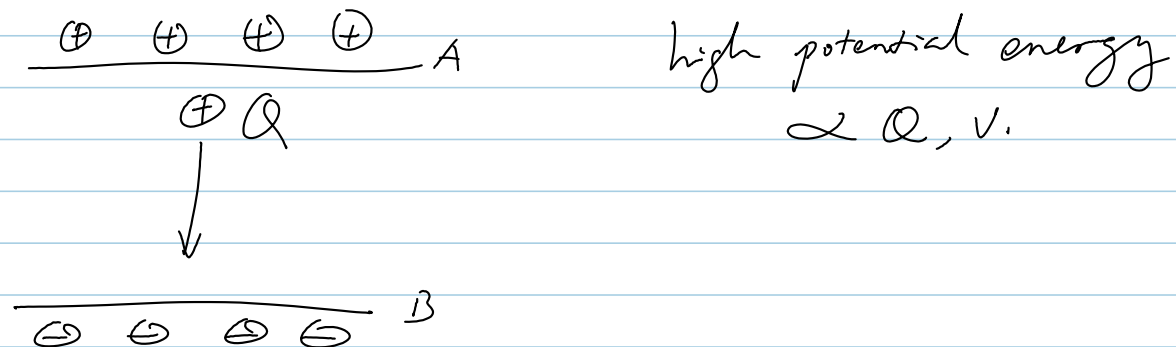- Similarly, due to electrical forces, positive charge tends to flow from a positively charged plate to a negatively charged plate



- Thus, positive charge at point A has higher potential energy.

- As it moves from A to B, its potential energy is converted to other form of energy, e.g. heat.

- Similar to height, the potential energy at A is proportional to the "voltage" drop between A & B. "potential difference"

Voltage (potential difference A \rightarrow B) / unit


$$= \frac{\text{Energy converted (Joules)}}{\text{Quantity of Charge Moved (C)}}$$

- Unit: Volt $1 \text{ Volt} = 1 \text{ J/C}$

- V :
- $v(t)$:



Battery

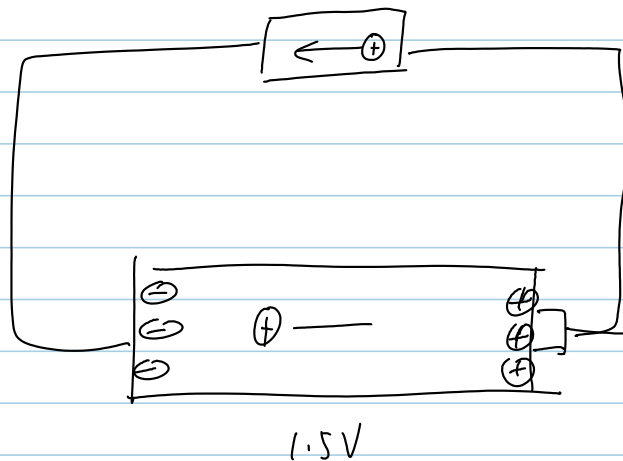- In battery, such a voltage is produced by accumulation of charged particles at different terminals due to the chemistry reaction.



energy released
 $= 1.5V \times Q$

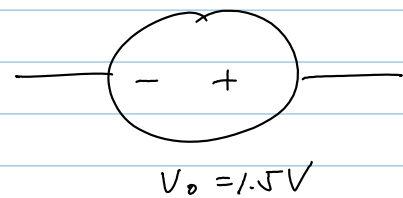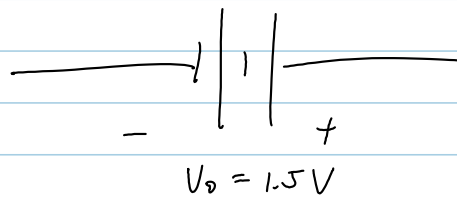- A battery produces a nearly-constant voltage, which is determined by the chemistry. e.g. 1.5V.




- Then, when the two sides are connected,

e.g. by a coil, current flows,
which converts potential energy to heat


Chemical energy \rightarrow electrical energy
 \rightarrow heat

Positive and negative voltage(drop)

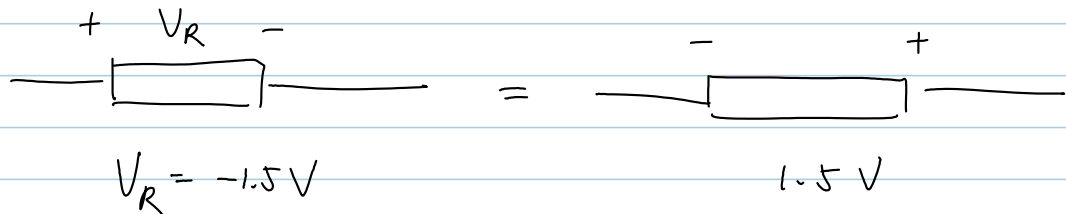
- The plus and negative sign represent the polarity
- Like for current, in circuit analysis we often need to guess the polarity in advance. What if the actual polarity is the reverse?




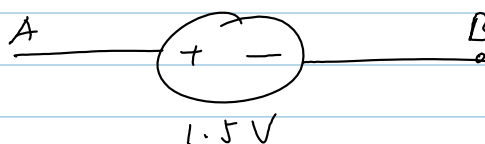- useful if we do not know the voltage drop direction in advance.
- Or, we can use V_{AB} to denote the voltage drop from A to B




$$V_{AB} = 1.5 V$$
$$V_{BA} = -1.5 V$$

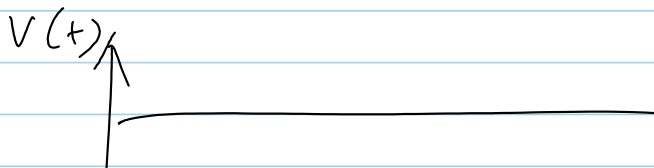

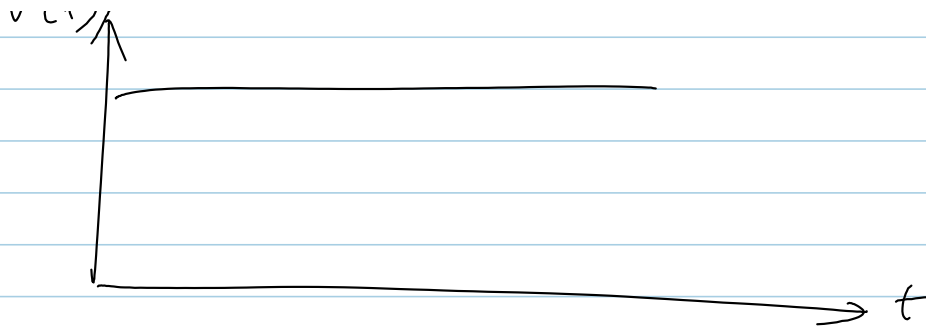

A DC battery (direct current)

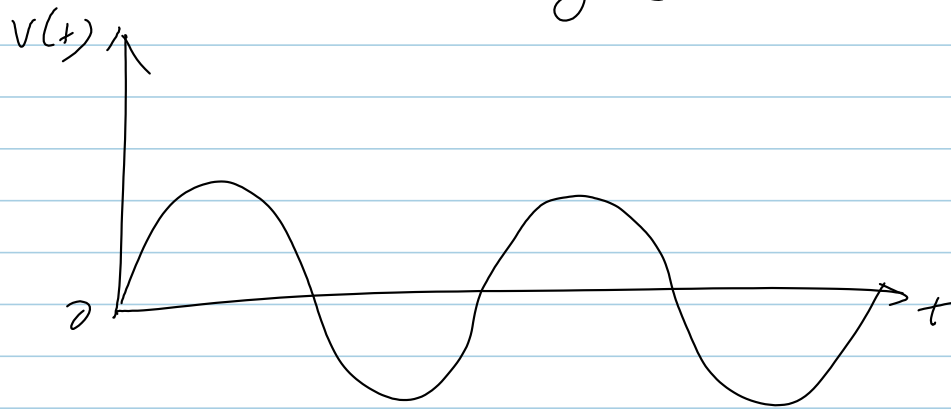


AC voltage source (alternate current)

Voltage example-10min

Tuesday, January 03, 2012
5:08 PM

Ex 2.1 (P13)

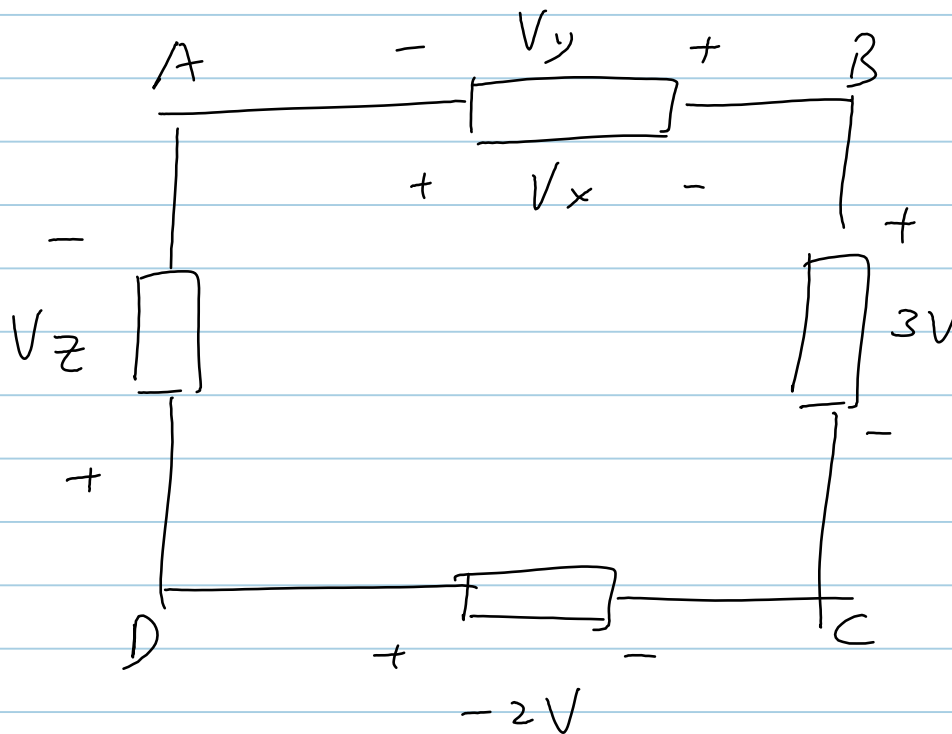

Suppose $V_{AB}=4V$, $V_{AD}=9V$

Find V_x , V_y , V_z , V_{BC} , V_{CD}

$$V_x = V_{AB} = 4V$$

$$V_y = V_{BA} = -V_{AB} = -4V$$

$$V_z = V_{DA} = -V_{AD} = -9V$$

$$V_{BC} = 3V$$

$$V_{CD} = -V_{DC} = -(-2V) = 2V$$

Resistance and ohm's law-10min

Thursday, January 05, 2012
4:33 PM

- Ohm found that for many materials (metal, etc.), the current through $\hat{}$ is proportional to the voltage
a device made of it


$$I \propto V$$

Write $I = \frac{V}{R} = GV$, $V = IR$

The proportional constant R is called resistance, the inverse G is called the conductance of the device.

- Such a device is called a Resistor
- This relationship between V & I is called Ohm's Law

Ohm's Law

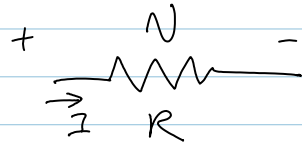

$$V = IR, \quad I = \frac{V}{R}$$
$$V(+)=i(+)\,R, \quad i(+)=\frac{V(+)}{R}$$

- Note the signs:
 - Water flows from high altitude to low altitude
 - Electric current flows from high voltage to low voltage.


— Basic unit:

— Resistance R : Ohm (Ω)


$$1\Omega = \frac{1V}{1A}$$

— Conductance G : Siemens (S or \mathcal{S})

Here is a problem:

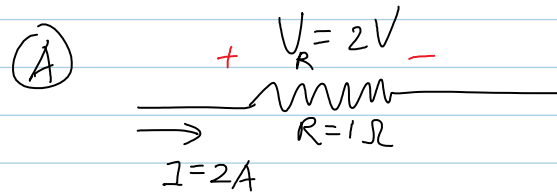

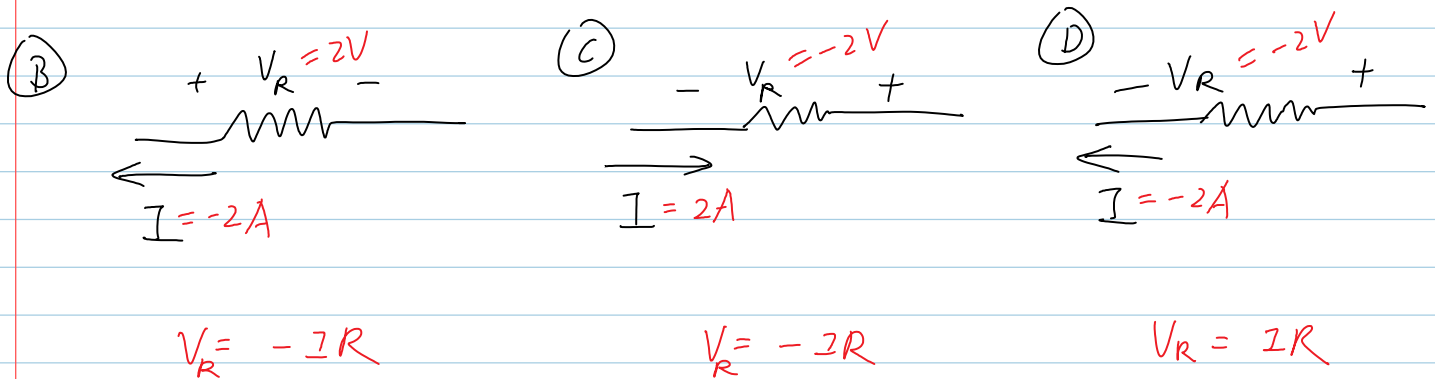— What if I put the reference directions differently?



— Problem: When do I need to/not to add the minus sign??


- For both cases A and D, the reference directions of voltage & current are "naturally compatible"
- Current flows from high voltage to low voltage
- Not for cases B and C

Passive sign convention-5min

Tuesday, January 03, 2012
5:15 PM

Passive sign convention

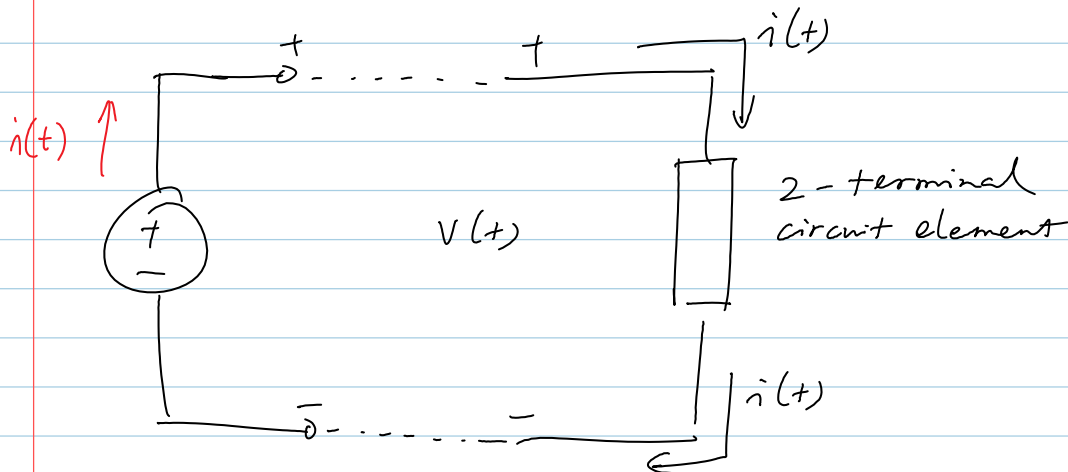- For a passive component (resistor, inductor, capacitor, i.e. RLS)



- The passive-sign convention is said to be followed when we take the reference direction of current from \oplus to \ominus of the reference direction of voltage drop.

- For a resistor:

- positive voltage^{drop} will then produce positive current
- negative voltage^{drop} will produce negative current

} Ohm's Law
without additional
minus sign!

- The current into one terminal equals the exit current

-
- The situation is however different at the battery (or voltage source)

- If voltage is positive, usually current flow $\ominus \rightarrow \oplus$ inside the battery
- ↑
An active component
-


This convention is very important:

- Critical for writing down Ohm's Law correctly
- Most common mistakes for ECE201 students
(Imagining omitting a minus sign in equations)
- Also important for power calculation

Example - 5min

Tuesday, January 08, 2013
11:50 AM

Ex 2.2

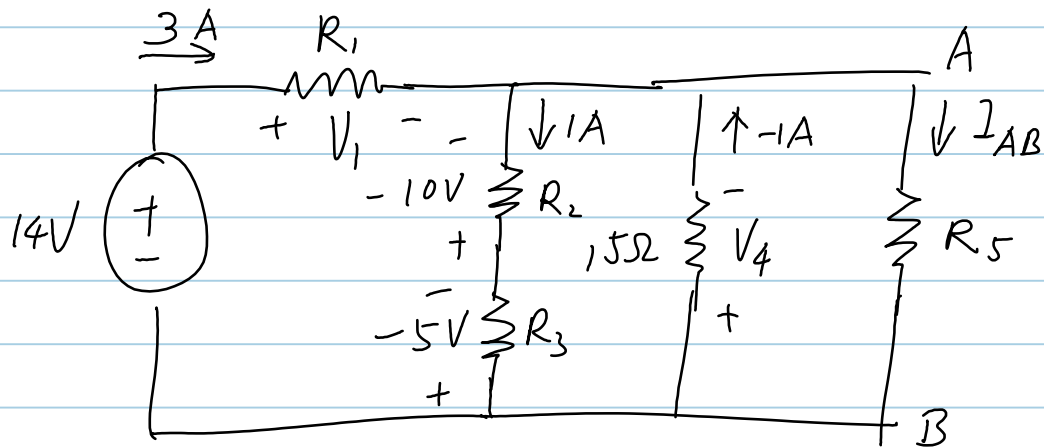

Which of the following relationship does not follow the passive-sign convention? Which of them is incorrect?

(1) For R_1 : $V_1 = 3R_1$

X (2) For R_2 : $-10 = 1R_3$


(3) For R_3 : $-5 = -(1R_3)$

(4) For 15Ω : $V_4 = (-1) \times 15$

X (5) For R_5 : $V_{BA} = I_{AB} R_5$

Power-10min

Wednesday, January 04, 2012
2:36 PM

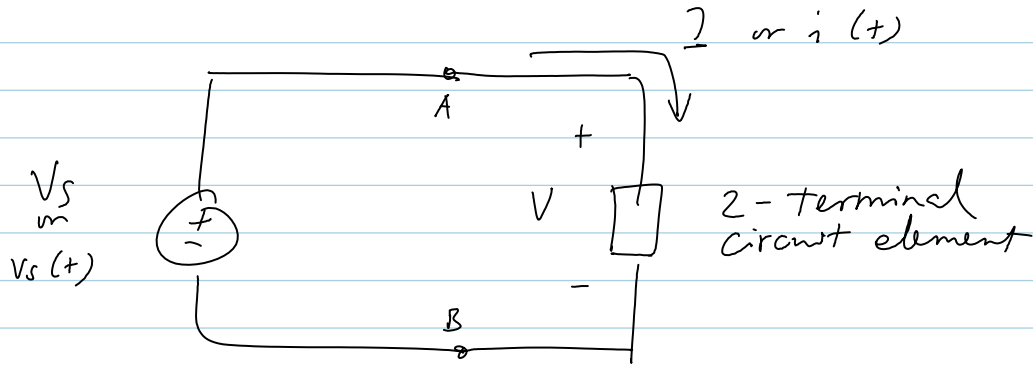

Assume the passive-sign convention on any circuit element.

The power absorbed by the circuit element in Watts is given by

- DC case:

$$P_{CE} = V \cdot I = \frac{V \cdot \Delta Q}{\Delta t} \quad \leftarrow \text{energy released}$$

$$P_{CE} = V \cdot I = V_{AB} \cdot I = V_S \cdot I$$

due to KVL, which we will study soon.

(Note the signs!)

- Instantaneous absorbed power (depends on t)


$$p_{CE}(t) = V(t) \cdot i(t) = v_{AB}(t) \cdot i(t) = v_s(t) \cdot i(t)$$

- Integrating power over time leads to the total energy consumed

$$W(t) = \int_{-\infty}^t p(\tau) d\tau = \int_{-\infty}^t v(\tau) i(\tau) d\tau$$


Over finite intervals $\int_{t_0}^{t_1} p(t) dt$

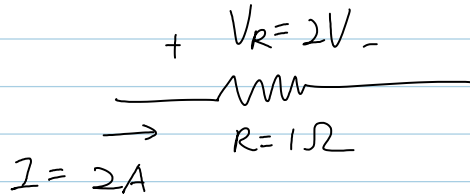For a resistor (e.g. a heating coil on oven)




$$P_{abs}^R = V_R I = 4W$$

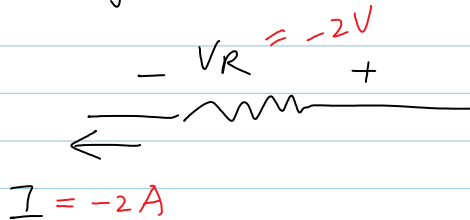- If the reference directions are ^{both} reversed



$$P_{abs}^R = V_R I = 4W$$

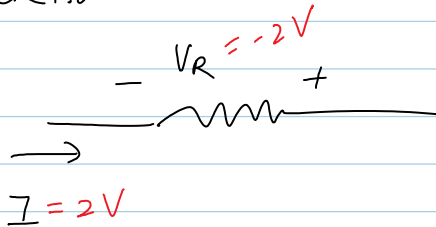
- As long as the passive-sign convention is followed, the absorbed power of a resistor is always positive (good!)
- The following represents a case not following the passive-sign convention



$$V_R \cdot I = -4W$$

X
Avoid!!!

What about the source?

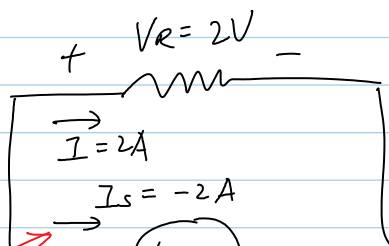


passive-sign
for the source

$$P_{abs}^S = V_S I_S = -4W$$

$$P_{del}^S = V_S I = 4W$$

due to KCL, which we will study soon.

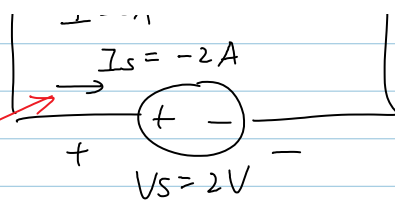

$$P_{abs} = V_S I_S = -4 \text{ W}$$

$$P_{del} = V_S I = 4 \text{ W}$$

passive-sign for other parts of the circuit

- If we had applied the passive-sign convention to the source, the absorbed power would have been negative!
- This is because the source is delivering power, not absorbing power.

If you want to compute the delivered power from a source, apply the passive sign convention to the opposite components

- Note \pm label on voltage source
- current direction leaving the source \oplus
- Delivered power

$$\begin{aligned} P_{del} &= V_S I \\ P_{del} &= V_S (+) i (+) \end{aligned}$$

positive value indicating that power is delivered from the source

- This is the same expression as P_{abs}^{CE}

$$P_{del}^S = P_{abs}^{CE}$$

What is delivered from the battery is consumed by the other circuit elements!

- Conservation of power.

$$P_{abs}^S = -P_{del}^S$$

Summary:


- Positive P_{abs} means consuming power
negative P_{abs} means delivering power
- Positive P_{del} means delivering power
negative P_{del} means absorbing power

Example

Wednesday, January 04, 2012
2:47 PM


Ex 2.3. Goal: Practice the use of passive sign convention!!!

Find P_{del}^S and P_{abs}^{CE}

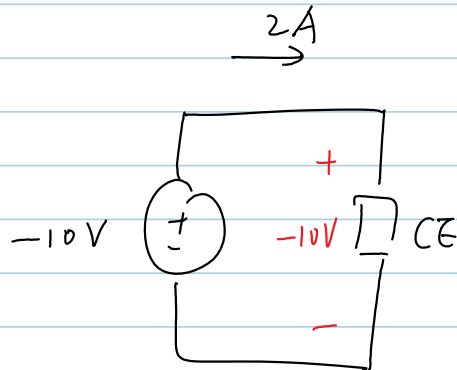


$$P_{del}^S = -10 \times 2 = -20W \quad \text{absorbing}$$
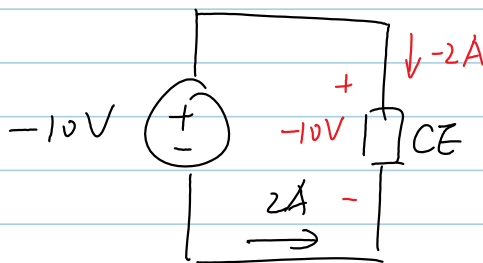
$$P_{abs}^{CE} = (-10) \times 2 = -20W \quad \text{delivering}$$




$$P_{del}^S = (-10) \times (-2) = 20W$$
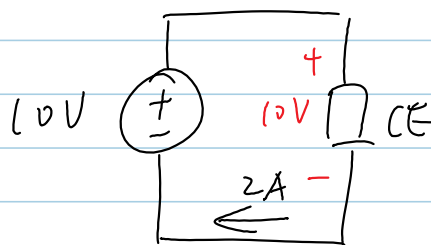
$$P_{abs}^{CE} = (-10) \times (-2) = 20W$$



$$P_{del}^S = 10 \times 2 = 20W$$

$$P_{abs}^{CE} = 10 \times 2 = 20W$$

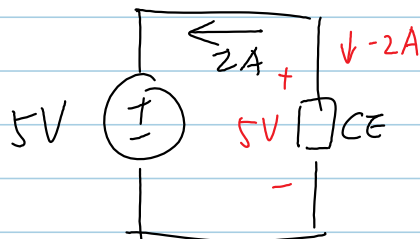


$$P_{del}^S = 5 \times (-2) = -10W$$

$$P_{abs}^{CE} = 5 \times (-2) = -10W$$

- P_{del}^S & P_{abs}^{CE} are essentially the same expression

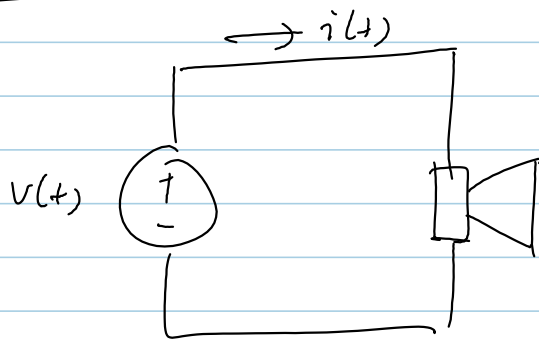— $P_{del}^S = P_{abs}^{CE}$ — Conservation of Power.



May skip

$$v(t) = 40 \sin(200\pi t) \quad i(t) = 5 \sin(200\pi t)$$

$$p(t) = v(t) \cdot i(t) = 200 \sin^2(200\pi t)$$