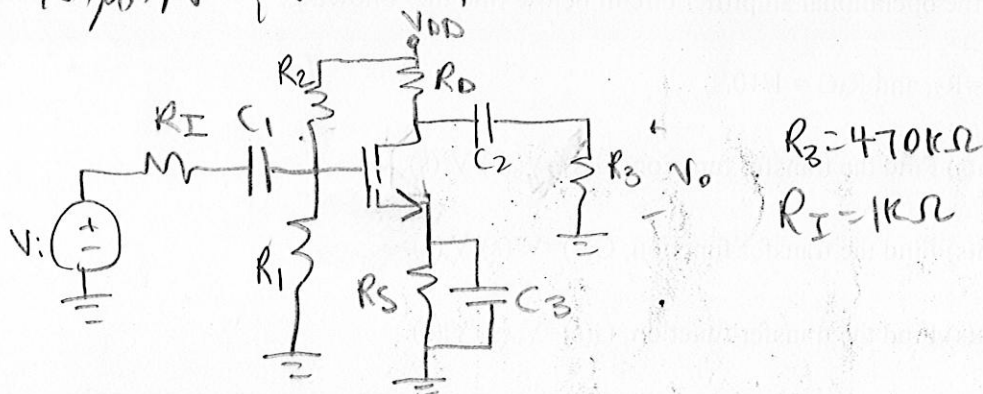


14.91 a)

$R_1 = 500k\Omega$, $R_2 = 1.4M\Omega$, $K_S = 27k\Omega$, $R_D = 75k\Omega$, $V_{DD} = 15V$
 $K_n = 400\mu A/V^2$, $V_{TN} = 1V$, $\lambda = 0.02V^{-1}$, p14.1(d)



Common Source amplifier

eq. 14.107

$$\frac{1}{\omega C_1} \ll R_I + R_{in}$$

$$R_{in} = R_1 // R_2 // R_{ig}, \quad R_{ig} = \infty \text{ for FET}$$

$$C_1 \gg \frac{1}{\omega (R_I + R_1 // R_2)} = \frac{1}{(500Hz)(2\pi)(1k\Omega + 500k\Omega // 1.4M\Omega)} = 862pF$$

choose $C_1 \approx 9.1nF \approx 10(862pF)$ next standard value greater

$$C_2 \gg \frac{1}{\omega (R_{out} + R_3)} = \frac{1}{(500Hz)(2\pi)(74k\Omega + 470k\Omega)} = 5.85pF$$

$$R_{out} = R_D // R_{iD} = R_D // r_o(1 + g_m R_S) = 74.2k\Omega$$

DC Analysis: $I_D = 85.0\mu A$, $V_{GS} = 1.65V$, $V_{DS} = 6.32V$
(Not shown)

$$r_o = \frac{662k\Omega}{1 + 2V_{DS}} = \frac{2I_D}{V_{GS} - V_{th}}$$

$$g_m = 261\mu S$$

choose $C_2 \approx 6nF \approx 10(5.85pF)$ next standard value greater

14.91 (con) a) (con)

$$C_3 \gg \frac{1}{\omega [R_4' // (R_S' + \frac{1}{g_m})]} = \frac{1}{(500\text{Hz})(2\pi) [R_S // \frac{1}{g_m}]} = 95\text{nF}$$


$$R_4 = R_S, \quad R_S' = 0\Omega$$

So choose $\boxed{C_3 \approx 10(95\text{nF}) = 950\text{nF} \approx 1\mu\text{F}}$ or closest standard value $\geq 950\text{nF}$

b) cutoff freq. for C_1, C_2 is about 50Hz as chosen, so they can be neglected

$$C_3 = \frac{1}{(4000\text{Hz})(2\pi) [R_S // \frac{1}{g_m}]} = \boxed{11.9\text{nF}} \text{ for } 4000\text{Hz cutoff freq.}$$

14.94 part (a) only

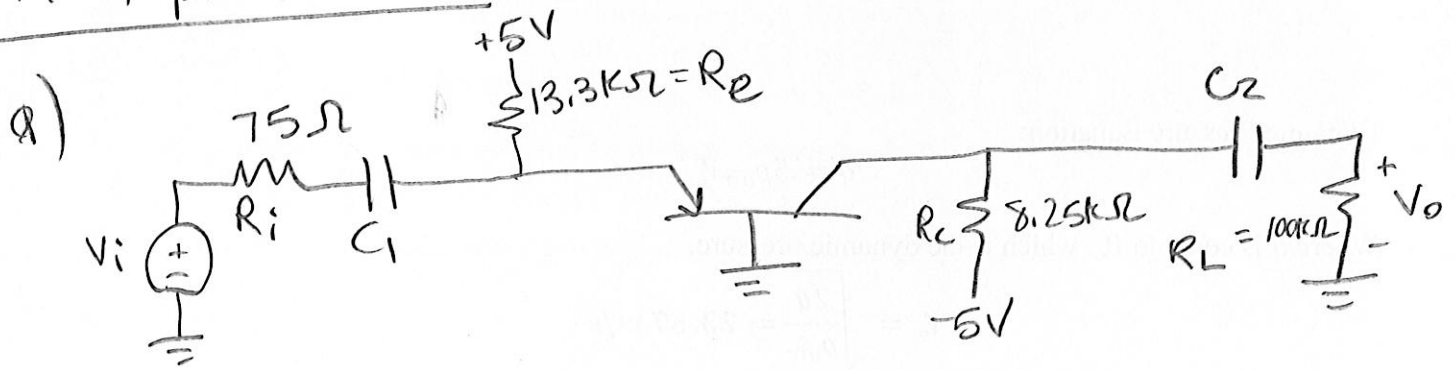

DC analysis

$$I_C \approx I_E \approx \frac{5V - 0.7V}{R_E} = 323 \mu A$$

$$C_1 \gg \frac{1}{\omega (R_i + R_{in})} = \frac{1}{(50000)(2\pi)(75\Omega + 77\Omega)} = 21 \text{ nF}$$

$$R_{in} = R_E \parallel R_{ie} = R_E \parallel \frac{1}{g_m} = 77\Omega$$

$$g_m = \frac{I_C}{V_T} \approx 12.9 \text{ mS}$$

choose $C_1 = 10(21 \text{ nF}) = 220 \text{ nF}$

$$C_2 \gg \frac{1}{\omega (R_{out} + R_L)} = \frac{1}{\omega (R_C + R_L)} = \frac{1}{(50000)(8.25k\Omega + 100k\Omega)(2\pi)} = 29.4 \text{ pF}$$

$$R_{out} = R_C \parallel R_{ic} = R_C \parallel r_o(1 + g_m(R_i \parallel R_E)) = R_C$$

No V_A is given, so assume $V_A = \infty$, $r_o = \infty$.

$$R_{out} = R_C$$

choose $C_2 = 10(29.4 \text{ pF}) \approx 300 \text{ pF}$

14.97

In the example, all capacitor values are chosen so that their cutoff frequency at 100 Hz. This is because they multiplied the capacitance value by 10 after calculating the capacitance values for the 1000 Hz cutoff frequency. Therefore simply

choose $C_3 = 67.2 \text{ nF}$ as calculated in example 14.7 for 1000 Hz, and

$C_1 = 1.8 \text{ nF}$ and $C_2 = 15 \text{ nF}$ as previously chosen for 100 Hz.

$$C_3 = \frac{1}{1000(2\pi)(R_H // (R_E + \frac{1}{g_m}))} = 67.2 \text{ nF}$$

$$C_1 = \frac{1}{100(2\pi)(R_I + R_{in})} = 1.78 \text{ nF} \approx 1.8 \text{ nF}$$

$$C_2 = \frac{1}{100(2\pi)(\frac{21.0}{k\Omega} + R_3)} = 13.1 \text{ nF} \approx 15 \text{ nF}$$

$$R_{out} = R_D // R_{iD} = 22 \text{ k}\Omega // 442 \text{ k}\Omega = 21.0 \text{ k}\Omega$$

For Spice, $K_n = 0.5 \text{ mA/V}^2$, $V_{TN} = 1 \text{ V}$, $\lambda = 0.0133 \text{ V}^{-1}$

Q point: $I_D = 0.24 \text{ mA}$, $V_{DS} = 3.81 \text{ V}$ (from example 14.3 pg. 881)

16.8

$$a) \frac{I_0}{I_{ref}} = \frac{\left(\frac{W}{L}\right)_2 (1 + \lambda V_{DS2})}{\left(\frac{W}{L}\right)_1 (1 + \lambda V_{DS1})}$$

Find $V_{GS1} = V_{DS1}$

$$35 \mu A = \frac{1}{2} K_n' \left(\frac{4}{1}\right) (V_{GS1} - V_{TN})^2$$

$$I_0 = 35 \mu A \quad K_n' = 25 \mu A/V^2 \quad V_{TN} = 0.75V$$

Solve for V_{GS} , $V_{GS1} = 1.59V = V_{DS1}$

$$I_{02} = \frac{10}{4} \frac{(1 + 0.01 \cdot 10V)}{(1 + 0.01 \cdot 1.59V)} (35 \mu A) = 94.7 \mu A$$

$$I_{03} = \frac{20}{4} \frac{(1 + 0.01 \cdot 8V)}{(1 + 0.01 \cdot 1.59V)} (35 \mu A) = 186 \mu A$$

$$I_{04} = \frac{40}{4} \frac{(1 + 0.01 \cdot 12V)}{(1 + 0.01 \cdot 1.59V)} (35 \mu A) = 386 \mu A$$

b) $I_{ref} = 50 \mu A \Rightarrow V_{GS} = 1.75V$

$$I_{02} = 135 \mu A, \quad I_{03} = 265 \mu A, \quad I_{04} = 550 \mu A$$

c) for $35 \mu A = I_{ref}$ in part c) w/ $\lambda = 0$ $50 \mu A$ I_{ref}

$$I_{02} = (35 \mu A) \left(\frac{10}{4}\right) = 87.5 \mu A$$

$$I_{03} = (35 \mu A) \left(\frac{20}{4}\right) = 175 \mu A$$

$$I_{04} = (35 \mu A) \left(\frac{40}{4}\right) = 350 \mu A$$

$$I_{02} = 125 \mu A$$

$$I_{03} = 250 \mu A$$

$$I_{04} = 100 \mu A$$

$$\underline{16.8 \text{ (cm)}}$$

output resistances (small signal)

$$a) \quad r_o = \frac{1 + \lambda V_{DS}}{\lambda I_D}$$

$$r_{o2} = \frac{1 + \lambda(10V)}{\lambda I_{o2}} = 1.16 \text{ M}\Omega$$

$$r_{o3} = \frac{1 + \lambda(8V)}{\lambda I_{o3}} = 580 \text{ k}\Omega$$

$$r_{o4} = \frac{1 + \lambda(12V)}{\lambda I_{o4}} = 290 \text{ k}\Omega$$

$$b) \quad r_{o2} = 814 \text{ k}\Omega, \quad r_{o3} = 407 \text{ k}\Omega, \quad r_{o4} = 204 \text{ k}\Omega$$

$$c) \quad \text{for } \lambda = 0, \quad r_{o1} = r_{o2} = r_{o3} = r_{o4} = \infty \Omega$$

16.12

$$R = 24 \text{ k}\Omega, \quad k_p' = 15 \mu\text{A/V}^2, \quad V_{tp} = -0.90 \text{ V}, \quad \lambda = 0.01 \text{ V}^{-1}$$

$$V_{gs1} = I_{d1} R = 5 \text{ V}$$

$$I_{d1} = \frac{1}{2} (k_p') (2) (V_{gs1} - V_{tp})^2$$

$$\text{Solve, } V_{gs1} = -3.16 \text{ V}, \quad I_{d1} = 76.6 \mu\text{A}$$

$$I_{o2} = \frac{8}{2} \frac{(1 + \lambda(5 \text{ V}))}{(1 + \lambda(3.16 \text{ V}))} (76.6 \mu\text{A}) = \boxed{312 \mu\text{A}}$$

$$r_{o2} = \frac{1 + \lambda(5 \text{ V})}{\lambda \cdot I_{o2}} = \boxed{336 \text{ k}\Omega}$$

should be positive $|V_{DS}|$
for pmos.

$$I_{o3} = \frac{16}{2} \cdot \frac{(1 + \lambda \cdot 10 \text{ V})}{(1 + \lambda \cdot 3.16 \text{ V})} (76.6 \mu\text{A}) = \boxed{654 \mu\text{A}}$$

$$r_{o3} = \frac{1 + \lambda \cdot 10 \text{ V}}{\lambda \cdot I_{o3}} = \boxed{168 \text{ k}\Omega}$$

16.16 part a only

$$R = 68k\Omega \quad \beta_{FO} = 50 \quad V_A = 60V$$

First, find I_{ref} through resistor R .

$$\begin{aligned} I_{ref} &= I_{C1} + I_{B1} + I_{B2} + I_{B3} \\ &= I_{C1} + I_{B1} + 5 I_{B1} + 8.3 I_{B1} \\ I_{ref} &= (13 + 14.3) I_{B1} \end{aligned}$$

$$I_{ref} \approx \frac{12V - 0.7V}{R} \approx 166\mu A.$$

$$I_{O2} = n_2 I_{ref} \frac{1 + \frac{V_{CE2}}{V_A}}{1 + \frac{V_{BE}}{V_A} + \frac{1 + n_2 + n_3}{\beta}} = 5(166\mu A) \frac{1 + \frac{5V}{60V}}{1 + \frac{0.7V}{60V} + \frac{1 + 5 + 8.3}{50}}$$

$$V_{BE} \approx 0.7V \text{ (assumed)}$$

$$n_2 = 5$$

$$n_3 = 8.3$$

$$I_{O2} = 694\mu A$$

$$I_{O3} = n_3 I_{ref} \frac{1 + \frac{V_{CE3}}{V_A}}{1 + \frac{V_{BE}}{V_A} + \frac{1 + n_2 + n_3}{\beta}} = 8.3(166\mu A) \frac{1 + \frac{3V}{60V}}{1 + \frac{0.7V}{60V} + \frac{1 + 5 + 8.3}{50}}$$

$$R_{O2} = \frac{V_A + V_{CE2}}{I_{C2}} = \frac{60V + 5V}{694\mu A} = 93.7k\Omega \quad I_{O3} = 1.12mA$$

$$R_{O3} = \frac{V_A + V_{CE3}}{I_{C3}} = \frac{60V + 3V}{1.12mA} = 56.5k\Omega$$