
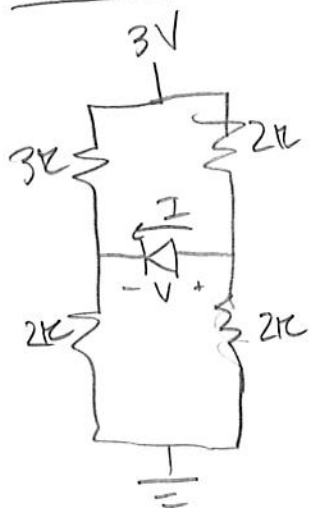


3.69

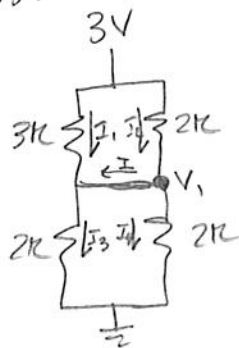

a) Ideal Diode model

Assume Diode on as initial guess



$$I = I_2 - I_4 = I_3 - I_1$$

$$V_1 = 3V \cdot \frac{2/12k\Omega}{3/12 + 2/12}$$

$$V_1 = 3V \cdot \frac{1k\Omega}{\frac{1}{\frac{1}{3k\Omega} + \frac{1}{2k\Omega}} + 1k\Omega}$$

$$V_1 = 3V \cdot \frac{1k\Omega}{\frac{6}{5}k\Omega + 1k\Omega}$$

$$V_1 = 3V \cdot \frac{5}{11}$$

$$I_2 = \frac{3V - 3V \cdot \frac{5}{11}}{2k\Omega} = \frac{3V \cdot (\frac{6}{11})}{2k\Omega} = \frac{9}{11} \text{ mA}$$


$$I_4 = \frac{3V \cdot \frac{5}{11}}{2k\Omega} = \frac{15}{22} \text{ mA}$$

$$I = I_2 - I_4 = (\frac{18}{22} - \frac{15}{22}) \text{ mA} = \frac{3}{22} \text{ mA} = 136 \mu\text{A}$$

$I = 136 \mu\text{A}$ ,  $V = 0V$  is Q-point our initial guess right

b) Constant Voltage Drop model

Assume Diode off.

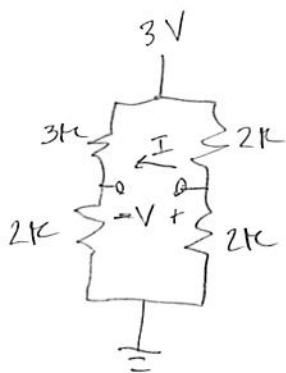

$$V = 3V \cdot \frac{2k\Omega}{2k\Omega + 2k\Omega} - 3V \cdot \frac{2k\Omega}{3k\Omega + 2k\Omega}$$

$$= 3V \left( \frac{1}{2} - \frac{2}{5} \right) V$$

$$= 3 \left( \frac{1}{10} \right) V$$


$$= 0.3 V$$

Because  $V = 0.3V < V_{on} = 0.6V$ , our assumption that the diode is off is right

so  $V = 0.3V$ ,  $I = 0A$  is Q-point

### 3.69 (con)

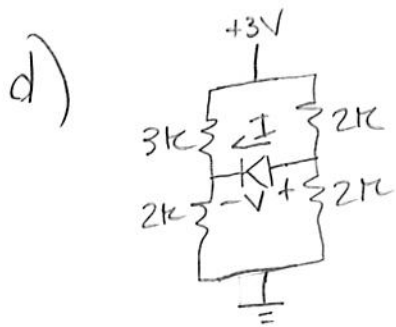
c) The constant voltage drop model should be more correct because the model more closely matches the real I-V characteristic for a diode.



We need to relate the  $I, V$  of diode to the circuit, and then plug that into the following equation for diode:



$$I = I_s \left( \exp\left(\frac{V}{V_T}\right) - 1 \right)$$

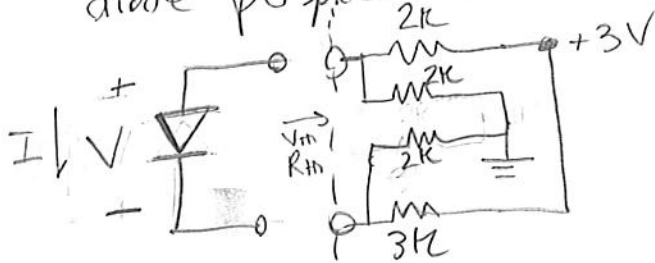To do this, we can find the thevenin equivalent from diode perspective.



Break circuit as shown and find Thevenin equivalent.

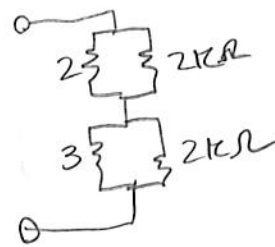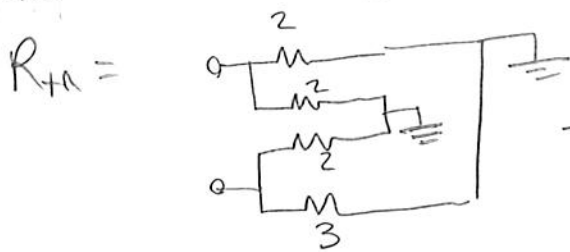
$$V_{oc} = V_{th} = 3V \left( \frac{2k\Omega}{2+2k\Omega} \right) - 3V \left( \frac{2k\Omega}{2k\Omega+3k\Omega} \right) = 0.3V$$



$$R_{th} = 2k\Omega // 2k\Omega + 3k\Omega // 2k\Omega$$

$$R_{th} = 1k\Omega + 1.2k\Omega = 2.2k\Omega$$

So we can rewrite the circuit as...

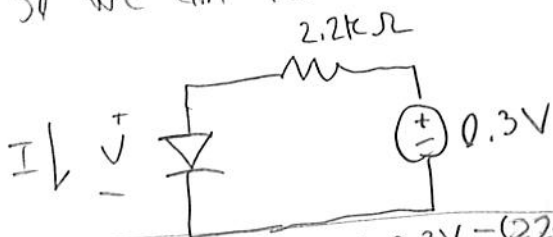

$$\Rightarrow V = 0.3V - (2.2k\Omega)I$$

plug this into Diode equation

$$I = 10^{-15} \left( \exp\left(\frac{0.3V - (2.2k\Omega)I}{0.025V}\right) - 1 \right) A$$

→ Solve by Iteration or by computer →

$$I = 162 \text{ pA}$$

$$V = 0.3V - (2.2k\Omega)I \approx 0.3V$$

3.72

a) Ideal Diode Model

a) Diode is forward Biased, so assume ~~short~~ short circuit.

Therefore  $V = -5V$ .  $I = \frac{+5V - (-5V)}{10k\Omega} = 625\mu A$

b) Diode is forward Biased, so assume short circuit.

Therefore  $V = +3V$ .  $I = \frac{+3V - (-7V)}{10k\Omega} = 625\mu A$

c) Diode reverse biased, assume ~~short circuit~~ open circuit.

Therefore  $V = +7V$ ,  $I = 0A$

d) Diode reverse biased, assume open circuit.

$\Rightarrow V = -5V$ ,  $I = 0A$

$V_{on} = 0.7V$  Model

a) Assume Diode off. ~~Then there~~ then there is  $10V$  across the diode which is ~~greater~~ greater than  $V_{on}$ . This is inconsistent w/ assumption that diode is off, so that must be false. Therefore diode must be on.

$V = -5V + V_{on} = -4.3V$ ,  $I = \frac{+5V - (-4.3V)}{10k\Omega} = 581\mu A$

b) Similar logic to a) indicates diode is again on.

$V = +3V - V_{on} = 2.3V$ ,  $I = \frac{+2.3V - (-7V)}{10k\Omega} = 581\mu A$

c) Assume Diode off. Then there is  $-10V$  across the diode, which is less than  $V_{on} = +0.7V$ . This is consistent with our assumption that the Diode is off, so the diode is indeed off.

$V = +7V$ ,  $I = 0A$

d) Same logic as in c) allows us to conclude that the diode is off. therefore

$V = -5V$ ,  $I = 0A$

3.74

Ideal Diode Model

a)  $D_1$  and  $D_2$  on

$$\textcircled{D} I_2 = \frac{6V}{43k\Omega} = \underline{140\mu A}, \quad \underline{V_2 = 0V}$$

$$I_1 = \textcircled{D} - I_2 + \textcircled{D} \left( \frac{9V}{22k\Omega} \right) = -140\mu A + \frac{9V}{22k\Omega} = \underline{270\mu A}$$

$$\underline{V_1 = 0V}$$

b)  $D_2$  off,  $D_1$  on

$$I_1 = \frac{6V}{43k\Omega} = \underline{140\mu A} \quad \underline{V_1 = 0V}$$

$$\underline{I_2 = 0A}, \quad \underline{V_2 = -9V}$$

c)  ~~$D_1$  off,  $D_2$  on~~

Assume:  $D_1$  off,  $D_2$  on - (we see later this assumption is wrong)

$$\textcircled{D} I_2 = \frac{15V}{22+43k\Omega} = \underline{230\mu A} \quad \underline{V_2 = 0V}$$

$$I_1 = 0A, \quad \textcircled{D} V_1 = (-9V + \left( \frac{22}{43+22} \right) (15V)) \times -1 = +3.9V$$

This is inconsistent w/ our original assumption, so  ~~$D_1$~~   $D_1$  is on, not off.

Assume:  $D_1$  on,  $D_2$  on.

$$I_2 = \frac{9V}{22k\Omega} = \underline{409\mu A} \quad \underline{V_2 = 0V}$$

$$I_1 = I_2 - \frac{6V}{43k\Omega} = \underline{270\mu A}, \quad \underline{V_2 = 0V}$$

} These are consistent w/ our assumption of Both  ~~$D_1$~~  Diodes on, so these should be correct.

3.74 (con)

Ideal Diode Model (con)

d)  $D_1$  off,  $D_2$  on

$$I_2 = \frac{15V}{22+43k\Omega} = \underline{230\mu A} \quad \underline{V_2 = 0V}$$

$$\underline{I_1 = 0A}, \quad V_2 = (-9V + (\frac{22}{43+22})(15V)) = \underline{-3.92V}$$

3.74, Constant  $V_{on}$  Model ( $V_{on} = 0.65V$ )

a)  $I_2 = \frac{V_{on} - V_{on} - (-6V)}{43k\Omega} = \frac{6V}{43k\Omega} = \underline{140\mu A}$   ~~$V_2 = V_{on} = 0.65V$~~

~~$I_1 = \frac{9V - V_{on}}{22k\Omega} - I_2$~~

$$I_1 = \frac{9V - V_{on}}{22k\Omega} - I_2 = \frac{9V - 0.65}{22k\Omega} - 140\mu A = \underline{240\mu A} \quad \underline{V_1 = V_{on} = 0.65V}$$

b)  $D_2$  off,  $D_1$  on

$$I_1 = \frac{6V - V_{on}}{43k\Omega} = \frac{6V - 0.65V}{43k\Omega} = \underline{124\mu A} \quad \underline{V_1 = V_{on} = 0.65V}$$

$$\underline{I_2 = 0A} \quad \underline{V_2 = -9V}$$

c)  $D_1$  on,  $D_2$  on

$$I_2 = \frac{-V_{on} - V_{on} - (-9V)}{22k\Omega} = \frac{-0.65 - 0.65 + 9V}{22k\Omega} = \underline{350\mu A} \quad \underline{V_2 = V_{on} = 0.65V}$$


$$I_1 = I_2 - \frac{6V + V_{on}}{43k\Omega} = \underline{350\mu A} - \frac{6V + 0.65V}{43k\Omega} = \underline{195\mu A} \quad \underline{V_1 = V_{on} = 0.65V}$$

d)  $D_1$  off,  $D_2$  on

$$I_2 = \frac{15V - V_{on}}{43+22k\Omega} = \frac{15V - 0.65V}{43+22k\Omega} = \underline{221\mu A} \quad \underline{V_2 = 0.65V}$$

$$\underline{I_1 = 0A} \quad V_1 = -9V + V_{on} + \frac{22}{43+22}(15V - V_{on}) = \underline{-3.49V}$$

3.81

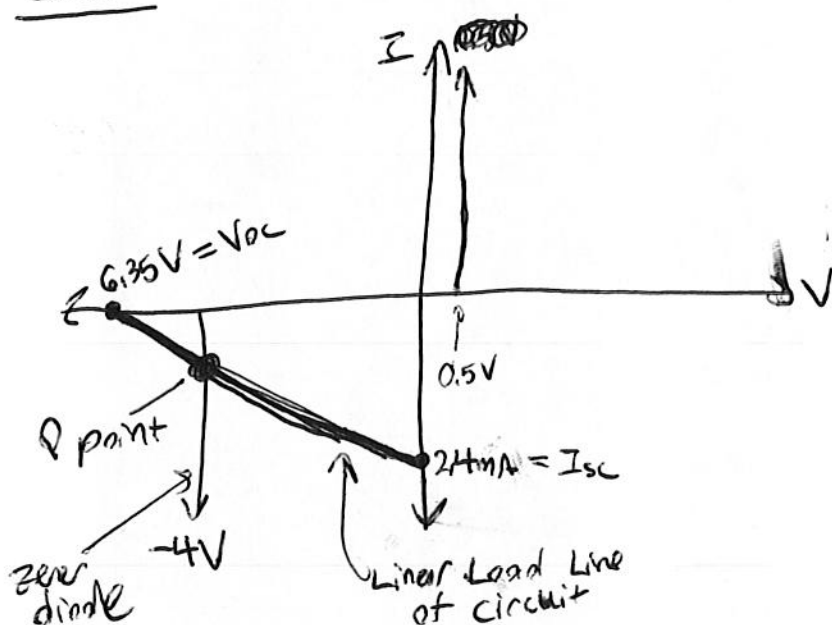


$$V_{oc} = \frac{3.6}{10 + 3.6} 24V = 6.35V$$

$$I_{sc} = \frac{24V}{10k\Omega} = 2.4mA$$

From thevenin and Norton equivalent from the diode perspective

What is Q point?

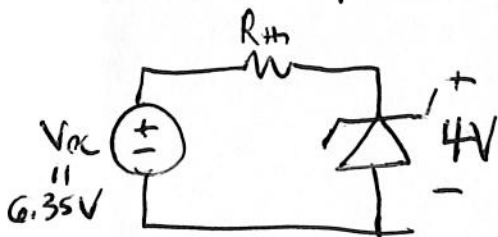


$$R_{th} = 10k\Omega // 3.6k\Omega$$

$$R_{th} = 2.65k\Omega$$

$$V = -4V \text{ from graph}$$

$$I = \frac{V_{oc} + V}{R_{th}} = \frac{6.35V - 4V}{2.65k\Omega} = 889\mu A$$

3.86

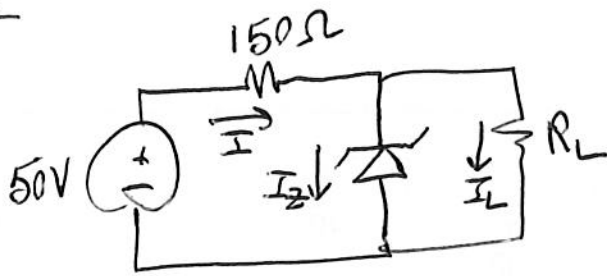

$$I = I_Z + I_L \Rightarrow I_Z = I - I_L = I - \frac{V_Z}{R_L} = \frac{50V - V_Z}{150\Omega} - \frac{V_Z}{R_L} = I_Z$$

$$I_L = \frac{V_Z}{R_L}$$

$$I = \frac{50V - V_Z}{150\Omega}$$

$$I_Z = \frac{50V - V_Z}{150\Omega} - \frac{V_Z}{R_L}$$

~~100~~

a) for  $R_L = 100\Omega$   $I_Z = \frac{50V - 15V}{150} - \frac{15V}{100\Omega} = 83.3\text{mA}$

$$\text{Power} = V_Z I_Z = (15V)(83.3\text{mA}) = \boxed{1.25\text{W}}$$

b) for  $R_L = \infty\Omega$   $I_Z = \frac{50V - 15V}{150\Omega} = 233\text{mA}$

$$\text{Power} = V_Z I_Z = (15V)(233\text{mA}) = \boxed{3.5\text{W}}$$

3.104 - ~~THIS problem statement is ambiguous~~  
 see eqs 3.63 to 3.67

a)  ~~$V_{DC} = V_p - V_{on}$~~

$$V_i = V_p \sin(\omega t)$$

$$-V_{DC} = V_p - V_{on}$$

$$V_{RMS} = 18V, \text{ so } V_p = V_{RMS} \cdot \sqrt{2} = 18V \cdot \sqrt{2} = 25.5V$$

$$-V_{DC} = 25.5V - 1V = \underline{24.5V} \Rightarrow \boxed{V_{DC} = -24.5V} \quad (\text{Note diode direction})$$

b)  $V_r = \frac{(V_p - V_{on})}{R} \cdot \frac{T}{2C} = \frac{24.5V}{0.5\Omega} \cdot \frac{1/60Hz}{2C} = 0.25V$

~~Solve for C~~

Solve for C,  $\boxed{C = 1.63 F}$  is the minimum capacitance

c)  $PIV = 2V_p = 2 \cdot 25.5V = \underline{51V}$

d) With the definition of  $V_i$  as in the problem, the ~~surge current of the peak~~ surge current is the same for the full wave rectifier as the half wave rectifier. Therefore use eq. 3.57.

$$I_{sc} = \omega C V_p = (2\pi)(60Hz)(1.63F)(25.5V) = \underline{15600A}$$

↑  
assume minimum capacitance.

e)  $I_p = I_{DC} \frac{T}{\Delta T}$

$$\Delta T = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_p}} = \frac{1}{2\pi(60Hz)} \sqrt{\frac{2(0.25V)}{25.5V}} = 372 \times 10^{-6} \text{ seconds}$$

$$I_{DC} = \frac{-V_{DC}}{R} = \frac{-24.5V}{0.5\Omega} = -49.0A, \quad I_p = (49.0A) \cdot \frac{1/60Hz}{372 \times 10^{-6} \text{ seconds}} = \underline{2170A}$$