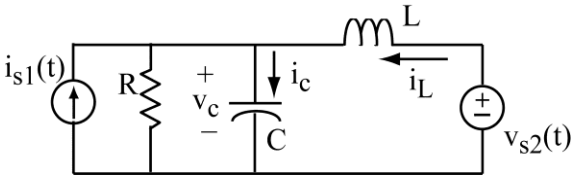
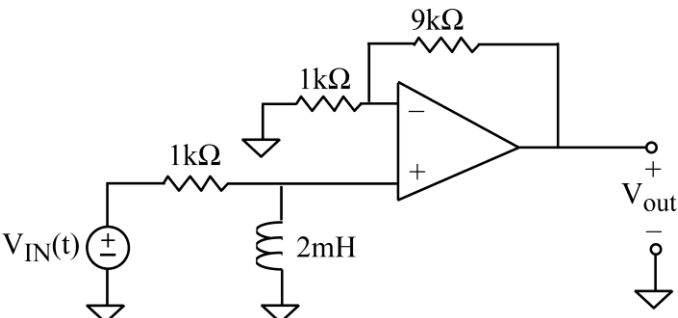
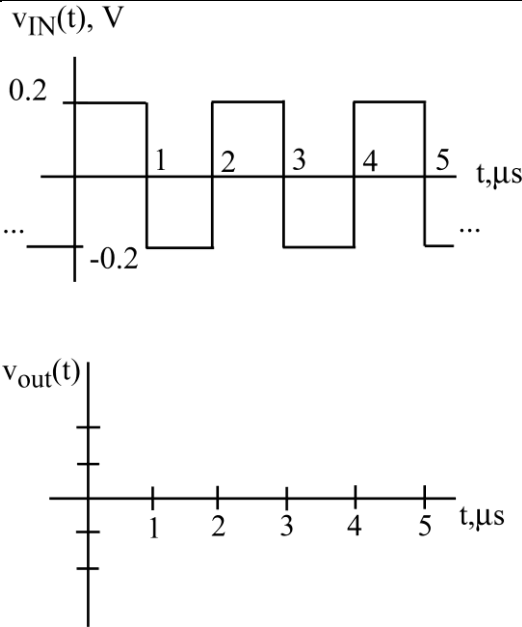


ECE 201
Spring 2013
Homework Sets
(All problems are from the 3rd edition of DeCarlo and Lin)

HW Set #1 Due W 1/9	<ol style="list-style-type: none"> Chapter 1 – prob. 1 (For part e, use Figure P1.1b) Chapter 1 – prob. 7(a) Chapter 1 – prob. 8
HW Set #2 Due F 1/11	<ol style="list-style-type: none"> Chapter 1 – prob. 11 Chapter 1 – prob. 13 Chapter 1 – prob. 17
HW Set #3 Due M 1/14	<ol style="list-style-type: none"> Chapter 1 – prob. 19 (Be careful. Table 1.2 lists <u>relative</u>, not <u>absolute</u>, resistivities!) Chapter 1 – prob. 22(a) Chapter 1 – prob. 27 Chapter 1 – prob. 37
HW Set #4 Due W 1/16	<ol style="list-style-type: none"> Chapter 2 – prob. 3 Chapter 2 – prob. 6 Chapter 2 – prob. 14 (there are 2 typos: <ol style="list-style-type: none"> In 14.(a), “Figure P2.13” should be “Figure P2.14”) In 14.(b) “$I_1 = 4A$” should be “$I_{in} = 4A$” Chapter 2 – prob. 17
HW Set #5 Due F 1/18	<ol style="list-style-type: none"> Chapter 2 – prob. 26 (It is the current <u>out</u> of the positive terminal of the source) Chapter 2 – prob. 32 (a) Chapter 2 – prob. 40
HW Set #6 Due W 1/23	<ol style="list-style-type: none"> Chapter 2 – prob. 39 Chapter 2 – prob. 46 Chapter 2 – prob. 63
HW Set #7 Due F 1/25	<ol style="list-style-type: none"> Chapter 3 – prob. 2 Chapter 3 – prob. 6(a)
HW Set #8 Due M 1/28	<ol style="list-style-type: none"> Chapter 3 – prob. 13 Chapter 3 – prob. 18 Chapter 3 – prob. 26
HW Set #9 Due W 1/30	<ol style="list-style-type: none"> Chapter 3 – prob. 37 Chapter 3 – prob. 42 Chapter 3 – prob. 52

HW Set #10 Due F 2/1	<ol style="list-style-type: none"> Chapter 5 – prob. 1 Chapter 5 – prob. 21(a) Chapter 5 – prob. 26
HW Set #11 Due M 2/4	<ol style="list-style-type: none"> Chapter 5 – prob. 41 Chapter 5 – prob. 43
HW Set #12 Due W 2/6	<ol style="list-style-type: none"> Chapter 6 – prob. 2 Chapter 6 – prob. 5
HW Set #13 Due M 2/11	<ol style="list-style-type: none"> Chapter 6 – prob. 9(a) and (b) Chapter 6 – prob. 17 Chapter 6 – prob. 21 Chapter 6 – prob. 37
HW Set #14 Due W 2/13	<ol style="list-style-type: none"> Chapter 6 – prob. 48 Chapter 6 – prob. 53 <p>In Figure P6.53, change the symbol inside the circle on the left of the circuit to an upward arrow for i_{s1}.</p>
HW Set #15 Due F 2/15	<ol style="list-style-type: none"> Chapter 7 – prob. 2 (Change part (b) to read “Find and plot the instantaneous absorbed power.”) Chapter 7 – prob. 4
HW Set #16 Due M 2/18	<ol style="list-style-type: none"> Chapter 7 – prob. 12 Chapter 7 – prob. 16 Chapter 7 – prob. 17
HW Set #17 Due W 2/20	<ol style="list-style-type: none"> Chapter 7 – prob. 27 Chapter 7 – prob. 38 Chapter 7 – prob. 41
HW Set #18 Due F 2/22	<ol style="list-style-type: none"> Chapter 8 – prob. 4 Chapter 8 – prob. 5 Chapter 8 – prob. 9(b)
HW Set #19 Due M 2/25	<ol style="list-style-type: none"> Chapter 8 – prob. 18 (a) and (b) Chapter 8 – prob. 19 (a) and (b) Chapter 8 – prob. 20 (a) and (b)
HW Set #20 Due W 2/27	<ol style="list-style-type: none"> Chapter 8 – prob. 18 (c) - (e) Chapter 8 – prob. 19 (c) - (e) Chapter 8 – prob. 20 (c) and (d)
HW Set #21 Due F 3/1	<ol style="list-style-type: none"> Chapter 8 – prob. 31 Chapter 8 – prob. 33

HW Set #22 Due M 3/4	<ol style="list-style-type: none"> Chapter 9 – prob. 1 Chapter 9 – prob. 10
HW Set #23 Due W 3/6	<ol style="list-style-type: none"> Chapter 9 – prob. 16(b) Chapter 9 – prob. 18 (use $C = 10\text{mF}$ instead of $C = 8\text{mF}$) Chapter 9 – prob. 20
HW Set #24 Due M 3/18	<ol style="list-style-type: none"> Chapter 9 – prob. 28 Chapter 9 – prob. 32(a) (complete response only)
HW Set #25 Due W 3/20	<ol style="list-style-type: none"> Chapter 9 – prob. 43 Chapter 9 – prob. 49 <p>Please use the following figure in place of Figure P9.49 in the textbook.</p> 
HW Set #26 Due F 3/22	<ol style="list-style-type: none"> Chapter 4 – prob. 3 Chapter 4 – prob. 5
HW Set #27 Due M 3/25	<ol style="list-style-type: none"> Chapter 4 – prob. 7 Chapter 4 – prob. 13
HW Set #28 Due W 3/27	<ol style="list-style-type: none"> Chapter 6 – prob. 29 Chapter 6 – prob. 31 (Change answer to part b to “(b) $3R$”)
HW Set #29 Due F 3/29	<ol style="list-style-type: none"> Chapter 8 – prob. 40(a) The op amps in the following circuit are ideal <p>For $v_{IN}(t)$ as shown in the plot, find and plot $v_{out}(t)$. Label the axis.</p> 

	 <p>The top graph shows the input voltage $v_{IN}(t)$ in Volts versus time t in microseconds. The signal is a square wave alternating between 0.2 V and -0.2 V with a period of 1 μs. The bottom graph shows the output voltage $v_{OUT}(t)$ versus time t in microseconds, with a blank coordinate system for the student to draw the response.</p>
<p>HW Set #30 Due M 4/1</p>	<ol style="list-style-type: none"> 1. Add the complex numbers $z_1 = 10e^{j\pi/4}$ and $z_2 = 5e^{j5\pi/8}$. Express your answer (a) in real and imaginary parts, and (b) as a magnitude and phase. Draw z_1, z_2 and $z_1 + z_2$ on the complex plane. Label the real part, the imaginary part, and magnitude and the phase of $z_1 + z_2$. 2. Multiply the complex numbers $z_1 = 12 - 16j$ and $z_2 = 1 + 0.75j$. Express your answer (a) in real and imaginary parts, and (b) as a magnitude and phase. (c) Compare $z_1 z_2$ to $z_1 z_2$. (d) What is the relationship between the phase of z_1, the phase of z_2, and the phase of $z_1 z_2$? 3. For z_1 and z_2 given in problem 2, determine z_1/z_2. Express your answer (a) in real and imaginary parts, and (b) as a magnitude and phase. (c) Compare z_1 and z_2 to z_1/z_2. (d) What is the relationship between the phase of z_1, the phase of z_2, and the phase of z_1/z_2?

HW Set #31 Due W 4/3	<ol style="list-style-type: none"> 1. Chapter 10 – prob. 7 2. Chapter 10 – prob. 10 3. Chapter 10 – prob. 14
HW Set #32 Due F 4/5	<ol style="list-style-type: none"> 1. Chapter 10 – prob. 21 2. Chapter 10 – prob. 23 3. Chapter 10 – prob. 25
HW Set #33 Due M 4/8	<ol style="list-style-type: none"> 1. Chapter 10 – prob. 30 2. Chapter 10 – prob. 40
HW Set #34 Due W 4/10	<ol style="list-style-type: none"> 1. Chapter 10 – prob. 46 2. Chapter 10 – prob. 54 3. Chapter 10 – prob. 60
HW Set #35 Due M 4/15	<ol style="list-style-type: none"> 1. Chapter 10 – prob. 66 2. Chapter 10 – prob. 68
HW Set #36 Due W 4/17	<ol style="list-style-type: none"> 1. Chapter 11 – prob. 1 2. Chapter 11 – prob. 2
HW Set #37 Due F 4/19	<ol style="list-style-type: none"> 1. Chapter 11 – prob. 5 2. Chapter 11 – prob. 7 3. Chapter 11 – prob. 9 4. Chapter 11 – prob. 10
HW Set #38 Due M 4/22	<ol style="list-style-type: none"> 1. Chapter 11 – prob. 17 2. Chapter 11 – prob. 20
HW Set #39 Due W 4/24	<ol style="list-style-type: none"> 1. Chapter 11 – prob. 22 2. Chapter 11 – prob. 23 3. Chapter 11 – prob. 26 <p>The last sentence before (a) should be: “This constitutes a pf of 0.866 lagging.”</p>
HW Set #40 Due F 4/26	<ol style="list-style-type: none"> 1. Chapter 11 – prob. 30 2. Chapter 11 – prob. 37