

Practice Homework Solution for Module 1

1. Unsigned base conversions (LO 1-1).

(a) $(2C9E)_{16}$ to base 2

$(0010\ 1100\ 1001\ 1110)_2$

(b) $(1101001)_2$ to base 10

$(105)_{10}$

(c) $(1101001)_2$ to base 16

$(69)_{16}$

(d) $(8576)_{10}$ to base 16

$(2180)_{16}$

(e) $(A27F)_{16}$ to base 8

$(121177)_8$

2. Short answer questions over basic electronic components (LO 1-7).

- (a) Write two different
- formulas
- for OHM's LAW:

$$V=IR \quad V/I=R$$

- (b) Describe what a
- resistor
- does:

Limits current flow

- (c) Write two different
- formulas
- for calculating the power dissipation of a
- resistor
- :

$$V^2/R \quad I^2R$$

- (d) Describe what a
- diode
- does.

Restricts direction of current flow (from anode to cathode)

- (e) Describe what affects the
- brightness
- of a light emitting diode (LED):

Forward current

- (f) Describe what a
- capacitor
- does:

Stores charge

- (g) Describe a
- functional difference
- between a MOSFET and a BJT:

MOSFETs are voltage-controlled switches, BJTs are current-controlled

- (h) When a MOSFET is
- off
- , its drain-to-source impedance is on the order of:

$o(1,000,000)$ ohms

- (i) When a MOSFET is
- on
- , its drain-to-source impedance is on the order of:

$o(10)$ ohms

- (j) Describe a
- functional difference
- between an N-channel MOSFET and a P-channel MOSFET:

positive V_{gs} turns N-channel on, negative V_{gs} turns P-channel on

3. Prove DeMorgan's Law (T13) for $n=3$ using perfect induction (LO 1-6).

| X1 | X2 | X3 | $X1 \cdot X2 \cdot X3$ | $(X1 \cdot X2 \cdot X3)$ | $(X1 \cdot X2 \cdot X3)'$ | X1' | X2' | X3' | $X1' + X2' + X3'$ |
|----|----|----|------------------------|--------------------------|---------------------------|-----|-----|-----|-------------------|
| 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 |

4. Prove the dual of the Covering theorem ($T9^D$) using axioms and other theorems (LO 1-3).

$$(T9^D) \quad X \cdot (X + Y) = X$$


$$X \cdot (X + Y) = (X+0) \cdot (X + Y) \quad T1$$

$$= X + (Y \cdot 0) \quad T8^D$$

$$= X + 0 \quad T2^D$$

$$= X \quad T1$$

 5. Determine voltages V_A , V_B , V_C , and V_D if each resistor is 100Ω and the voltage source is 10 volts (LO 1-7).




$$V_A = 10 \times (75/275) = 2.73 \text{ V}$$


$$V_A = V_B + V_C + V_D \text{ where } V_B = V_C = V_D$$

$$V_B = V_C = V_D = 0.91 \text{ V}$$

 6. Using a total of **three** N-channel MOSFETs and **three** P-channel MOSFETs, draw a circuit schematic for a **two-input AND** gate. The gate inputs should be labeled A and B, and the gate output should be labeled F. Be sure to show the power (Vcc) and ground (GND) connections as well (LO 1-10).



 7. Using a total of **three** N-channel MOSFETs and **three** P-channel MOSFETs, draw a circuit schematic for a **three-input NOR** gate. The gate inputs should be labeled A, B and C, and the gate output should be labeled F. Be sure to show the power (V_{CC}) and ground (GND) connections as well (LO 1-12).



8. Given that a (5-volt) CMOS gate's P-channel output pull-up has an "on" resistance of 160Ω and that its N-channel output pull-down has an "on" resistance of 80Ω :

- (a) If the desired V_{OHmin} is 4.4 volts and the desired V_{OLmax} is 0.4 volts, what are the gate's I_{OHmax} and I_{OLmax} ratings? (LO 1-19)

$$I_{OHmax} = -0.6/160 = -3.75 \text{ mA}$$

$$I_{OLmax} = 0.4/80 = 5.0 \text{ mA}$$

- (b) If a DCNM of 1.2 volts is desired for this CMOS gate family, what do its V_{IHmin} and V_{ILmax} specifications need to be, based on the values given in part (a)? (LO 1-14)

$$V_{IHmin} = 4.4 - 1.2 = 3.2 \text{ V}$$

$$V_{ILmax} = 0.4 + 1.2 = 1.6 \text{ V}$$

- (c) If the I_{IH} and I_{IL} specifications for gates in this family are +0.1 mA and -0.1 mA, respectively, what is the practical fan-out for circuits constructed using these gates, based on values calculated in part (a)? (LO 1-20)

$$\text{fanout} = \min(3.75/0.1, 5.0/0.1) = 37.5$$

Practical fan-out = 37 ("floor" of 37.5)


- (d) Show how an LED (with forward voltage $V_{LED} = 1.5 \text{ V}$) should be interfaced to gates in this family to obtain maximum brightness, and calculate the value of the current limiting resistor required along with its power dissipation. (LO 1-21)

Circuit and calculations:

$$V_R = 5 - 1.5 - 0.4 = 3.1 \text{ V}$$

$$I_R = 5 \text{ mA}$$

$$R = 3.1/.005 = 620 \Omega$$

 


Current limiting resistor = 620 Ω

Resistor power dissipation = 15.5 mW

9. Given that the P-channel device in the circuit below has **ON** and **OFF** resistances of **80 Ω** and **2 M Ω** (respectively) and that the N-channel device has **ON** and **OFF** resistances of **60 Ω** and **3 M Ω** (respectively), complete the table listing the **output voltages** obtained for each input combination as well as the **power dissipation** (in *milliwatts*). Show your calculations (LOs 1-10 and 1-11).

| A | B | P-ch | N-ch | Req (N+P) | V _{out} | Power Dissip V_{cc}^2/Req |
|----|----|------|------|--------------------|------------------|--------------------------------|
| 0V | 0V | on | off | 3,000,080 Ω | 4.99987 | 0.008333 mW |
| 0V | 5V | on | on | 140 Ω | 2.14286 | 178.57 mW |
| 5V | 0V | off | off | 5,000,000 Ω | 3.00000 | 0.005 mW |
| 5V | 5V | off | on | 2,000,060 Ω | 0.0001499 | 0.0124996 mW |

 


10. One of your best friends from another major, “Raul”, found some N- and P-channel MOSFETs in your “geek box” and wired them together as shown below. Help Raul figure out what he has created by determining V_{out} for all possible input combinations (for the sake of analysis, assume the **ON** resistance of **each** MOSFET (both P- and N-channel) is **10 Ω** and that its **OFF** resistance is **1 M Ω** (LOs 1-10 and 1-11).


| A | B | V _{out} |
|----|----|------------------|
| 0V | 0V | 4.99995 |
| 0V | 5V | 2.5000 |
| 5V | 0V | 2.5000 |
| 5V | 5V | 0.000049995 |

Describe what Raul has created:

“nothing useful”

 

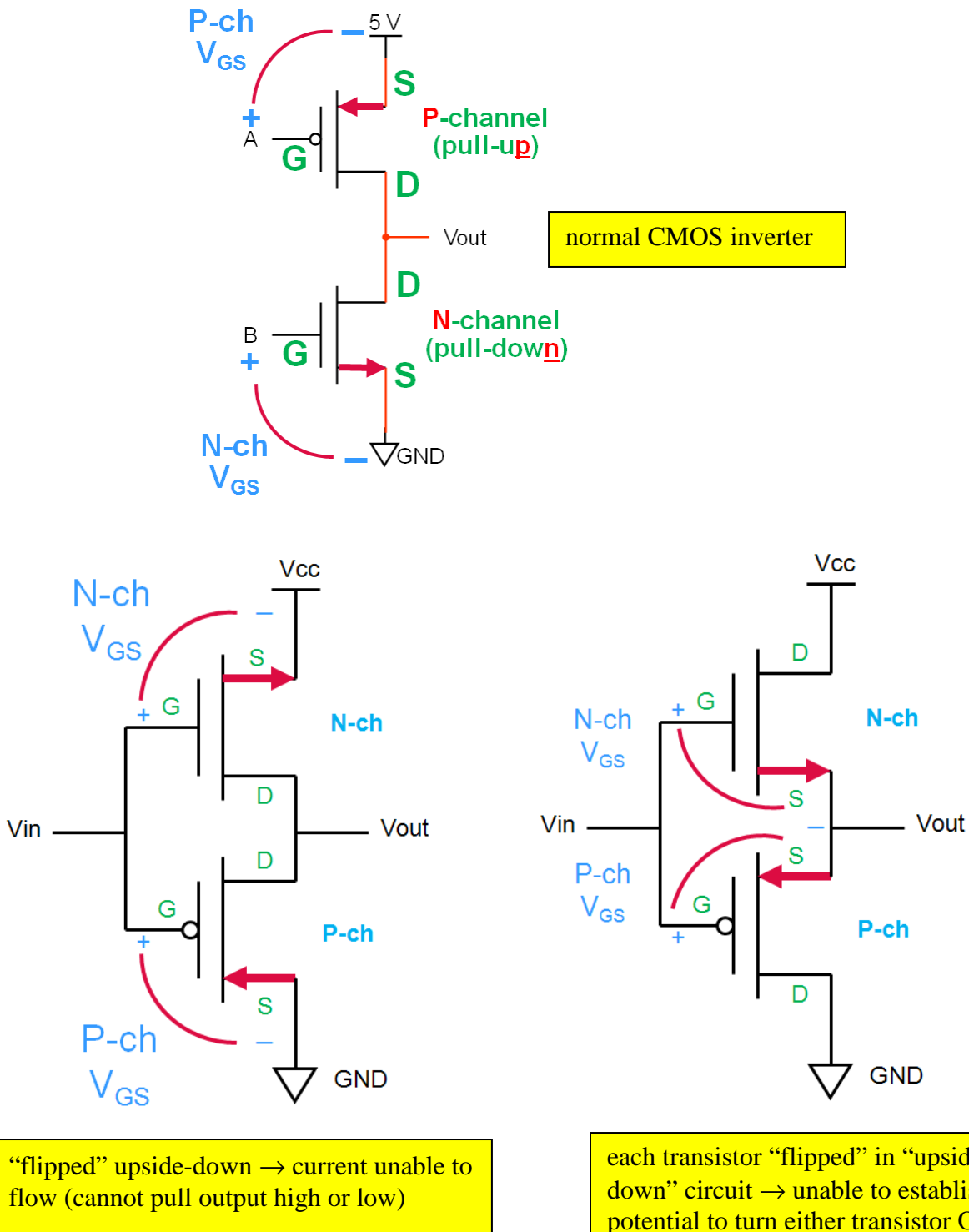11. A common question students have relates to **why** the P-channel device has to serve as a “pull-up” while the N-channel device has to serve as a “pull-down” (i.e., why can’t it be the “other way around”?). To convince yourself of this reality, try drawing a CMOS inverter “upside down” (with an N-channel device used as a pull-up and a P-channel device used as a pull-down) and analyze the circuit you have created (i.e., determine its V_i - V_o characteristics). Describe your conclusion. (LO 1-10)



12. Assume two hypothetical logic families have the following D.C. characteristics:

Logic Family “A”

| | | | | |
|--------------------------------|-------------------------|--------------------------|-----------------------------------|------------------------------------|
| $V_{CC} = 5\text{ V}$ | $V_{OH} = 4.4\text{ V}$ | $V_{OL} = 0.40\text{ V}$ | $V_{IH} = 3.60\text{ V}$ | $V_{IL} = 1.60\text{ V}$ |
| $V_{TH} = (V_{OH} - V_{OL})/2$ | $I_{OH} = -4\text{ mA}$ | $I_{OL} = 4\text{ mA}$ | $I_{IH} = 0.4\text{ }\mu\text{A}$ | $I_{IL} = -0.4\text{ }\mu\text{A}$ |

Logic Family “B”


| | | | | |
|--------------------------------|------------------------------------|--------------------------|----------------------------------|---------------------------|
| $V_{CC} = 5\text{ V}$ | $V_{OH} = 3.3\text{ V}$ | $V_{OL} = 0.30\text{ V}$ | $V_{IH} = 2.60\text{ V}$ | $V_{IL} = 1.60\text{ V}$ |
| $V_{TH} = (V_{OH} - V_{OL})/2$ | $I_{OH} = -400\text{ }\mu\text{A}$ | $I_{OL} = 8\text{ mA}$ | $I_{IH} = 40\text{ }\mu\text{A}$ | $I_{IL} = -0.4\text{ mA}$ |

(a) Calculate the following (*show work*):

- (LO 1-14) $DCNM_{A \rightarrow B} = \min(4.4 - 2.6, 1.6 - 0.4) = 1.2\text{ V}$
- (LO 1-14) $DCNM_{B \rightarrow A} = \min(3.3 - 3.6, 1.6 - 0.3) = -0.3\text{ V}$
- (LO 1-20) Practical Fanout $_{A \rightarrow B} = \min(4/0.04, 4/0.4) = 10$
- (LO 1-20) Practical Fanout $_{B \rightarrow A} = \min(400/0.4, 8/0.0004) = 1000$


(b) Draw the circuit and calculate the **value of the current limiting resistor** for a **Type “A”** gate driving an LED to the maximum brightness possible in a **current sourcing** configuration. Assume V_{LED} is 1.5V. (LO 1-21)

$$R = 2.9/0.004 = 725\text{ }\Omega$$

 


(c) Draw the circuit and calculate the **value of the current limiting resistor** for a **Type “B”** gate driving an LED to the maximum brightness possible in a **current sinking** configuration. Assume V_{LED} is 1.5V. (LO 1-21)

$$R = 3.2/0.008 = 400\text{ }\Omega$$

 


13. A particular CMOS microcontroller is designed to operate over a supply voltage range of **1.0 V** to **5.0 V** and at a maximum clock frequency of **80 MHz** (no minimum clock frequency is specified). The *maximum power dissipation* over this range of supply voltage and clock frequency is specified to be **500 milliwatts**.

 
- (a) Plot the relationship between *power dissipation* and *supply voltage* for this microcontroller (LO 1-29).



 - (b) Plot the relationship between *power dissipation* and *clock frequency* for this microcontroller (LO 1-28).



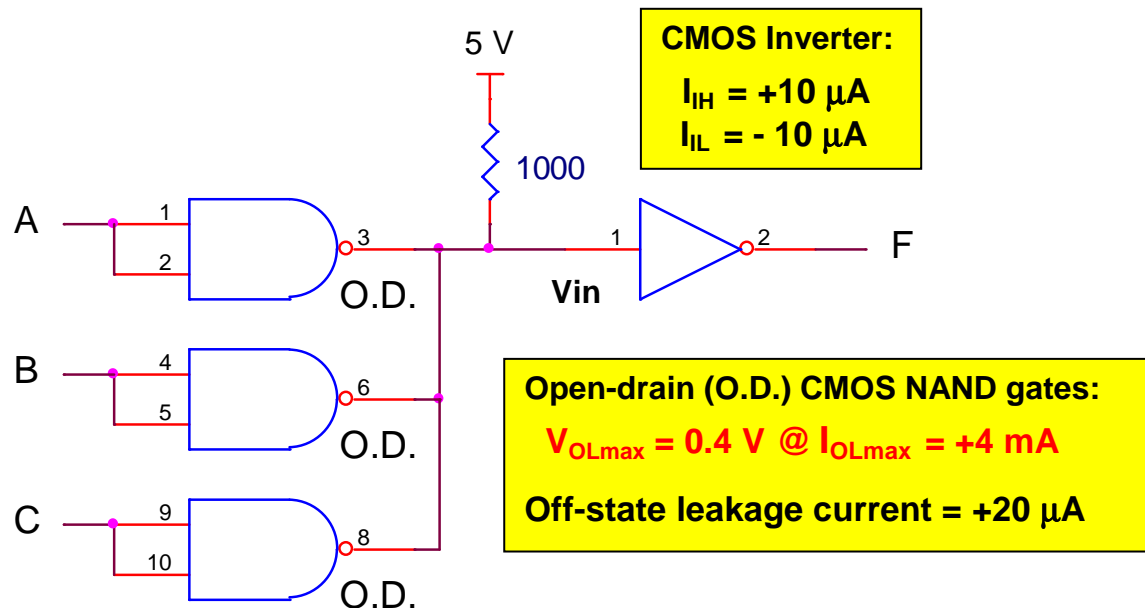14. Given the circuit, below, calculate V_{in} (the CMOS inverter input voltage) for each of the cases indicated along with the current *individually* sunk by each active open drain gate. *Show your calculations.* (LOs 1-34 and 1-35).



Key: ON resistance of each OD gate is $0.4/0.004 = 100 \Omega$

| A | B | C | Ron Total | V_{in} to Inverter | Current Sunk by Each Active O.D. Gate |
|-----|-----|-----|-----------|--------------------------------------|---------------------------------------|
| 0 V | 0 V | 0 V | - | $5 - (0.00007 \times 1000) = 4.93 V$ | (20 μA leakage) |
| 5 V | 0 V | 0 V | 1100 | $5 \times 100 / 1100 = 0.4545 V$ | 4.545 mA |
| 5 V | 5 V | 0 V | 1050 | $5 \times 50 / 1050 = 0.2381 V$ | 2.381 mA |
| 5 V | 5 V | 5 V | 1033 | $5 \times 33 / 1033 = 0.1597 V$ | 1.618 mA |

15. Given the circuit, below, along with its Vi-Vo (input – output voltage) relationship, determine the following (show calculations where applicable):

- (a) estimate the ON resistance of the O.D. NAND gate (LO 1-25)

$$\text{fall time} = 10 \text{ ns} = R_{\text{on}} \times 100 \text{ pF} \rightarrow R_{\text{on}} = 100\Omega$$

- (b) estimate the value of the pull-up resistor (LO 1-36)

$$\text{rise time} = 100 \text{ ns} = R_{\text{pullup}} \times 100 \text{ pF} \rightarrow R_{\text{pullup}} = 1000\Omega$$

- (c) estimate the t_{TLH} of the O.D. NAND gate (LO 1-25)

$$\text{rise time} = 100 \text{ ns}$$

- (d) estimate the t_{THL} of the O.D. NAND gate (LO 1-25)

$$\text{fall time} = 10 \text{ ns}$$

- (e) estimate the t_{PHL} of the O.D. NAND gate (LO 1-23)

$$\text{fall propagation delay} = 10 \text{ ns}$$

- (f) estimate the t_{PLH} of the O.D. NAND gate (LO 1-23)

$$\text{rise propagation delay} = 40 \text{ ns}$$

