

LECTURE 7

- Equivalent circuits of L with initial conditions
- Equivalent circuits of C with initial conditions

Reference: Decarlo/Lin PP 618-625

Equivalent s-domain circuits for 'L' and 'C' with initial conditions

Integration Property of Laplace Transform


$$\mathcal{L} \left[\int_{-\infty}^t f(q) dq \right] = \frac{F(s)}{s} + \frac{\int_{-\infty}^{0^-} f(q) dq}{s}$$

Capacitor

$$v_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(q) dq$$

Laplace Transform
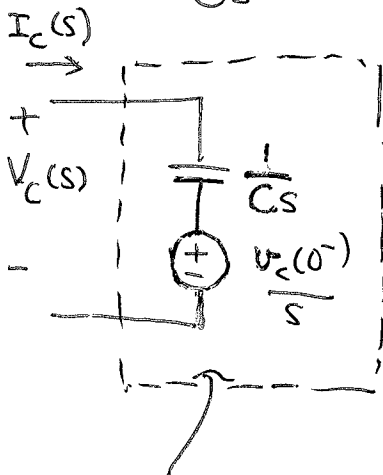
$$V_C(s) = \frac{I_C(s)}{Cs} + \frac{v_c(0^-)}{s}$$




equivalent s-domain circuit for 'C' with initial condition

Inductor

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(q) dq$$

Laplace Transform
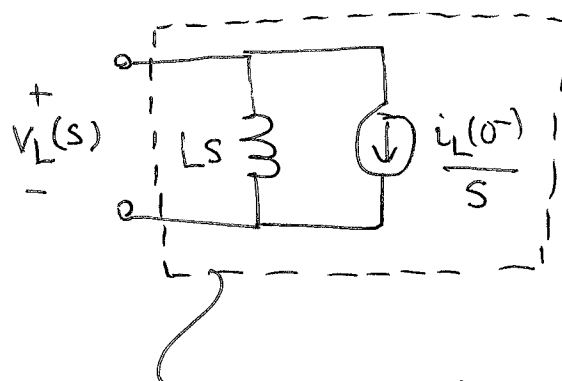
$$I_L(s) = \frac{V_L(s)}{Ls} + \frac{i_L(0^-)}{s}$$




equivalent s-domain circuit for 'L' with initial condition

Differentiation Property of Laplace Transform


$$\mathcal{L} \left[\frac{df}{dt} \right] = sF(s) - f(0^-)$$

Capacitor

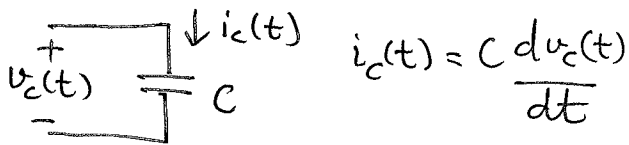


Laplace Transform

$$I_C(s) = Cs V_C(s) - C v_c(0^-)$$

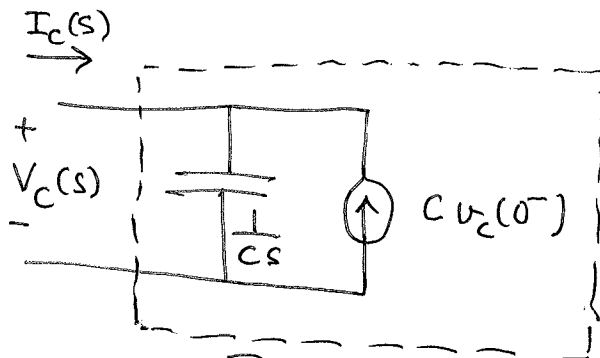


equivalent s-domain
circuit for 'C' with
initial condition

Inductor

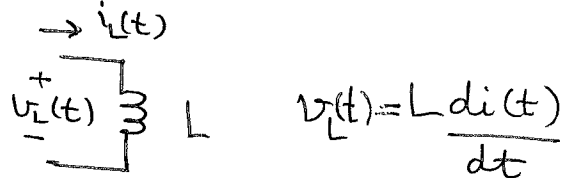


Laplace Transform

$$V_L(s) = Ls I_L(s) - L i_L(0^-)$$

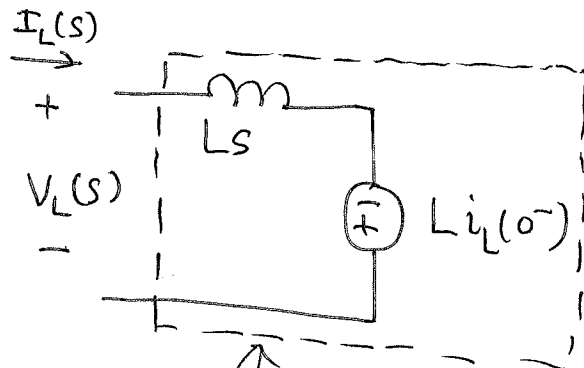


equivalent s-domain
circuit for 'L' with
initial condition

Example 1:

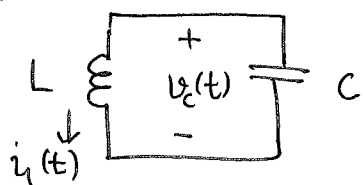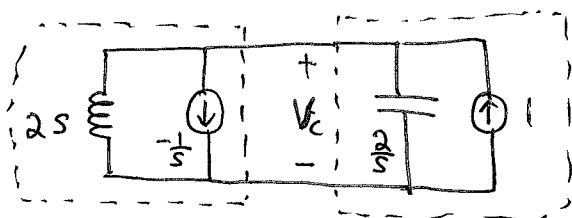

$$L = 2 \text{ H}, \quad C = 0.5 \text{ F}$$

$$i_L(0^-) = -1 \text{ A}, \quad v_C(0^-) = 2 \text{ V}$$

Find $v_C(t)$ for $t > 0$ 


$$2s \parallel \frac{2}{s} = \frac{2s(\frac{2}{s})}{2s + \frac{2}{s}} = \frac{4}{2s^2 + 2}$$

$$Z = \frac{2s}{s^2 + 1}$$

$$V_C = \left(1 + \frac{1}{s}\right) \cdot \frac{2s}{s^2 + 1} = \frac{2(s+1)}{s^2 + 1} = \frac{2s}{s^2 + 1} + \frac{2}{s^2 + 1}$$

$$\therefore v_C(t) = [2 \cos(t) u(t) + 2 \sin(t) u(t)] \text{ V} \leftarrow$$

Alternatively,

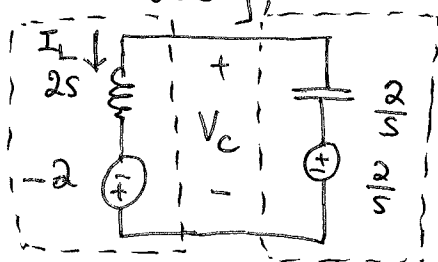

$$V_C = 2s(I_L) - (-2)$$

$$= 2s \left(\frac{\frac{2}{s} - 2}{\frac{2}{s} + 2s} \right) + 2$$

$$= 2s \left(\frac{2 - 2s}{2 + 2s^2} \right) + 2$$

$$= \frac{2s(1-s)}{s^2 + 1} + 2$$


$$= \frac{2s - 2s^2 + 2s^2 + 2}{s^2 + 1}$$

$$= \frac{2s + 2}{s^2 + 1} = \frac{2s}{s^2 + 1} + \frac{2}{s^2 + 1}$$


$$\therefore v_C(t) = [2 \cos(t) u(t) + 2 \sin(t) u(t)] \text{ V} \leftarrow$$

Example 2

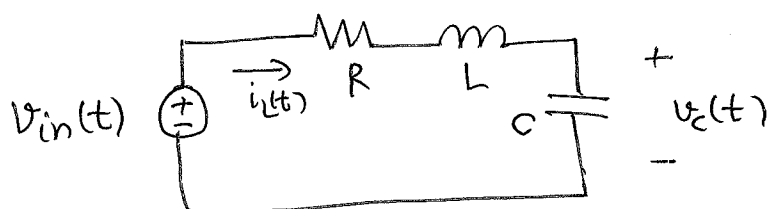(a) Draw s-domain equivalent circuit and solve for $V_C(s)$.




s-domain equivalent circuit

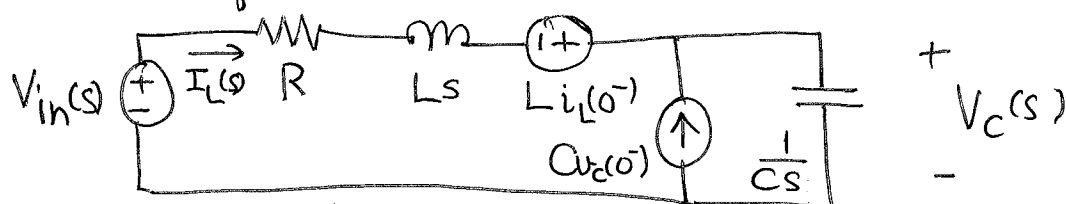

solve for $V_C(s)$ using superposition


(a) Input source:

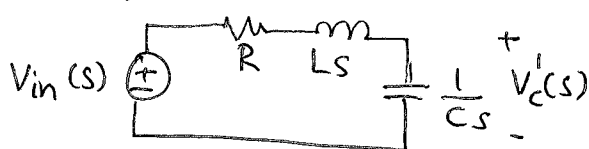

$$V_C^1(s) = \frac{1}{Cs} V_{in}(s)$$

$$V_C^1(s) = \frac{\frac{1}{Cs}}{\frac{1}{Cs} + R + Ls} V_{in}(s)$$


(b) V-source $Li_L(0^-)$:

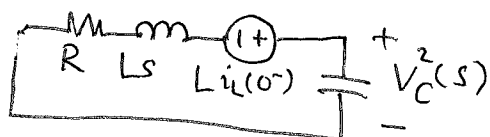

$$V_C^2(s) = \frac{\frac{1}{Cs}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} Li_L(0^-)$$

$$V_C^2(s) = \frac{\frac{1}{Cs}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} i_L(0^-)$$

(c) Current source $Cv_C(0^-)$

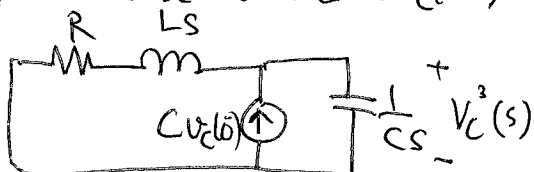

$$V_C^3(s) = \frac{\frac{1}{Cs} \cdot (R + Ls)}{\frac{1}{Cs} + R + Ls} Cv_C(0^-)$$

$$V_C^3(s) = \frac{s + \frac{R}{L}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} v_C(0^-)$$

$$\therefore V_C(s) = V_C^1(s) + V_C^2(s) + V_C^3(s)$$

$$= \frac{\frac{1}{LC} V_{in}(s)}{s^2 + \frac{R}{L}s + \frac{1}{LC}} + \frac{\frac{1}{C} i_L(0^-)}{s^2 + \frac{R}{L}s + \frac{1}{LC}} + \frac{s + \frac{R}{L}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} v_C(0^-)$$

(b) If $R = 2\Omega$, $C = 0.25\text{ F}$, $L = 0.25\text{ H}$, $v_{in}(t) = (1 - e^{-4t})u(t)\text{ V}$
then find $V_C(s)$ and then $v_C(t)$.

$$V_{in}(s) = \frac{1}{s} - \frac{1}{s+4}$$


Plugging into $V_C(s)$, we get

$$V_C(s) = \left[\frac{16}{s(s+4)^2} - \frac{16}{(s+4)^3} \right] + \left[\frac{4 i_L(0^-)}{(s+4)^2} \right] + \left[\frac{s+8}{(s+4)^2} v_C(0^-) \right]$$


$$V_C(s) = \left(\frac{1}{s} - \frac{1}{s+4} - \frac{4}{(s+4)^2} - \frac{16}{(s+4)^3} \right) + \left(\frac{4 i_L(0^-)}{(s+4)^2} \right) + \left[\left(\frac{1}{s+4} + \frac{4}{(s+4)^2} \right) v_C(0^-) \right]$$

$$v_C(t) = (1 - e^{-4t} - 4te^{-4t} - 8t^2e^{-4t})u(t) + 4i_L(0^-)te^{-4t}u(t) + v_C(0^-)(1 + 4t)e^{-4t}u(t) \leftarrow$$

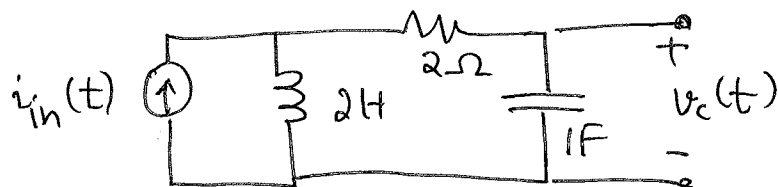Example 3. Find $v_c(t)$ when $v_c(0^-) = 1\text{ V}$, $i_L(0^-) = 1\text{ A}$
and $i_{in}(t) = 2u(t)\text{ A}$



s-domain equivalent circuit

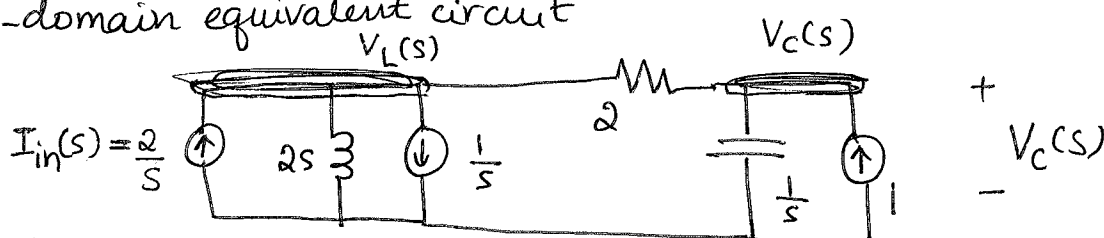

Writing down node equations at $V_L(s)$ and $V_C(s)$

At $V_L(s)$ node: $\frac{2}{s} - \frac{1}{s} - \frac{V_L(s)}{2s} - \frac{V_L(s) - V_C(s)}{2} = 0$

$$V_L(s) \left(\frac{1}{2s} + \frac{1}{2} \right) - \frac{V_C(s)}{2} = \frac{1}{s}$$

At $V_C(s)$ node: $\frac{V_C(s) - V_L(s)}{2} + \frac{V_C(s)}{1/s} - 1 = 0$

$$-\frac{1}{2} V_L(s) + \left(s + \frac{1}{2} \right) V_C(s) = 1$$

Putting into matrix form,

$$\begin{bmatrix} \frac{1}{2s} + \frac{1}{2} & -\frac{1}{2} \\ -\frac{1}{2} & s + \frac{1}{2} \end{bmatrix} \begin{bmatrix} V_L \\ V_C \end{bmatrix} = \begin{bmatrix} \frac{1}{s} \\ 1 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} V_L \\ V_C \end{bmatrix} = \begin{bmatrix} \frac{1}{2s} + \frac{1}{2} & -\frac{1}{2} \\ -\frac{1}{2} & s + \frac{1}{2} \end{bmatrix}^{-1} \begin{bmatrix} \frac{1}{s} \\ 1 \end{bmatrix} = \frac{2s}{s^2 + s + 0.5} \begin{bmatrix} s + 0.5 & 0.5 \\ 0.5 & \frac{s+1}{2s} \end{bmatrix} \begin{bmatrix} \frac{1}{s} \\ 1 \end{bmatrix}$$

$$\therefore V_L = \frac{3s+1}{s^2+s+0.5} \quad \text{and} \quad V_C = \frac{s+2}{s^2+s+0.5} = \frac{s+2}{(s+0.5)^2 + (0.5)^2}$$

By MATLAB,

$$v_c(t) = e^{-0.5t} [\cos(0.5t) u(t) + 3 \sin(0.5t) u(t)]$$