

Aung Kyi San
Summer 2012

ECE 20200 : Linear Circuit Analysis II
School of ECE, Purdue University

LECTURE 10


- Switching in linear circuits

Reference : Decarlo/ Lin


PP 640-645

Switching in RLC circuits

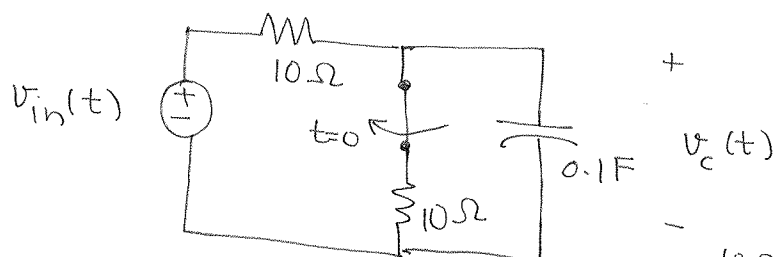
Example 1. Find $v_c(t)$ for $t \geq 0$ when $v_{in}(t) = -20u(-t) + 20u(t)$ V



1) $v_c(0^-) = -10V$

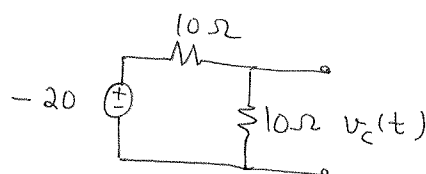

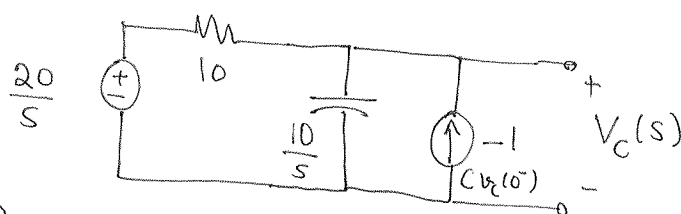2) Draw equivalent s-domain circuit for $t \geq 0$



3) By superposition,

$$V_{cV} = \frac{10/s}{10/s + 10} \cdot \frac{20}{s} = \frac{200/s}{10 + 10s} = \frac{20}{s(s+1)}$$


$$V_{cI} = \frac{10 \cdot \frac{10}{s}}{\frac{10}{s} + 10} \cdot (-1) = \frac{-100/s}{\frac{10}{s} + 10} = \frac{-10}{s+1}$$

$$\therefore V_c(s) = V_{cV} + V_{cI} = \frac{20}{s(s+1)} - \frac{10}{s+1} = \frac{20}{s} - \frac{20}{s+1} - \frac{10}{s+1}$$

$$V_c(s) = \frac{20}{s} - \frac{30}{s+1}$$

$$\therefore v_c(t) = 20u(t) - 30e^{-t}u(t) \text{ V}$$

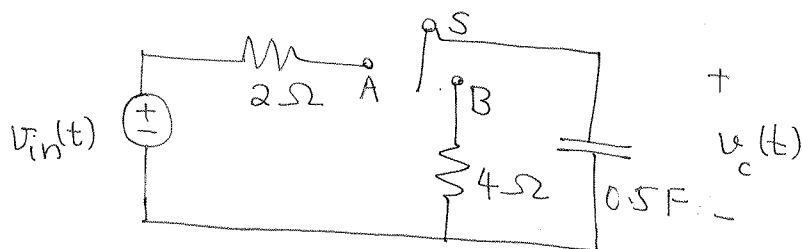Example 2. $v_{in}(t) = 10u(t) + 10u(t-3)V$



Switch 'S' is initially in position A. Switch moves to position B at $t=2s$ and back to A at $t=4s$.

Find $v_c(t)$ for all t .

$$t < 0 \Rightarrow v_c(t) = 0 \quad v_c(0^-) = 0$$

$0 \leq t < 2s \Rightarrow$ Draw equivalent s-domain circuit. Find $V_c(s)$ and $v_c(t)$




$$V_c(s) = \frac{\frac{2}{s}}{2 + \frac{2}{s}} \cdot \frac{10}{s} = \frac{20/s}{(2s+2)} = \frac{10}{s(s+1)} = \frac{10}{s} - \frac{10}{s+1}$$

$$v_c(t) = 10u(t) - 10e^{-t}u(t) \quad 0 \leq t < 2$$

$2 \leq t < 4s \Rightarrow$ Draw equivalent s-domain circuit. Find $V_c(s)$ and $v_c(t)$.


$$v_c(2^-) = 10 - 10e^{-2} = 8.65 V$$

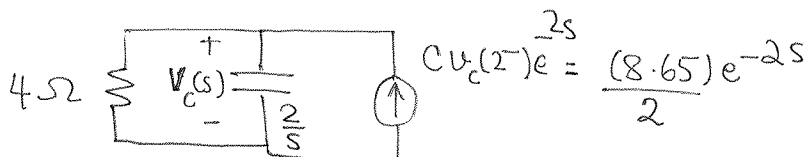

$$V_c(s) = \frac{\frac{2}{s} \cdot 4}{\frac{2}{s} + 4} \cdot \left(\frac{8.65}{2}\right)e^{-2s} = \frac{2}{s+0.5} \left(\frac{8.65}{2}\right)e^{-2s} = \frac{8.65}{s+0.5} e^{-2s}$$

$$v_c(t) = 8.65 e^{-0.5(t-2)} u(t-2), \quad 2 \leq t < 4$$

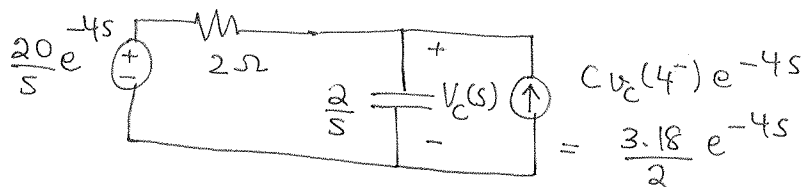$t \geq 4 \Rightarrow$ Draw equivalent s-domain circuit. Find $V_c(s)$ and $v_c(t)$. $v_c(4^-) = 3.18 \text{ V}$




Use superposition,

$$\begin{aligned} V_c(s) &= \frac{20}{s} e^{-4s} \cdot \frac{2/s}{2/s + 2} + \frac{2(\frac{2}{s})}{2 + 2/s} \cdot \frac{3.18}{2} e^{-4s} \\ &= \frac{20 e^{-4s}}{s(s+1)} + \frac{2}{s+1} \cdot \frac{3.18}{2} e^{-4s} \end{aligned}$$

$$v_c(t) = 20(1 - e^{-(t-4)}) u(t-4) + 3.18 e^{-(t-4)} u(t-4) \quad t \geq 4$$

Remark: The voltage across capacitor is continuous, so each segment matches at the switching instant.

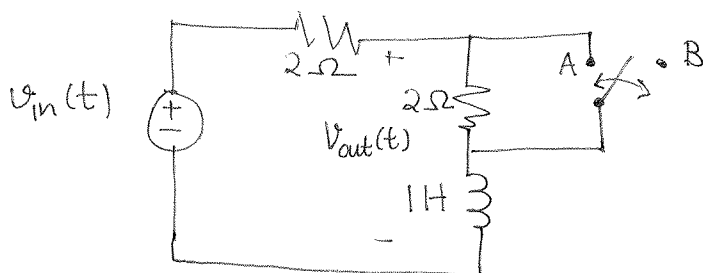
Example 3. RL circuit. Let $v_{in}(t) = 4u(-t) + 8u(t) + 8u(t-2) \text{ V}$. Initially switch is in position B; moves to A at $t=0 \text{ s}$ and back to B at $t=4 \text{ s}$. Find $v_{out}(t)$ for $t \geq 0$



$t < 0$ Inductor short

$$\therefore i_L(0^-) = \frac{4}{2+2} = 1 \text{ A}$$

$0 \leq t < 4 \text{ s}$

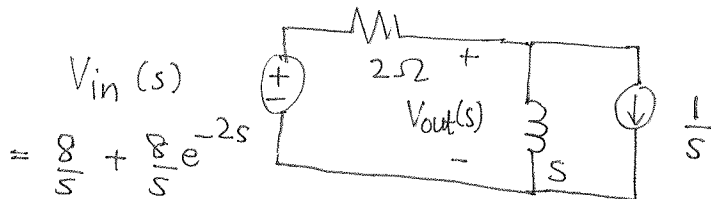

By superposition,

$$V_{out}(s) = \frac{s}{s+2} V_{in}(s) - \frac{2s}{2+s} \cdot \frac{1}{s}$$

$$= \frac{s}{s+2} \left(\frac{8}{s} + \frac{8}{s} e^{-2s} \right) - \frac{2}{s+2}$$


$$= \frac{8}{s+2} + \frac{8}{s+2} e^{-2s} - \frac{2}{s+2}$$

$$= \frac{6}{s+2} + \frac{8}{s+2} e^{-2s}$$

$$v_{out}(t) = 6 e^{-2t} u(t) + 8 e^{-2(t-2)} u(t-2)$$

$0 \leq t < 4 \text{ s}$

$t \geq 4 \text{ s}$


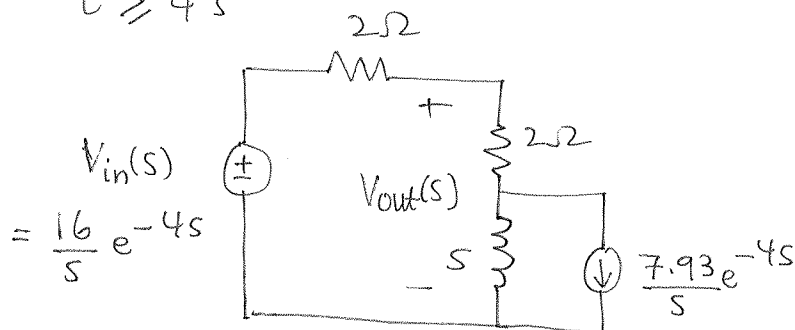


$$i_L(4^-) = ?$$

$$\begin{aligned} i_L(4^-) &= \frac{v_{in}(4^-) - v_{out}(4^-)}{2} \\ &= \frac{15.85}{2} \\ &= 7.93 \text{ A} \end{aligned}$$

By superposition,
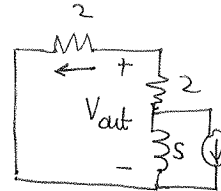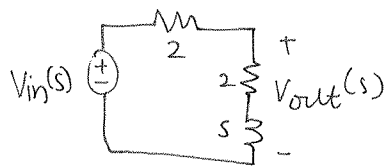
$$V_{out}(s) = \frac{s+2}{s+2+2} V_{in}(s) + \left(\frac{s}{s+4} \right) \left(-\frac{7.93}{s} e^{-4s} \right)$$




$$= \frac{s+2}{s+4} \frac{16}{s} e^{-4s} + \frac{-7.93}{s+4} e^{-4s}$$

$$= \left(\frac{8}{s} + \frac{8}{s+4} \right) e^{-4s} - \frac{7.93}{s+4} e^{-4s}$$

$$V_{out}(t) = 8(1 + e^{-4(t-4)}) u(t-4) - 7.93 e^{-(t-4)} u(t-4) \text{ V}$$

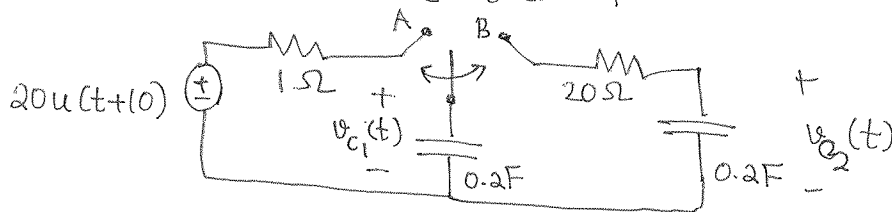Example 4. The switch is in position A for a long time.


At $t=0$, the switch moves to position B and at $t=2s$, the switch moves back to position A and remains there forever.



(a) $V_{C1}(0) = ?$ $V_{C2}(0) = ?$

Since $R_1 C_1 = 0.2$, the charging time constant for C_1 is much less than $10s$, the capacitor C_1 is fully charged to $20V$. $\therefore V_{C1}(0) = 20V$, $V_{C2}(0) = 0V$.

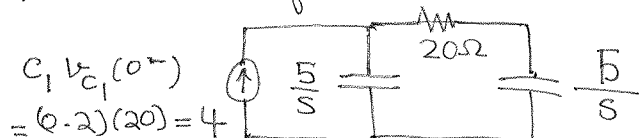(b) Draw equivalent s-domain circuit for $0 \leq t < 2s$




(c) Compute $v_{C_1}(t)$ for $0 \leq t \leq 2$ s.

$$\begin{aligned}
 V_{C_1}(s) &= 4 \cdot \frac{1}{\frac{s}{5} + \frac{1}{20 + \frac{5}{s}}} = \frac{4}{\frac{s}{5} + \frac{s}{20s+5}} \\
 &= \frac{4}{\frac{s}{5} + \frac{s}{20(s+0.25)}} \\
 &= \frac{4}{\frac{4s(s+0.25) + s}{20(s+0.25)}} \\
 &= \frac{80(s+0.25)}{s(4s+1+1)} \\
 &= 20 \frac{80(s+0.25)}{4s(s+0.5)} \\
 &= \frac{20(s+0.25)}{s(s+0.5)} \\
 &= \frac{10}{s} + \frac{10}{s+0.5}
 \end{aligned}$$

$0 \leq t < 2$ s

$$\therefore v_{C_1}(t) = 10(1 + e^{-0.5t})u(t)$$

$$(d) v_{C_1}(2) \approx 10(1 + e^{-0.5(2)}) = 13.4 \text{ V}$$

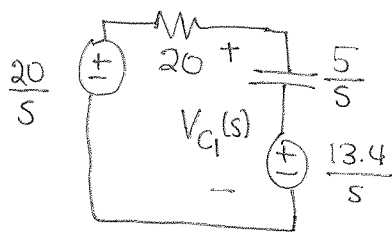(e) Compute $v_{C_1}(t)$ for $t \geq 2 \rightarrow t' = (t-2)$ 

Superposition:

$$\begin{aligned}
 V_{C_1}(s) &= \frac{5}{20 + \frac{5}{s}} \cdot \frac{20}{s} + \frac{20}{20 + \frac{5}{s}} \cdot \frac{13.4}{s} \\
 &= \frac{20}{s} - \frac{20}{s+5} + \frac{13.4}{s+5}
 \end{aligned}$$

$$\therefore v_{C_1}(t') = 20 - 6.6e^{-5t'}u(t') \text{ V}, \quad t' \geq 0$$

$$(or) v_{C_1}(t) = 20 - 6.6e^{-5(t-2)}u(t-2) \text{ V} \quad t \geq 2$$