

14.16

a) when $g_m R_E \gg 1$, we can approximate the common emitter gain as

$$A \approx \frac{-R_L}{R_E} = \frac{-8.2k\Omega // 47k\Omega}{390\Omega + 620\Omega} \approx -6.91 \frac{V}{V}$$

b)

$$A \approx \frac{-R_L}{R_E} = \frac{-8.2k\Omega // 47k\Omega}{620\Omega} = -11.3$$

Place a bypass capacitor in parallel with the 390Ω resistor.

$$c) A \approx \frac{-R_L}{R_E} = \frac{-8.2k\Omega // 47k\Omega}{390} = -17.9 \frac{V}{V}$$

Place a bypass capacitor in parallel w/ the 620Ω resistor (or from the node between the 390Ω and 620Ω resistors to ground).

d) Maximum gain is achieved when $R_E = 0\Omega$. Therefore place the bypass capacitor from the emitter node to AC ground.

$$e) A \approx -10 V_{CC} = -10(24V) = -240 \frac{V}{V}$$

14.28

$R_{in} = R_G$ for common drain amplifier


$$R_{in} = 2\text{M}\Omega.$$

$$R_{out} = R_{is} = \frac{1}{g_m} = \frac{1}{8\text{mS}} = 125\Omega$$

$$\begin{aligned} A_v &= \left(\frac{g_m R_L}{1 + g_m R_L} \right) \left(\frac{R_G}{R_I + R_G} \right) = \left(\frac{(2\text{k}\Omega)(8\text{mS})}{1 + (2\text{k}\Omega)(8\text{mS})} \right) \left(\frac{2\text{M}\Omega}{100\text{k}\Omega + 2\text{M}\Omega} \right) \\ &= \left(\frac{16}{17} \right) \left(\frac{2}{2.1} \right) \\ &= 0.896 \frac{\text{V}}{\text{V}} \end{aligned}$$

$$A_i = \frac{i_o}{i_i} = \frac{V_o / R_L}{V_i / (R_I + R_G)} = A_v \left(\frac{R_I + R_G}{R_L} \right) = (0.896) (1050) = 941 \frac{\text{A}}{\text{A}}$$

14.32

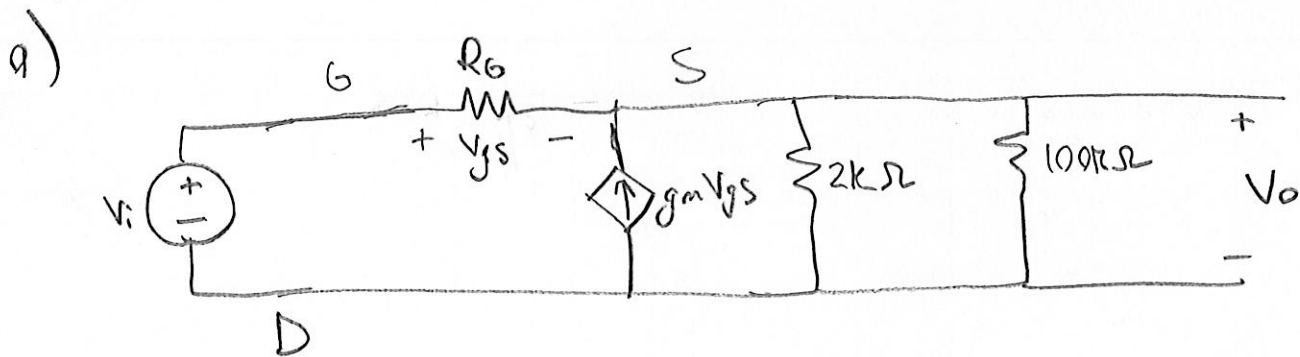

$$A_v = \frac{V_o}{V_i}$$

Node eq. at source:

$$\frac{V_o - V_i}{R_g} - g_m V_{gs} + V_o / 2k\Omega + V_o / 100k\Omega = 0$$

$$\frac{V_o - V_i}{R_g} - g_m (V_i - V_o) + V_o / 2k\Omega + V_o / 100k\Omega = 0$$

$$\frac{V_o}{100k\Omega} + \frac{V_o}{2k\Omega} + \frac{V_o}{R_g} + g_m V_o = \frac{V_i}{R_g} + g_m V_i$$


$$A_v = \frac{V_o}{V_i} = \frac{100k\Omega // 2k\Omega // R_g // 1/g_m}{R_g // 1/g_m} = \boxed{0.874 \frac{V}{V}}$$

$$R_{in} = \frac{V_i}{i_i} = \frac{V_i - V_o}{R_g} = \frac{V_i - A_v V_i}{R_g} \Rightarrow R_{in} = \frac{R_g}{1 - A_v}$$

$$R_{in} = \frac{R_g}{1 - A_v} = \frac{1M\Omega}{1 - 0.874} = \boxed{7.94M\Omega}$$

14.32 (continued)

R_{out}

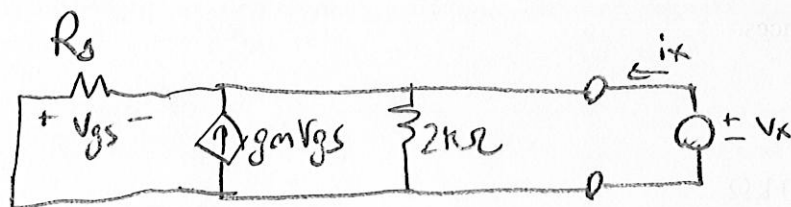

$$-i_x + -g_m V_{gs} + V_x / 2\text{ k}\Omega + \frac{V_x}{R_g} = 0$$

$$-i_x = -g_m(-V_x) + \frac{V_x}{2\text{ k}\Omega} + \frac{V_x}{R_g}$$


$$R_{out} = \frac{V_x}{i_x} = \frac{1}{g_m} \parallel 2\text{ k}\Omega \parallel R_g = \boxed{247\ \Omega}$$

b) If $A_v = 1\frac{V}{V}$,

$$R_{in} = \frac{R_g}{1 - A_v} = \frac{R_g}{0} = \infty\ \Omega$$

$$\boxed{R_{in} = \infty\ \Omega \text{ as } A_v \rightarrow 1\frac{V}{V}}$$

14.81

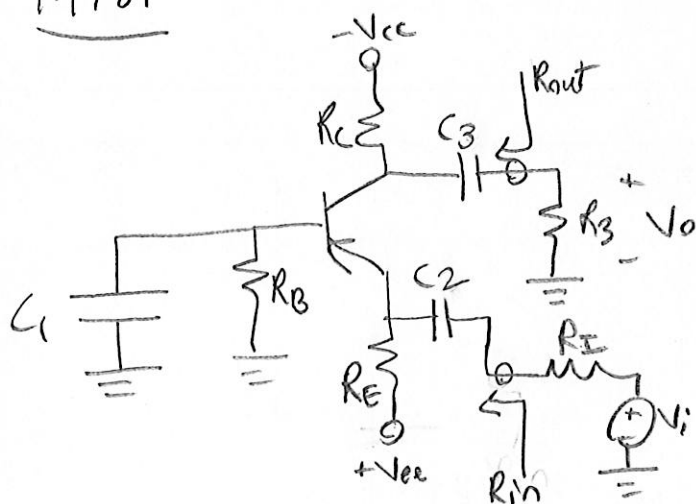

$$\begin{aligned} R_I &= 500\Omega \\ R_B &= 100k\Omega \\ R_3 &= 100k\Omega \\ R_E &= 82k\Omega \\ R_C &= 39k\Omega \\ V_{EE} &= V_{CC} = 12V \\ \beta_F &= 50 \\ V_A &= 50V \end{aligned}$$

$$\begin{aligned} C_1 &= 4.7\mu F \\ C_2 &= 4\mu F \\ C_3 &= 10\mu F \\ f &= 12kHz \end{aligned}$$

Common base amplifier

DC Q point (Assume $V_{eb} = 0.7V$ as in previous chapters)

$$V_{ee} - I_E R_E - V_{eb} - I_B R_B = 0$$

$$V_{ee} - (\beta + 1) I_B R_E - V_{eb} - I_B R_B = 0$$

$$I_B = \frac{V_{ee} - V_{eb}}{(\beta + 1) R_E + R_B} = \frac{12V - 0.7V}{(51)(82k\Omega) + 100k\Omega} = 2.64\mu A$$

$$I_C = \beta I_B = (50)(I_B) = 132\mu A$$

$$r_o = \frac{V_A - V_{CE}}{I_C} = \frac{50 - I_C R_C - I_E R_E}{I_C} = 256k\Omega$$

$$g_m = \frac{I_C}{V_T} = \frac{132\mu A}{0.025V} = 5.28mS$$

14.81

$$\begin{aligned} A_v &= \frac{g_m R_L}{1 + g_m R_{in}} \left(\frac{R_o}{R_I + R_o} \right) \\ &= \frac{g_m (R_3 // R_c)}{1 + g_m (R_I // R_E)} \left(\frac{R_E}{R_I + R_E} \right) \\ &= \frac{(5.28 \text{ mS})(100 \text{ k}\Omega // 39 \text{ k}\Omega)}{1 + (5.28 \text{ mS})(500 \Omega // 82 \text{ k}\Omega)} \left(\frac{82 \text{ k}\Omega}{500 \Omega + 82 \text{ k}\Omega} \right) \end{aligned}$$

$$A_v = 40.6 \frac{\text{V}}{\text{V}}$$

$$R_{in} = R_E // R_{ie} = R_E // \frac{1}{g_m} = 189 \Omega = R_{in}$$

$$\begin{aligned} R_{out} &= R_c // R_{ic} = R_c // r_o(1 + g_m R_{in}) \\ &= R_c // r_o(1 + g_m (R_I // R_E)) \\ &= R_c // 929 \text{ k}\Omega \end{aligned}$$

$$R_{out} = 37.4 \text{ k}\Omega$$

Spice Results:

$$R_{out} = \frac{V_x}{i_x} = \frac{1 \text{ mV}}{26.3 \text{ nA}} = 38.0 \text{ k}\Omega$$

$$A_v = \frac{39.0 \text{ mV}}{1 \text{ mV}} = 39.0 \frac{\text{V}}{\text{V}}$$

$$R_I + R_{in} = \frac{1 \text{ mV}}{-1.42 \mu\text{A}} = 704 \Omega$$

$$R_{in} = 704 \Omega - R_I = 704 \Omega - 500 \Omega = 204 \Omega = R_{in}$$

14.118

3rd Stage DC Analysis

$$V_g = \frac{R_{C3}}{R_5 + R_{C3}} (15V) = 8.53V$$

$$V_{gs3} = V_g - I_{D3} R_{E3} = 8.53V - I_{D3} (3.0k\Omega)$$

$$I_{D3} = (1mA/V^2) \left(\frac{1}{2}\right) (V_{gs3} - V_t)^2$$

$$= (1mA/V^2) \left(\frac{1}{2}\right) (V_{gs3} - 1V)^2$$

Solve for I_{D3} , $I_{D3} = \underline{1.87mA}$

$$V_{gs} = 2.93V$$

2nd Stage DC Analysis

$$\frac{15V - 0.7V - (\beta + 1) I_{B2} R_{E2}}{R_3} = \frac{0.7V + (\beta + 1) I_{B2} R_{E2}}{R_4} + I_{B2}$$

Solve for I_{B2} , $I_{B2} = 12.7\mu A$, $I_{C2} = \beta I_{B2} = \underline{1.27mA}$

1st Stage DC Analysis

$$\frac{15V - 0.7V - (\beta + 1) I_{B1} R_{E1}}{R_1} = \frac{0.7V + (\beta + 1) I_{B1} R_{E1}}{R_2} + I_{B1}$$

Solve for $I_{B1} = 3.20\mu A$, $I_{C1} = \beta I_{B1} = \underline{319\mu A}$

14.118

3rd Stage

Common Drain Amplifier

$$A_{v3} = \frac{V_o}{V_3} = \frac{g_{m3} R'_{L3}}{1 + g_{m3} R'_{L3}} \left(\frac{R_{G3}}{R_G + R_{G3}} \right) = \frac{g_{m3} R'_{L3}}{1 + g_{m3} R'_{L3}} = 0.308 \frac{V}{V}$$

$$R_{I3} = 0 \Omega$$

$$R_{G3} = R_5 // R_6 = 518 k\Omega$$

$$R'_{L3} = R_L // R_{e3} = 231 \Omega$$

$$g_{m3} = \frac{2I_{D3}}{V_{GS} - V_T} = \frac{2(1.87 \text{ mA})}{2.93 \text{ V} - 1 \text{ V}} = 1.93 \text{ mS}$$

$$R_{in3} = R_5 // R_6 = 518 k\Omega$$

2nd Stage

Common Emitter

$$A_{v2} = \frac{V_3}{V_2} = \frac{-g_{m2} R'_{L2}}{1 + g_{m2} R_{E2}} = -2.88 \frac{V}{V}$$

$$R'_{L2} = R_{in3} // R_{C2} = 4.66 k\Omega$$

$$g_{m2} = \frac{I_C}{V_T} = \frac{1.27 \text{ mA}}{0.025 \text{ V}} = 50.7 \text{ mS}$$

$$R_{in2} = R_3 // R_4 // R_{ib} = R_3 // R_4 // r_{\pi 2} (1 + g_{m2} R_{E2}) = 28.0 k\Omega$$

$$r_{\pi 2} = \frac{\beta_0}{g_{m2}} = \frac{100}{50.7 \text{ mS}} = 1.97 k\Omega$$

1st Stage common emitter

$$A_{v1} = \frac{V_1}{V_2} = \frac{-g_{m1} R'_{L1}}{1 + g_{m1} R_{E1}} = -5.27 \frac{V}{V}$$

$$R'_{L1} = R_{in2} // R_{C1} = 11.0 k\Omega$$

$$g_{m1} = \frac{I_C}{V_T} = \frac{319 \mu\text{A}}{0.025 \text{ V}} = 12.8 \text{ mS}$$

$$r_{\pi 1} = \frac{\beta_0}{g_{m1}} = \frac{100}{12.8 \text{ mS}} = 7.82 k\Omega$$

$$R_{in1} = R_1 // R_2 // R_{ib1} = R_1 // R_2 // r_{\pi 1} (1 + g_{m1} R_{E1}) = 62.4 k\Omega$$

$$\frac{14.118}{\frac{V_1}{V_S}} = \frac{R_{in1}}{10k\Omega + R_{in1}} = 0.861 \frac{V}{V}$$

$$A_V = \frac{V_1}{V_S} \cdot \frac{V_2}{V_1} \cdot \frac{V_3}{V_2} \cdot \frac{V_0}{V_3} = 4.03 \frac{V}{V}$$

Input Signal range

1st stage

$$V_{1max} \leq 0.005(1 + g_{m1} R_{E1}) = 133 \text{ mV}$$

$$V_{2max} \leq 0.005(1 + g_{m2} R_{E2}) = 411 \text{ mV}$$

$$V_{3max} \leq 0.2(V_{GS3} - V_{TN})(1 + g_{m3} R'_{L3}) = 559 \text{ mV}$$

$$V_S \leq \left(\frac{V_S}{V_1}\right) \cdot V_{1max} = 154 \text{ mV for stage 1}$$

$$V_S \leq \left(\frac{V_S}{V_1}\right) \left|\frac{V_1}{V_2}\right| V_{2max} = 90.3 \text{ mV for stage 2}$$

$$V_S \leq \left(\frac{V_S}{V_1}\right) \left|\frac{V_1}{V_2}\right| \left|\frac{V_2}{V_3}\right| V_{3max} = 42.7 \text{ mV for stage 3}$$

So the input signal range for V_S is 42.7 mV

The input signal range is enhanced by a factor of 460 at the expense of gain, which decreases by a factor of about 250. The order of magnitude difference between R_{S1} and R_{E1} should be the key contributor to the change in performance. $A_V \propto \frac{1}{R_E}$ signal range $\propto R_E$