

# Today

---

- Ammeters, Voltmeters, Ohmmeters, Oh my!
- Solving for  $Q(t)$  and  $I(t)$  in an RC circuit
- The "time constant" of an RC circuit is  $RC$

# Ammeters, Voltmeters and Ohmmeters

**Ammeter:** measures current  $I$

**Voltmeter:** measures voltage difference  $\Delta V$

**Ohmmeter:** measures resistance  $R$


# Ammeter Design: $r_{\text{int}}$

Ammeter is inserted in series into a circuit – measured current flows through it.



Process of measuring requires charges to do some work:

Internal resistance

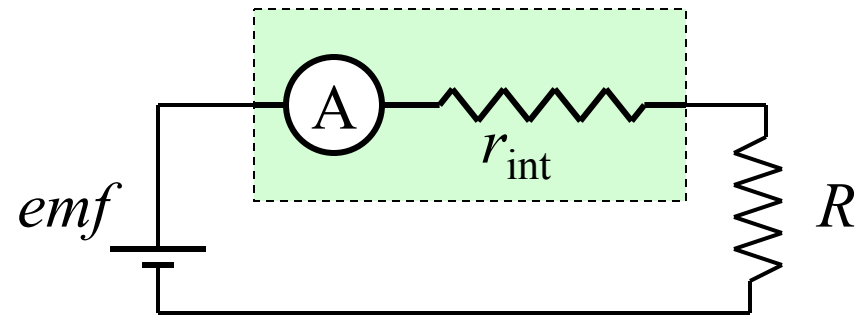


No ammeter:  $emf - RI = 0 \longrightarrow I = \frac{emf}{R}$

With ammeter:  $emf - r_{\text{int}}I - RI = 0 \longrightarrow I = \frac{emf}{R + r_{\text{int}}}$

Internal resistance of an ammeter must be very small

# Voltmeter


Voltmeters measure potential difference

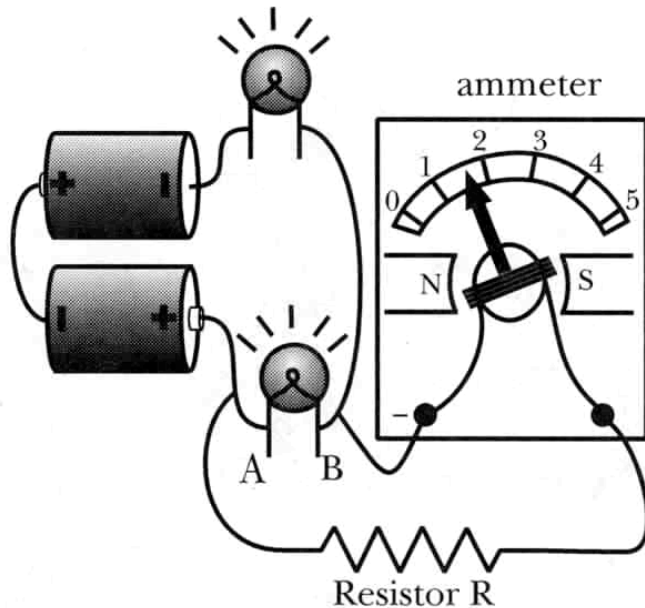

$\Delta V_{AB}$  – add a series resistor to ammeter

$$I = \frac{\Delta V}{R}$$

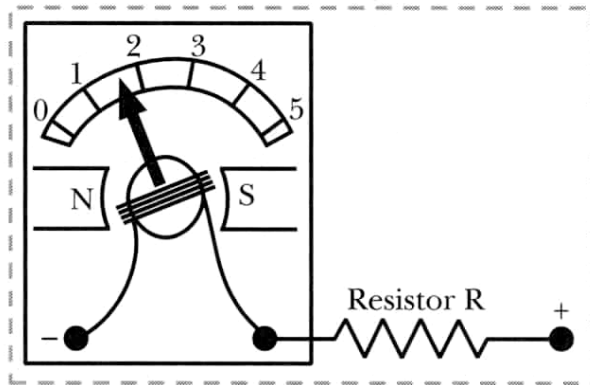
Measure  $I$  and convert to  $\Delta V_{AB} = IR$



Connecting Voltmeter:

Higher potential must be connected to the '+' socket and lower one to the '-' socket to result in positive reading.

# Voltmeter: Internal Resistance

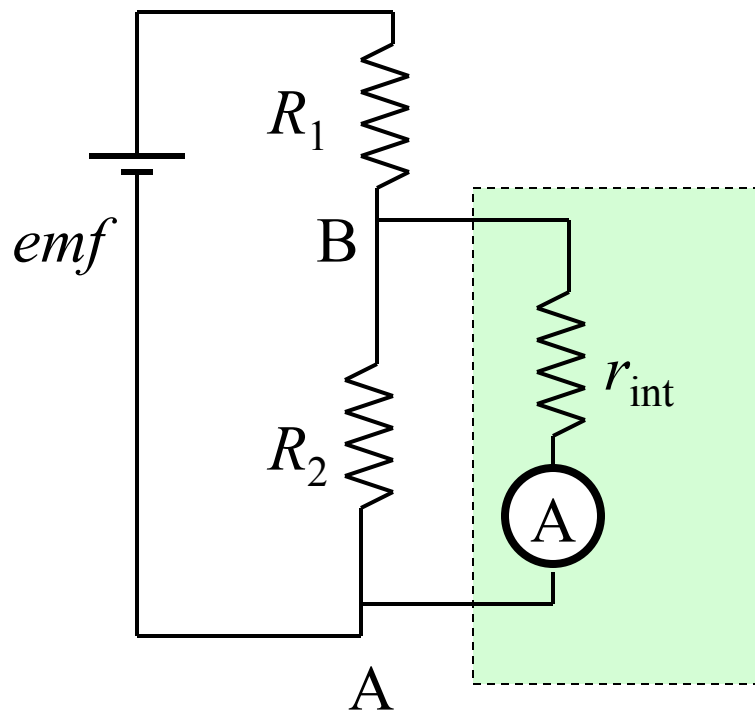

$\Delta V_{AB}$  in absence of a voltmeter

$$\Delta V_{AB} = \frac{R_2}{R_1 + R_2} emf$$

$\Delta V_{AB}$  in presence of a voltmeter


$$\Delta V_{AB} = \frac{R_{2||\text{int}}}{R_1 + R_{2||\text{int}}} emf$$

$$R_{2||\text{int}} = \frac{R_2 r_{\text{int}}}{R_2 + r_{\text{int}}}$$

Internal resistance of a voltmeter must be very large

# Ohmmeter

How would you measure R?

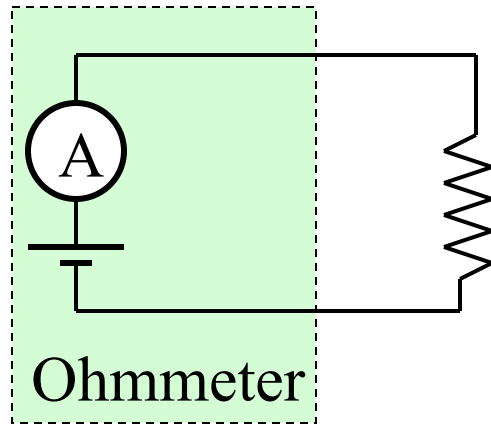

$$R = \frac{emf}{I}$$


$$I = \frac{emf}{R}$$

Ammeter with a small voltage source

# GOAL: Find $Q(t)$ , $I(t)$ in RC circuit

$$Q = CV$$

---

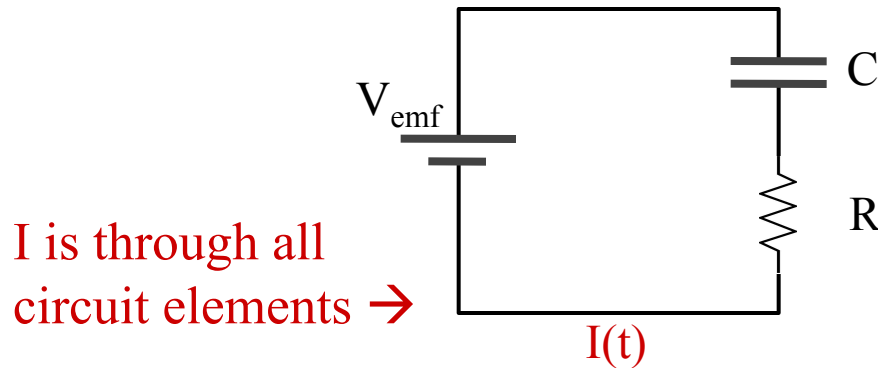


$\leftarrow Q$  is at the capacitor

First: What do we expect?

*Note: we use  $V_{emf}$  Book calls it "emf".*

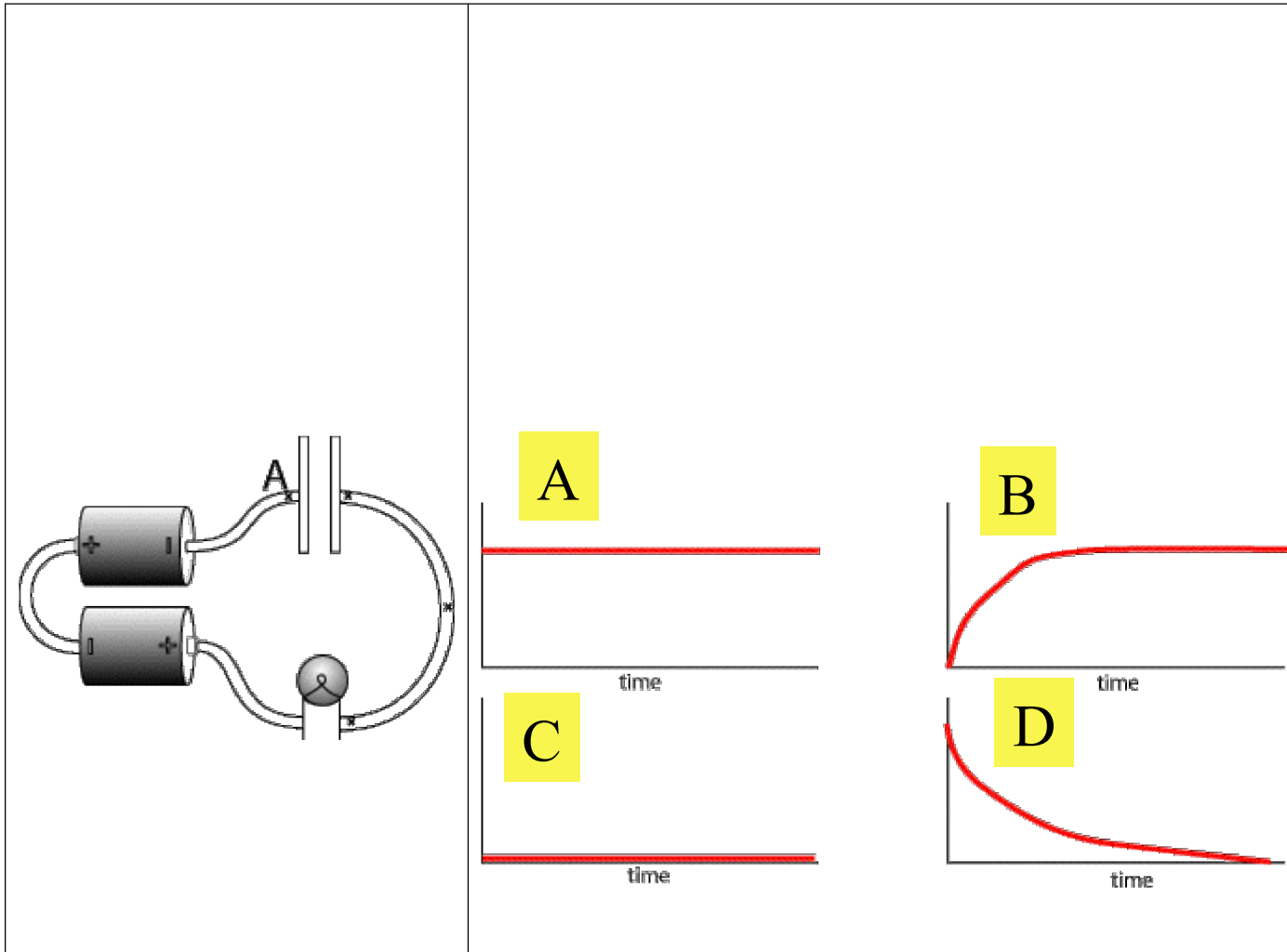
Capacitor initially uncharged. Which graph shows the magnitude of the POTENTIAL DIFFERENCE across the LIGHT BULB FILAMENT while CHARGING?





# GOAL: Find $Q(t)$ , $I(t)$ in RC circuit

$$Q = CV$$

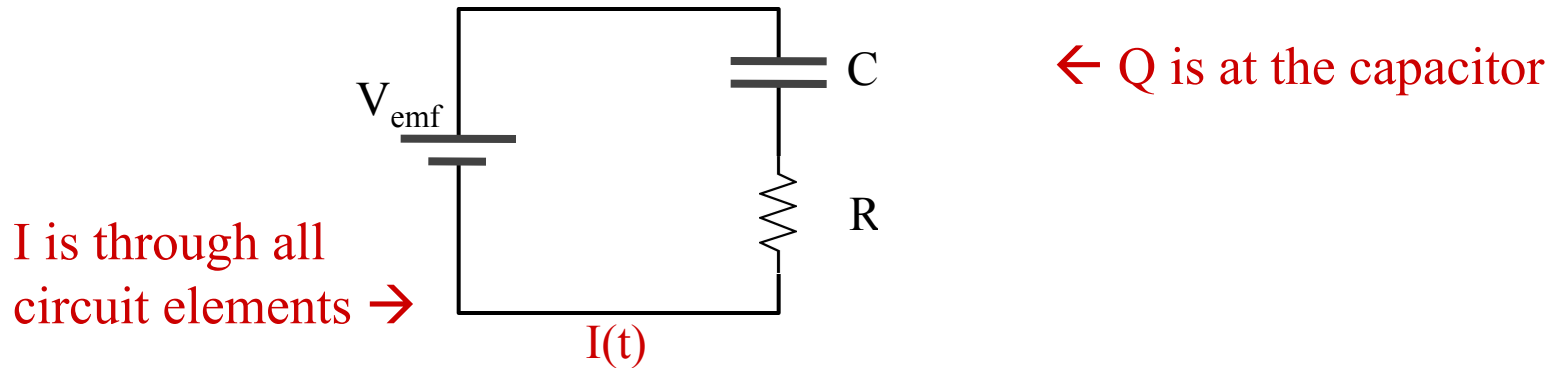

## First: What do we expect?

Just after we connect the circuit:

$$Q = 0$$

$$V_{\text{emf}} = I R$$

A long time after we connect it:


$$Q = C V_{\text{emf}}$$

$$I = 0$$

# GOAL: Find $Q(t)$ , $I(t)$ in RC circuit

$$Q = CV$$

---

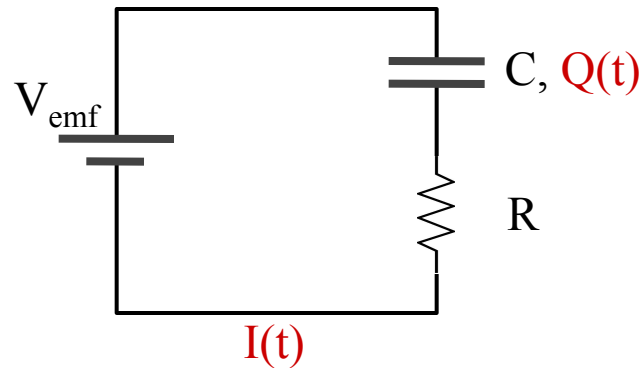


There's one more concept we need:

$$I = \frac{dQ}{dt}$$

Let's see how...

# How are $Q(t)$ and $I(t)$ related?

$$Q = CV$$

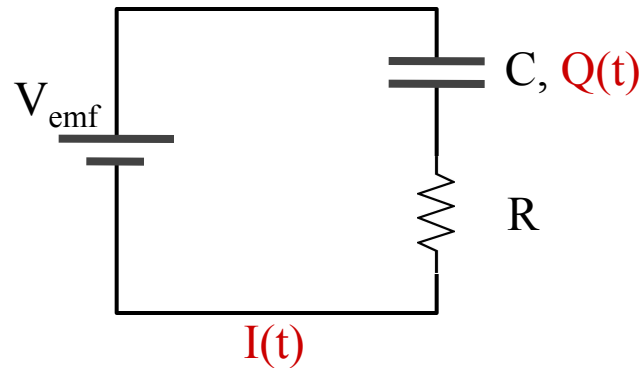

*In English:* Current  $I = |q| \text{ n A v}$  is:  
How much charge ( $\Delta Q$ ) passes by per unit time ( $\Delta t$ ).

*In Math:* 
$$I = \frac{\Delta Q}{\Delta t} \quad \lim_{\Delta t \rightarrow 0} \Rightarrow I = \frac{dQ}{dt}$$

Charge  $\Delta Q$  per time  $\Delta t$  moves throughout the circuit,  
but it **piles up** at  $C$ .


This is the same  $Q$  that is gathering on the capacitor.

# GOAL: Find $Q(t)$ , $I(t)$ in RC circuit

$$Q = CV$$

$$I = \frac{dQ}{dt}$$

$$V = IR$$

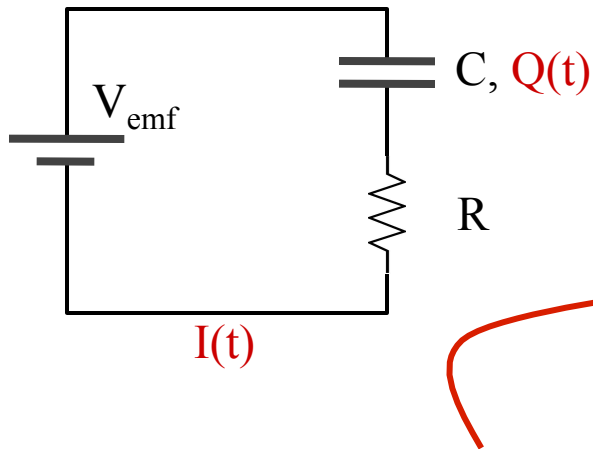

$$V_{\text{emf}} = \frac{Q}{C} + IR$$

Apply Voltage Loop Rule

$$V_{\text{emf}} = \frac{Q}{C} + \frac{dQ}{dt}R$$

Use  $I = \frac{dQ}{dt}$

Solve this Differential Equation for  $Q(t)$ .

TIP: How do you "solve" a differential equation? By already knowing the answer!

We have:

$$\frac{dQ(t)}{dt} = \frac{V_{\text{emf}}}{R} - \frac{1}{RC}Q(t)$$

And the solution is:

$$Q(t) = Ae^{-t/RC} + \text{constant}$$


*to be determined*

# GOAL: Find $Q(t)$ , $I(t)$ in RC circuit

$$Q = CV \quad I = \frac{dQ}{dt} \quad V = IR$$

$$Q(t) = Ae^{-t/RC} + \text{constant}$$
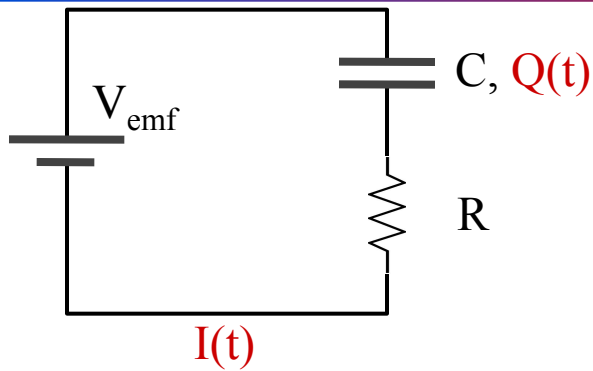
$$\frac{dQ(t)}{dt} = \frac{V_{\text{emf}}}{R} - \frac{1}{RC}Q(t)$$



Verify solution:

$$\begin{aligned} \frac{dQ}{dt} &= -\frac{1}{RC}Ae^{-t/RC} = -\frac{1}{RC}\left(Q(t) - \text{constant}\right) \\ &= \frac{1}{RC}\text{constant} - \frac{Q(t)}{RC} \end{aligned}$$


Use this

# GOAL: Find $Q(t)$ , $I(t)$ in RC circuit

$$Q = CV \quad I = \frac{dQ}{dt} \quad V = IR$$

$$Q(t) = Ae^{-t/RC} + \text{constant}$$
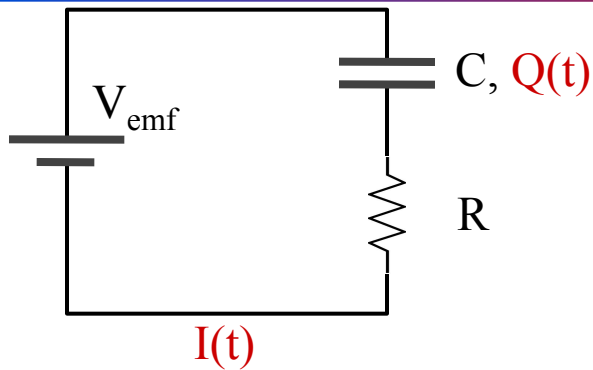
$$\frac{dQ(t)}{dt} = \frac{V_{\text{emf}}}{R} - \frac{1}{RC}Q(t) \quad \text{Compare to this}$$



Verify solution:

$$\begin{aligned} \frac{dQ}{dt} &= -\frac{1}{RC}Ae^{-t/RC} = -\frac{1}{RC}\left(Q(t) - \text{constant}\right) \\ &= \frac{1}{RC}\text{constant} - \frac{Q(t)}{RC} \end{aligned}$$

$$\Rightarrow \boxed{\text{constant} = V_{\text{emf}}C}$$

"Boundary conditions"

(i.e. use physics – think about the extremes)

$$\text{At } t=0: \quad Q(t \rightarrow 0) = Ae^0 + V_{\text{emf}}C = A + V_{\text{emf}}C = 0$$

$$\Rightarrow \boxed{A = -V_{\text{emf}}C}$$


# GOAL: Find $Q(t)$ , $I(t)$ in RC circuit

$$Q = CV \quad I = \frac{dQ}{dt}$$

$$V = IR$$

$$Q(t) = Ae^{-t/RC} + \text{constant}$$
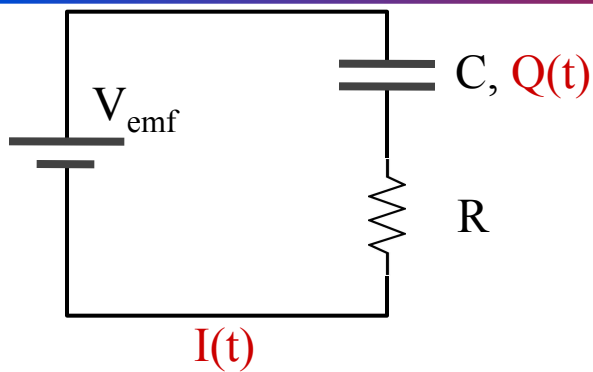
$$\frac{dQ(t)}{dt} = \frac{V_{\text{emf}}}{R} - \frac{1}{RC}Q(t)$$



$$\text{constant} = V_{\text{emf}}C$$


$$A = -V_{\text{emf}}C$$

$$Q(t) = -V_{\text{emf}}Ce^{-t/RC} + V_{\text{emf}}C$$

$$Q(t) = V_{\text{emf}}C \left[ 1 - e^{-t/RC} \right]$$


Doublecheck:  
Is it what we expected?

✓ Yes, it is.

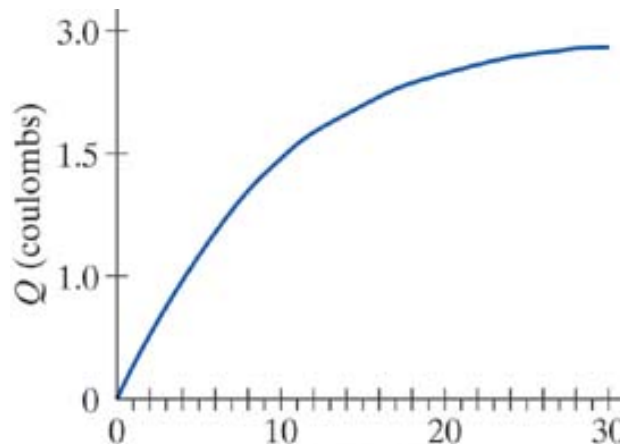
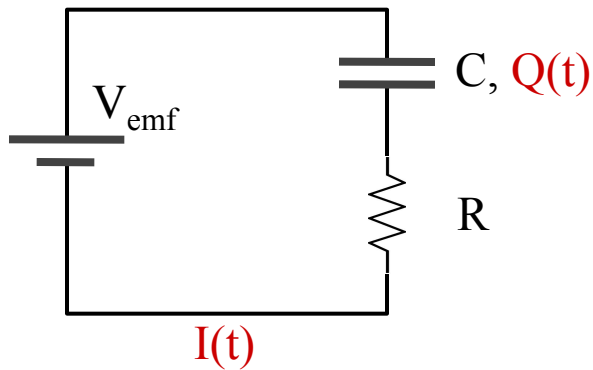
# GOAL: Find $Q(t)$ , $I(t)$ in RC circuit

$$Q = CV \quad I = \frac{dQ}{dt} \quad V = IR \quad Q(t) = V_{\text{emf}} C \left[ 1 - e^{-t/RC} \right]$$




Now find  $I(t)$ :

$$I(t) = \frac{dQ}{dt} = -V_{\text{emf}} C \left[ -\frac{1}{RC} e^{-t/RC} \right]$$

$$I(t) = \frac{V_{\text{emf}}}{R} e^{-t/RC}$$


Doublecheck:  
Is it what we expected?

✓ Yes, it is.

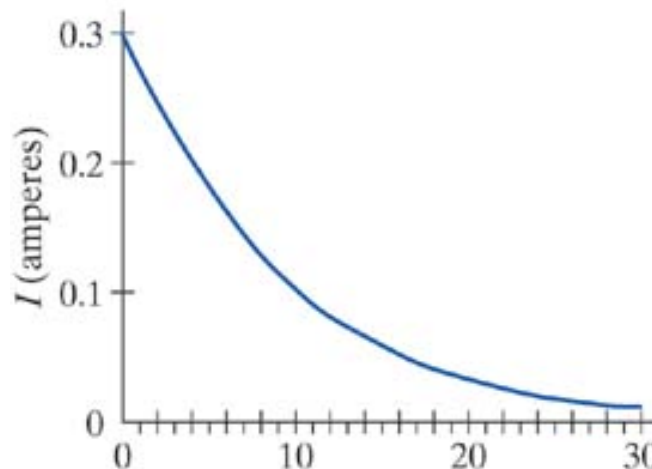



# RC Circuit: Summary


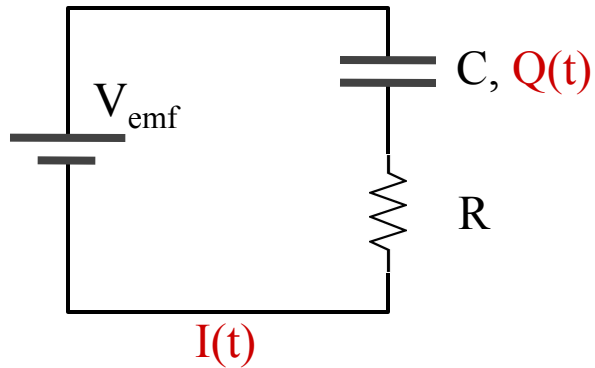


Charge in an RC circuit


$$Q = C(emf)[1 - e^{-t/RC}]$$

Current in an RC circuit

$$I = \frac{emf}{R} e^{-t/RC}$$

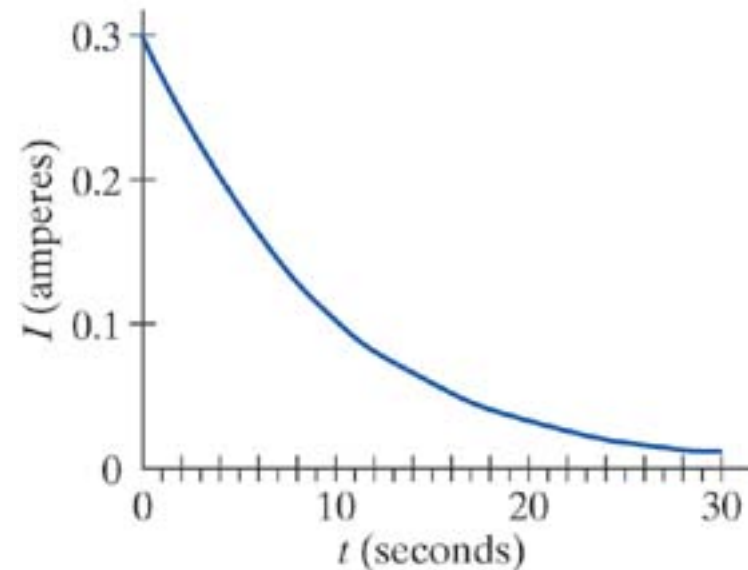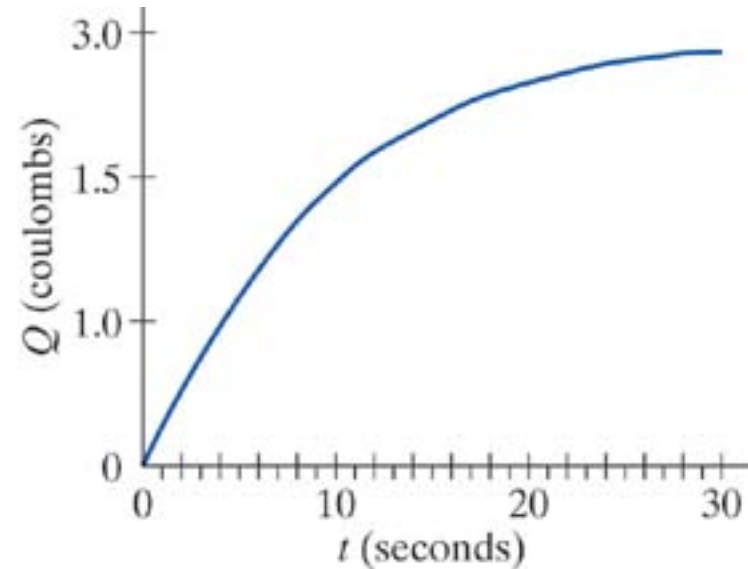

# The RC Time Constant

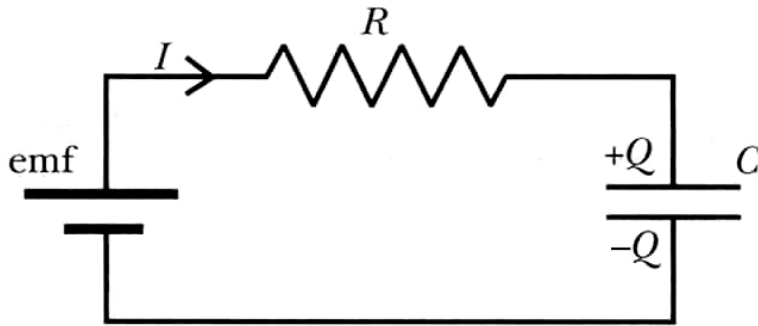

Current in an RC circuit

$$I = \frac{emf}{R} e^{-t/RC}$$


When time  $t = RC$ , the current  $I$  drops by a factor of  $e$ .

$RC$  is the ‘time constant’ of an RC circuit.

$$e^{-t/RC} = e^{-1} = \frac{1}{2.718} = 0.37$$

A rough measurement of how long it takes to reach final equilibrium

# What is the value of RC?

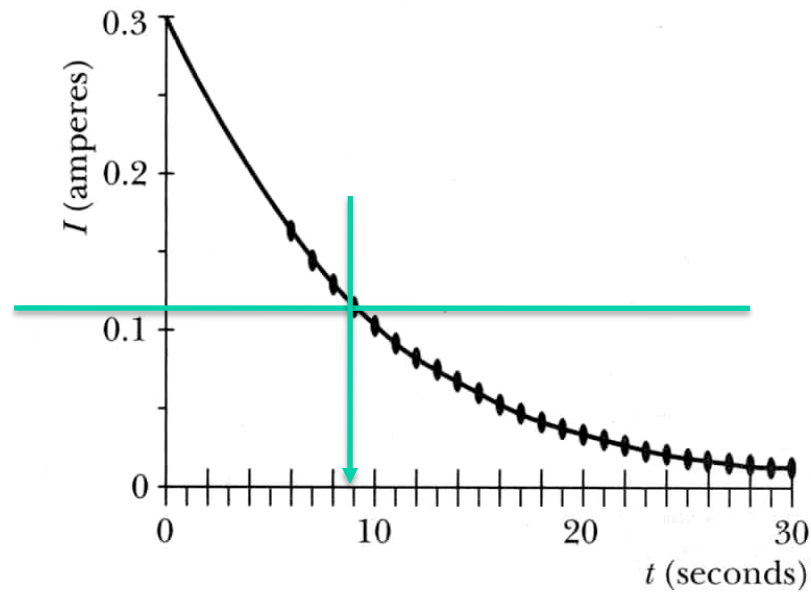

About 9 seconds

# Today

---

- Ammeters, Voltmeters, Ohmmeters, Oh my!
- Solving for  $Q(t)$  and  $I(t)$  in an RC circuit
- The "time constant" of an RC circuit is  $RC$