


## LECTURE 6

- Impedance  $Z(s)$
- Admittance  $Y(s)$

Reference: Decarlo/Lin PP 603-617

Impedance and AdmittanceImpedance (s-domain)

$$Z(s) = \frac{V(s)}{I(s)}$$

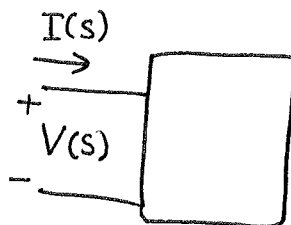

- No independent source, ~~zero~~ no initial condition  
(no internal stored energy)

$$V(s) = Z(s) I(s)$$

unit of impedance :  $\Omega$   
(ohm)

Admittance

$$Y(s) = \frac{I(s)}{V(s)}$$

$$I(s) = Y(s) V(s)$$


unit of admittance :  $S$  ( $\Omega^{-1}$ , mho)  
(siemen)

Relationship between Impedance and Admittance

$$Z(s) = \frac{1}{Y(s)}$$

or

$$Y(s) = \frac{1}{Z(s)}$$

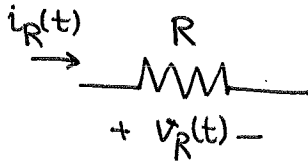Resistor


$$v_R(t) = R i_R(t)$$

$$V_R(s) = R I_R(s)$$

$$V_R(s) = Z_R I_R(s) \Rightarrow \boxed{Z_R = R}$$

$$I_R(s) = \frac{1}{R} V_R(s) = Y_R(s) V_R(s)$$

$$\Rightarrow \boxed{Y_R = \frac{1}{R}}$$

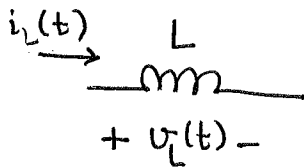Inductor


$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$V_L(s) = L s I_L(s)$$

$$V_L(s) = Z_L I_L(s) \Rightarrow \boxed{Z_L = L s}$$

$$I_L(s) = \frac{1}{L s} V_L(s) = Y_L(s) V_L(s)$$

$$\Rightarrow \boxed{Y_L = \frac{1}{L s}}$$

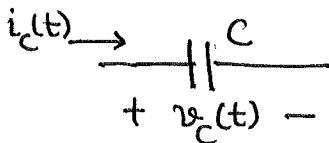Capacitor

$$i_C(t) = C \frac{dv_C(t)}{dt}$$

$$I_C(s) = C s V_C(s) \Rightarrow \boxed{Y_C = C s}$$

$$V_C(s) = \frac{1}{C s} I_C(s) \Rightarrow \boxed{Z_C = \frac{1}{C s}}$$


Manipulation Rules

(a) Impedances - manipulated as resistances




$$\Rightarrow Z_{eq}(s) = Ls + \frac{1}{Cs}$$

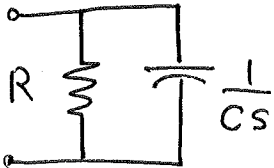(b) Admittances - manipulated as conductances



$$\Rightarrow Y_{eq}(s) = Cs + \frac{1}{R}$$

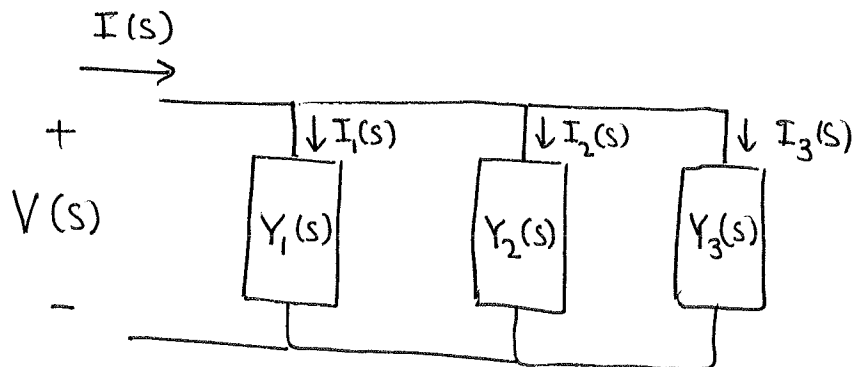Example: Parallel Admittances and Current Division



$$Y(s) = Y_1(s) + Y_2(s) + Y_3(s)$$

$$Z(s) = \frac{1}{Y(s)} = \frac{1}{Y_1(s) + Y_2(s) + Y_3(s)}$$


$$I_1(s) = \frac{Y_1(s)}{Y_1(s) + Y_2(s) + Y_3(s)} I(s)$$

$$I_2(s) = \frac{Y_2(s)}{Y_1(s) + Y_2(s) + Y_3(s)} I(s)$$

$$I_3(s) = \frac{Y_3(s)}{Y_1(s) + Y_2(s) + Y_3(s)} I(s)$$

$$Y(s) = \frac{I(s)}{V(s)} \Rightarrow V(s) = \frac{1}{Y(s)} \cdot I(s)$$

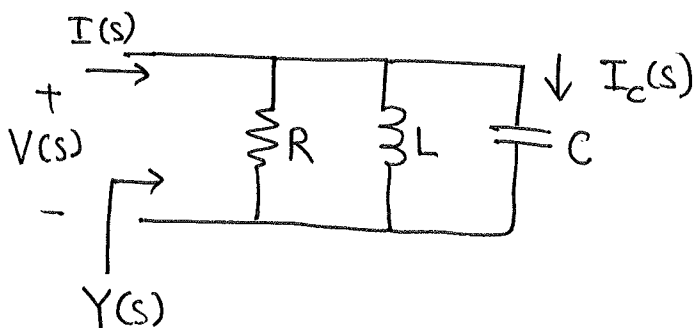Example: Find  $Y(s)$ ,  $Z(s)$  and  $I_c(s)$




$$\begin{aligned} Y(s) &= \frac{1}{R} + \frac{1}{Ls} + \frac{1}{1/Cs} = \frac{1}{R} + \frac{1}{Ls} + Cs \\ &= \frac{\frac{Ls}{R} + 1 + LCs^2}{Ls} \end{aligned}$$

$$Z(s) = \frac{1}{Y(s)} = \frac{Ls}{\frac{Ls}{R} + 1 + LCs^2} = \frac{\frac{1}{C}s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$


$$I_c(s) = \frac{Y_c(s)}{Y(s)} \cdot I(s) = Z(s) Y_c(s) I(s)$$

$$= \frac{\frac{1}{C}s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}} \cdot Cs \cdot I(s)$$

$$I_c(s) = \frac{s^2}{s^2 + \frac{1}{RC}s + \frac{1}{LC}} \cdot I(s)$$

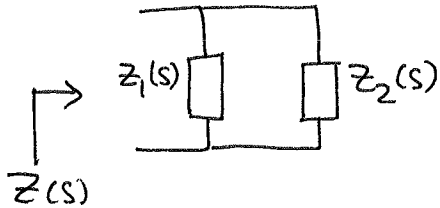
Product/Sum Rule

$$Z(s) = \frac{z_1(s) z_2(s)}{z_1(s) + z_2(s)}$$

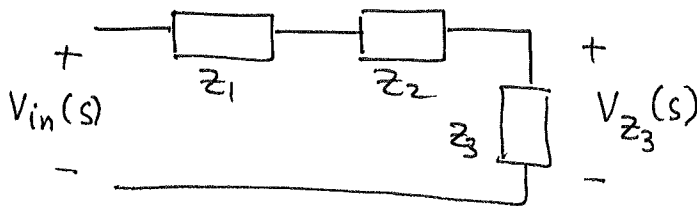Voltage Division

$$V_{z_3}(s) = \frac{z_3(s)}{z_1(s) + z_2(s) + z_3(s)} \cdot V_{in}(s)$$

Example:

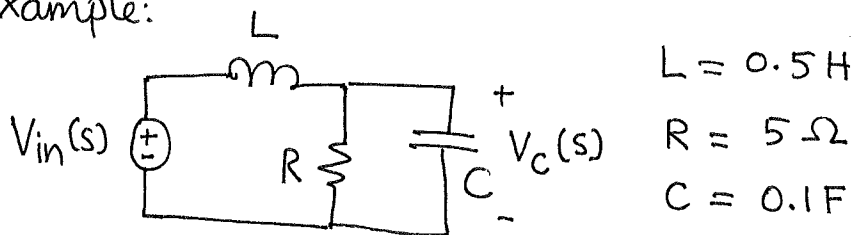

$$L = 0.5 \text{ H}$$

$$R = 5 \Omega$$

$$C = 0.1 \text{ F}$$

Find  $V_C(s)$  if  $v_{in}(t) = \delta(t)$ 

Solution:

$$V_{in}(s) = \mathcal{L}[v_{in}(t)] = \mathcal{L}[\delta(t)] = 1$$

$$V_C(s) = \frac{Z(s)}{Z(s) + Ls} \cdot V_{in}(s)$$

where  $Z(s) \Rightarrow$




$$Y(s) = \frac{1}{R} + Cs$$

$$Y(s) = 0.2 + 0.1s$$

$$\therefore Z(s) = \frac{1}{Y(s)} = \frac{1}{0.1s + 0.2}$$

$$\therefore V_C(s) = \frac{\frac{10}{s+2}}{\frac{10}{s+2} + 0.5s} \quad (1)$$


$$= \frac{10}{10 + 0.5s(s+2)} = \frac{10}{10 + 0.5s^2 + s} = \frac{20}{s^2 + 2s + 20} \leftarrow = \frac{10}{s+2}$$

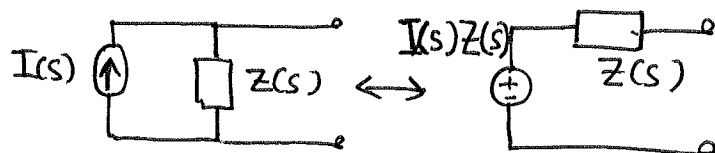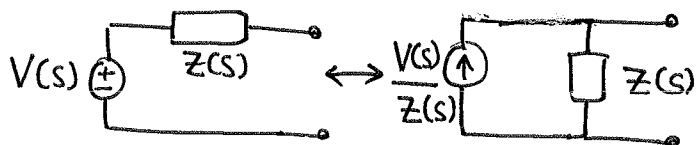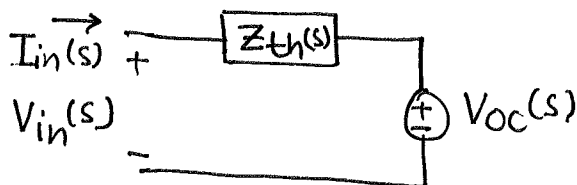Source TransformationThevenin and Norton EquivalentsThevenin (s-domain)

$$V_{in}(s) = Z_{th}(s) I_{in}(s) + V_{oc}(s)$$

Strategy: Find an equation of the circuit in one of the two forms. Use pattern recognition to identify  $Z_{th}(s)$  and  $V_{oc}(s)$  (or)  $I_{sc}(s)$ .

Example: Find Thevenin Equivalent

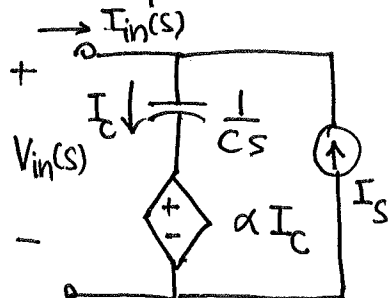

$$(c) \quad I_{in}(s) = \frac{Cs}{1 + \alpha Cs} V_{in}(s) - I_s(s)$$

$\uparrow 1/Z_{th}$ 
 $\uparrow I_{sc}(s)$

$$(a) \quad I_{in}(s) = I_c(s) - I_s$$


$$(b) \quad I_c(s) = Cs [V_{in}(s) - \alpha I_c(s)]$$

$$= Cs V_{in}(s) - \alpha Cs I_c(s)$$

$$(1 + \alpha Cs) I_c(s) = Cs V_{in}(s)$$

$$I_c(s) = \frac{Cs}{1 + \alpha Cs} V_{in}(s)$$

$$\text{Note: } V_{oc}(s) = I_{sc}(s) \cdot Z_{th}(s)$$

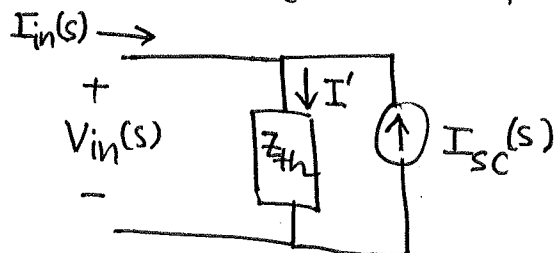Norton (s-domain)

$$I_{in}(s) = I' - I_{sc}(s)$$

$$I_{in}(s) = \frac{V_{in}(s)}{Z_{th}} - I_{sc}(s)$$