# CS250 Computer Architecture

Fall 2012

Part 7: Pipelining

# Acknowledgment

- Prof. Craig Zilles
- Mr. Howard Huang
   Both with the Department of Computer Science at UIUC

#### A relevant question

- Assuming you've got:
  - One washer (takes 30 minutes)



One drier (takes 40 minutes)




One "folder" (takes 20 minutes)



- It takes 90 minutes to wash, dry, and fold 1 load of laundry.
  - How long does 4 loads take?


#### The slow way

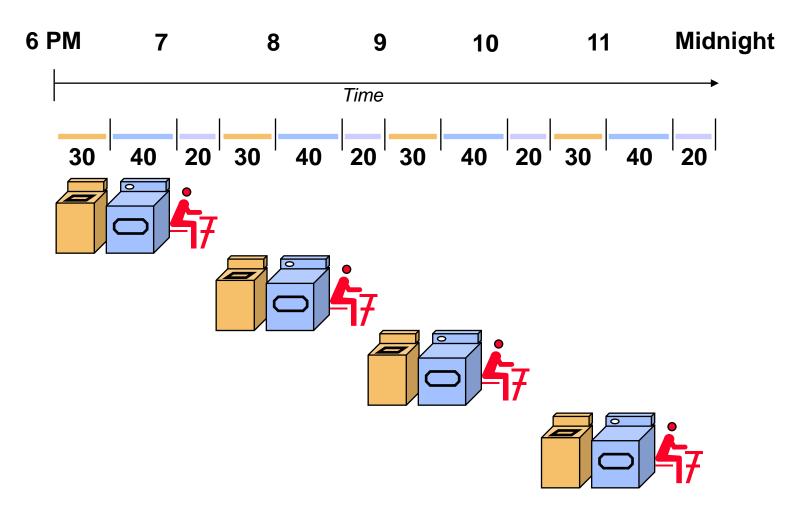

If each load is done sequentially it takes 6 hours

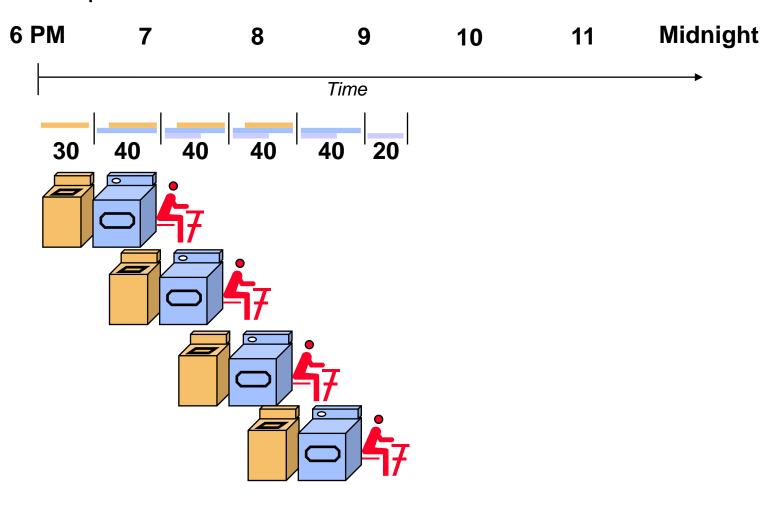
## **Laundry Pipelining**

- Start each load as soon as possible
  - Overlap loads



Pipelined laundry takes 3.5 hours

#### **Pipelining Lessons**

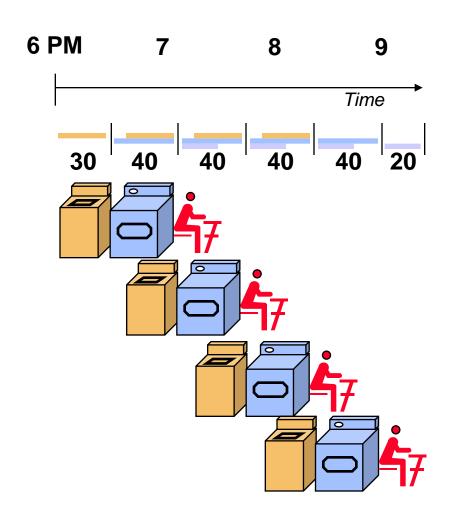

- Pipelining doesn't help latency of single load, it helps throughput of entire workload
- Pipeline rate limited by slowest pipeline stage
- Multiple tasks operating simultaneously using different resources
- Potential speedup = Number pipe stages
- Unbalanced lengths of pipe stages reduces speedup
- Time to "fill" pipeline and time to "drain" it reduces speedup

6

## Pipelining is not just Multiprocessing

- Pipelining does involve parallel processing, but in a specific way.
- Both multiprocessing and pipelining relate to the processing of multiple "things" using multiple "functional units"
  - Multiprocessing implies each thing is processed entirely by a single functional unit
    - e.g., multiple lanes at the supermarket
  - In pipelining, each thing is broken into a sequence of pieces, where each piece is handled by a different (specialized) functional unit.
    - Supermarket analogy?
- Pipelining and multiprocessing are not mutually exclusive
  - Modern processors do both, with multiple pipelines (e.g., superscalar)

- Pipelining is a general-purpose efficiency technique
  - It is not specific to processors
- Pipelining is used in:
  - Assembly lines
  - Bucket brigades
  - Fast food restaurants
- Pipelining is used in other CS disciplines:
  - Networking
  - Server software architecture
- Useful to increase throughput in the presence of long latency
  - More on that later...

#### Instruction execution review


Executing a MIPS instruction can take up to five steps.

Step	Name	Description
Instruction Fetch	IF	Read an instruction from memory.
Instruction Decode	ID	Read source registers and generate control signals.
Execute	EX	Compute an R-type result or a branch outcome.
Memory	MEM	Read or write the data memory.
Writeback	WB	Store a result in the destination register.

However, as we saw, not all instructions need all five steps.

Instruction	Steps required								
beq	IF	ID	EX						
R-type	IF	ID	EX		WB				
SW	IF	ID	EX	MEM					
lw	IF	ID	EX	MEM	WB				

## Single-cycle datapath diagram

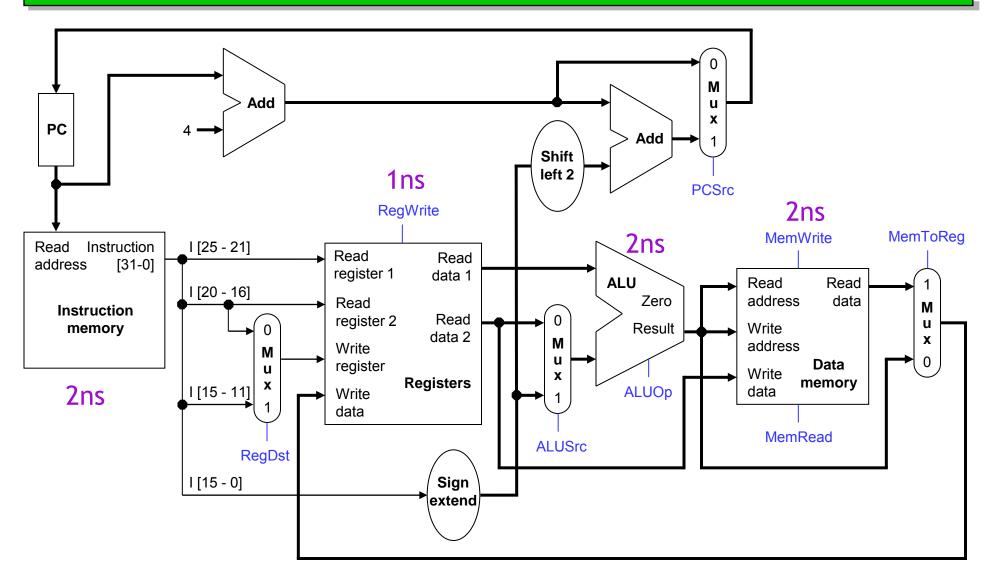


How long does it take to execute each instruction?

#### Single-cycle review

- All five execution steps occur in one clock cycle.
- This means the cycle time must be long enough to accommodate all the steps of the most complex instruction—a "lw" in our instruction set.
  - If the register file has a 1ns latency and the memories and ALU have a 2ns latency, "lw" will require 8ns.
  - Thus all instructions will take 8ns to execute.
- Each hardware element can only be used once per clock cycle.
  - A "lw" or "sw" must access memory twice (in the IF and MEM stages),
     so there are separate instruction and data memories.
  - There are multiple adders, since each instruction increments the PC
     (IF) and performs another computation (EX). On top of that, branches also need to compute a target address.

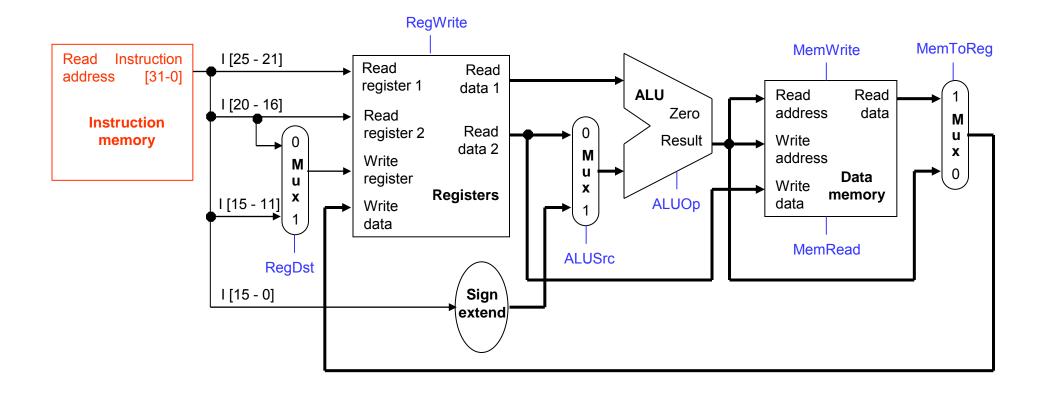
## Example: Instruction Fetch (IF)

- Let's quickly review how lw is executed in the single-cycle datapath.
- We'll ignore PC incrementing and branching for now.
- In the Instruction Fetch (IF) step, we read the instruction memory.



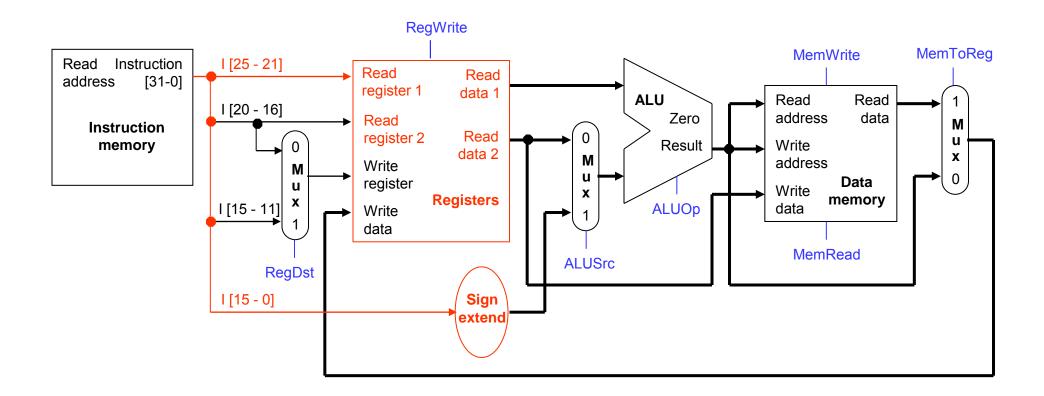
#### Instruction Decode (ID)

 The Instruction Decode (ID) step reads the source register from the register file.



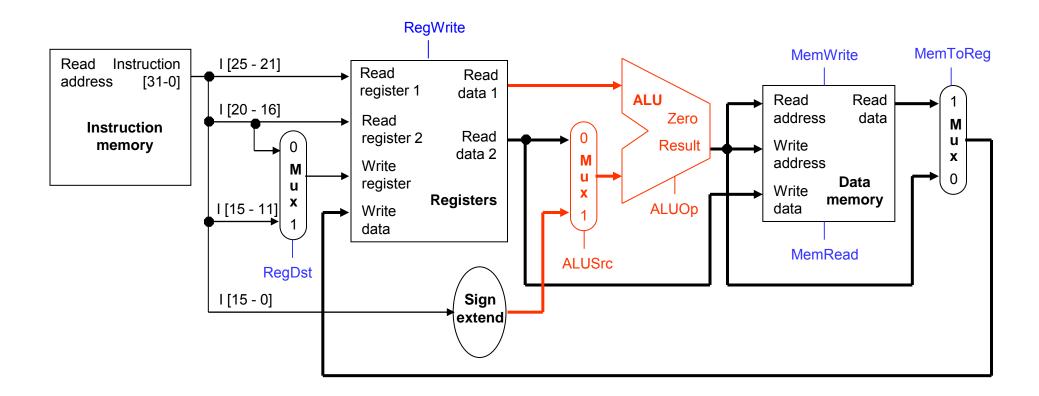
#### Execute (EX)

 The third step, Execute (EX), computes the effective memory address from the source register and the instruction's constant field.



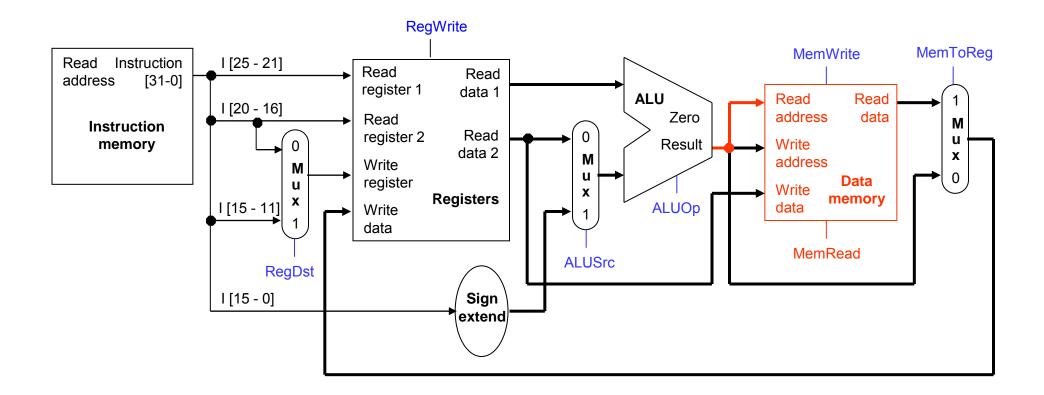
#### Memory (MEM)

 The Memory (MEM) step involves reading the data memory, from the address computed by the ALU.


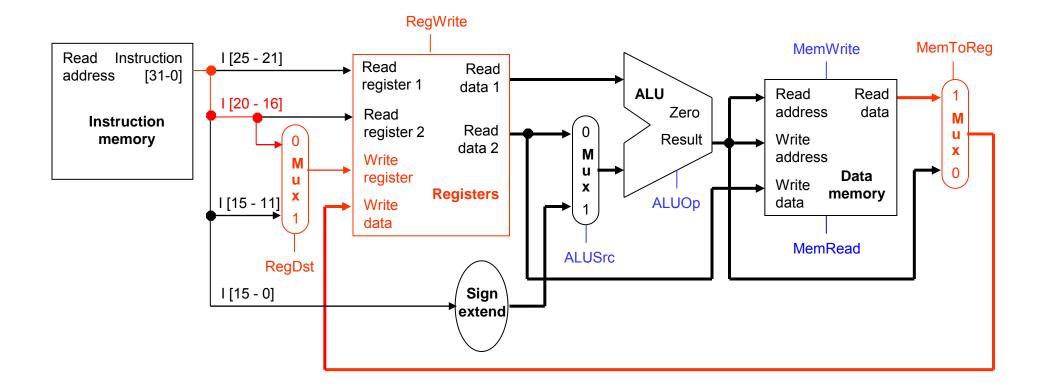
#### Writeback (WB)

• Finally, in the Writeback (WB) step, the memory value is stored into the destination register.




#### A bunch of lazy functional units

- Notice that each execution step uses a different functional unit.
- In other words, the main units are idle for most of the 8ns cycle!
  - The instruction RAM is used for just 2ns at the start of the cycle.
  - Registers are read once in ID (1ns), and written once in WB (1ns).
  - The ALU is used for 2ns near the middle of the cycle.
  - Reading the data memory only takes 2ns as well.
- That's a lot of hardware sitting around doing nothing.

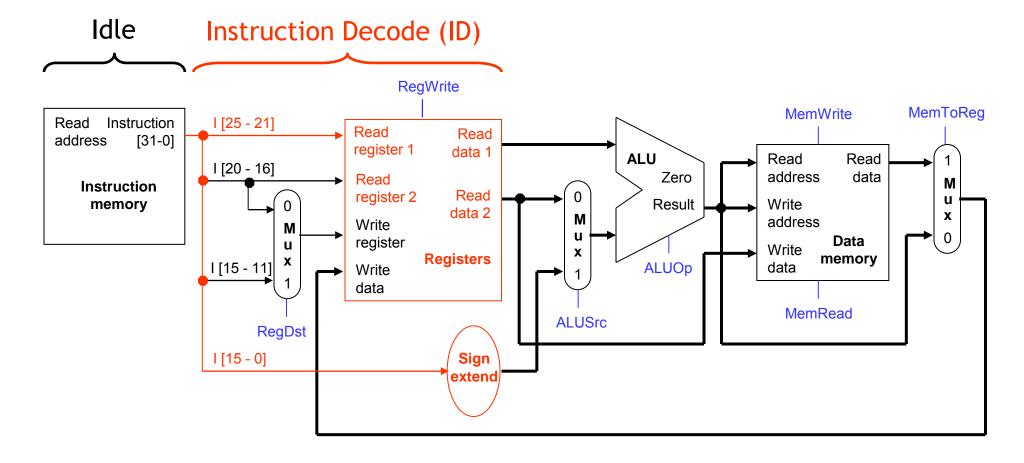
#### Putting those slackers to work

- We shouldn't have to wait for the entire instruction to complete before we can re-use the functional units.
- For example, the instruction memory is free in the Instruction Decode step as shown below, so...



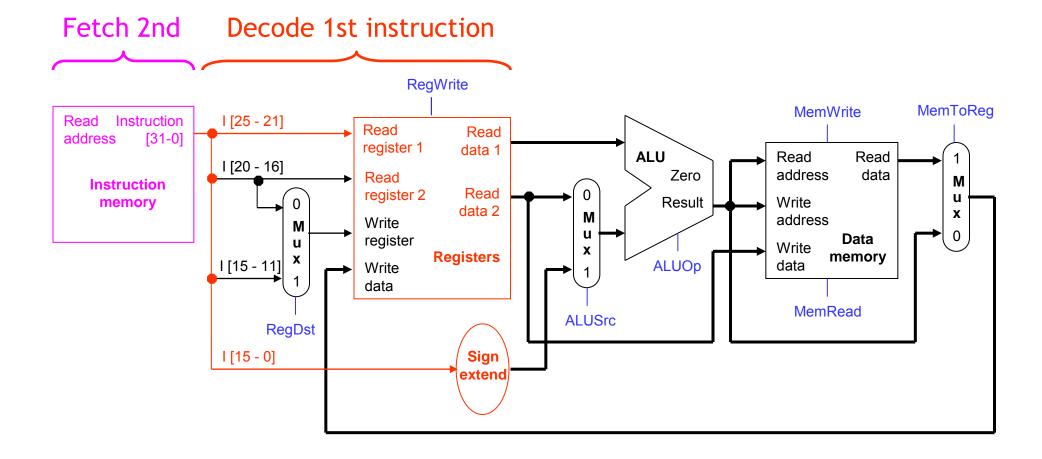
#### Decoding and fetching together

Why don't we go ahead and fetch the next instruction while we're decoding the first one?



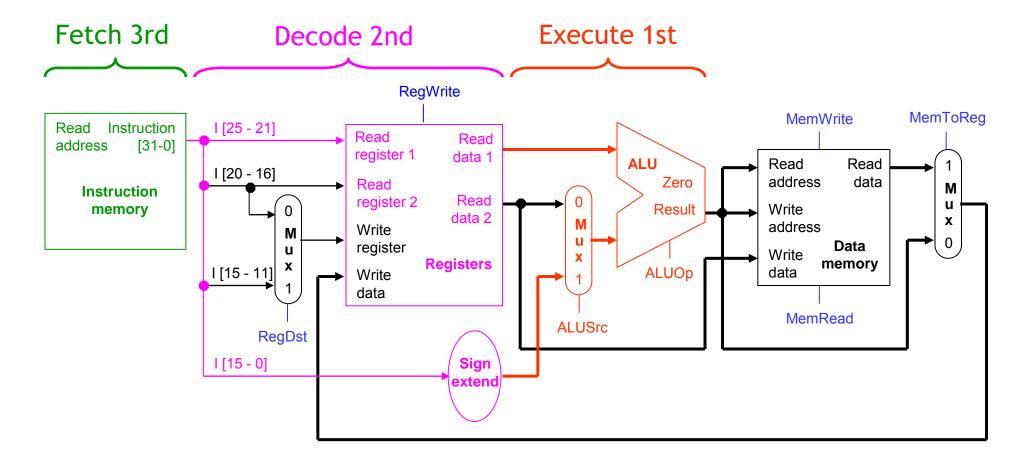
#### Executing, decoding and fetching

- Similarly, once the first instruction enters its Execute stage, we can go ahead and decode the second instruction.
- But now the instruction memory is free again, so we can fetch the third instruction!



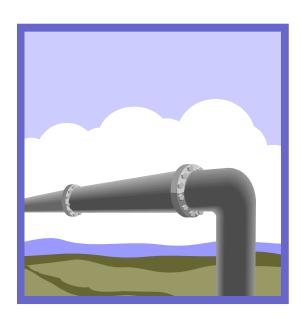
## Making Pipelining Work

- We'll make our pipeline 5 stages long, to handle each of the five steps in a load instructions (the longest instruction for this machine)
  - Stages are: IF, ID, EX, MEM, and WB
- We want to support executing 5 instructions simultaneously: one in each stage.



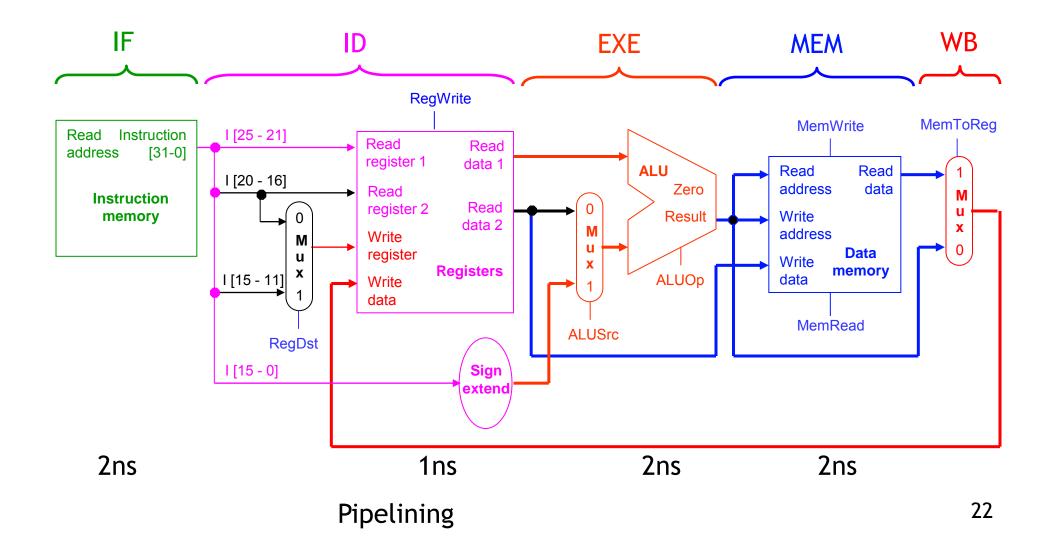
#### Break datapath into 5 stages

- Insert pipeline registers
- Each stage has its own functional units.
- Each stage can execute in 2ns



# **Pipelining Loads**

		Clock cycle								
		1	2	3	4	5	6	7	8	9
lw	\$t0, 4(\$sp)	IF	ID	EX	MEM	WB				
lw	\$t1, 8(\$sp)		IF	ID	EX	MEM	WB			
lw	\$t2, 12(\$sp)			IF	ID	EX	MEM	WB		
lw	\$t3, 16(\$sp)				IF	ID	EX	MEM	WB	
lw	\$t4, 20(\$sp)					IF	ID	EX	MEM	WB

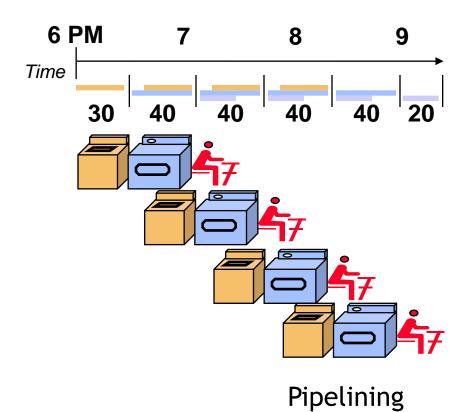


#### A pipeline diagram

		Clock cycle								
		1	2	3	4	5	6	7	8	9
lw	\$t0, 4(\$sp)	IF	ID	EX	MEM	WB				
sub	\$v0, \$a0, \$a1		IF	ID	EX	MEM	WB			
and	\$t1, \$t2, \$t3			IF	ID	EX	MEM	WB		
or	\$s0, \$s1, \$s2				IF	ID	EX	MEM	WB	
add	\$sp, \$sp, -4					IF	ID	EX	MEM	WB


- A pipeline diagram shows the execution of a series of instructions.
  - The instruction sequence is shown vertically, from top to bottom.
  - Clock cycles are shown horizontally, from left to right.
  - Each instruction is divided into its component stages. (We show five stages for every instruction, which will make the control unit easier.)
- This clearly indicates the overlapping of instructions. For example, there
  are three instructions active in the third cycle above.
  - The "lw" instruction is in its Execute stage.
  - Simultaneously, the "sub" is in its Instruction Decode stage.
  - Also, the "and" instruction is just being fetched.

## Pipeline terminology

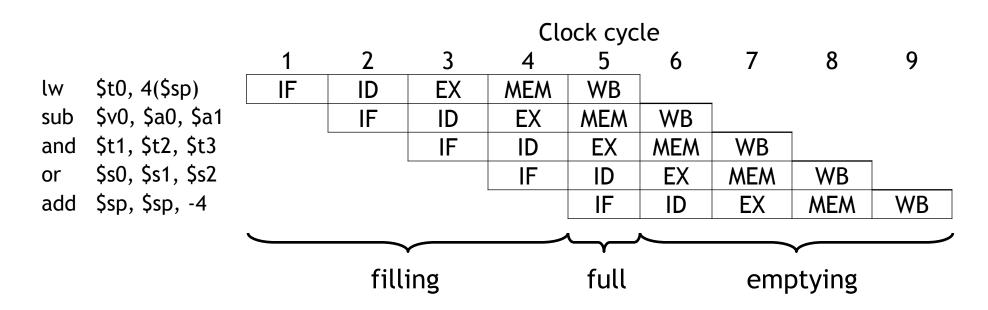

- The pipeline depth is the number of stages—in this case, five.
- In the first four cycles here, the pipeline is filling, since there are unused functional units.
- In cycle 5, the pipeline is full. Five instructions are being executed simultaneously, so all hardware units are in use.
- In cycles 6-9, the pipeline is emptying.

#### **Pipelining Performance**

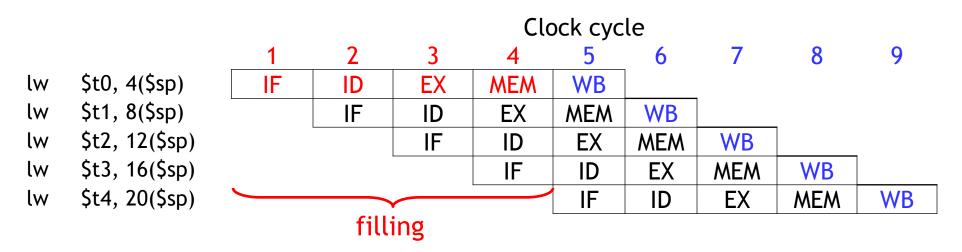

- Execution time on ideal pipeline:
  - time to fill the pipeline + one cycle per instruction
  - How long for N instructions?
- Compare with other implementations:
  - Single Cycle: (8ns clock period)
- How much faster is pipelining for N=1000?

#### Pipeline Datapath: Resource Requirements

		Clock cycle								
		1	2	3	4	5	6	7	8	9
lw	\$t0, 4(\$sp)	IF	ID	EX	MEM	WB				
lw	\$t1, 8(\$sp)		IF	ID	EX	MEM	WB			
lw	\$t2, 12(\$sp)			IF	ID	EX	MEM	WB		
lw	\$t3, 16(\$sp)				IF	ID	EX	MEM	WB	
lw	\$t4, 20(\$sp)					IF	ID	EX	MEM	WB

- We need to perform several operations in the same cycle.
  - Increment the PC and add registers at the same time.
  - Fetch one instruction while another one reads or writes data.
- What does that mean for our hardware?

# Pipelining other instruction types

- R-type instructions only require 4 stages: IF, ID, EX, and WB
  - We don't need the MEM stage
- What happens if we try to pipeline loads with R-type instructions?

		Clock cycle									
		1	2	3	4	5	6	7	8	9	
add	\$sp, \$sp, -4	IF	ID	EX	WB		_				
sub	\$v0, \$a0, \$a1		IF	ID	EX	WB					
lw	\$t0, 4(\$sp)			IF	ID	EX	MEM	WB			
or	\$s0, \$s1, \$s2				IF	ID	EX	WB			
lw	\$t1, 8(\$sp)					IF	ID	EX	MEM	WB	

#### **Important Observation**


- Each functional unit can only be used once per instruction
- Each functional unit must be used at the same stage for all instructions:
  - Load uses Register File's Write Port during its 5th stage
  - R-type uses Register File's Write Port during its 4th stage

		Clock cycle									
		1	2	3	4	5	6	7	8	9	
add	\$sp, \$sp, -4	IF	ID	EX	WB						
sub	\$v0, \$a0, \$a1		IF	ID	EX	WB					
lw	\$t0, 4(\$sp)			IF	ID	EX	MEM	WB			
or	\$s0, \$s1, \$s2				IF	ID	EX	WB			
lw	\$t1, 8(\$sp)					IF	ID	EX	MEM	WB	

This diagram doesn't work!
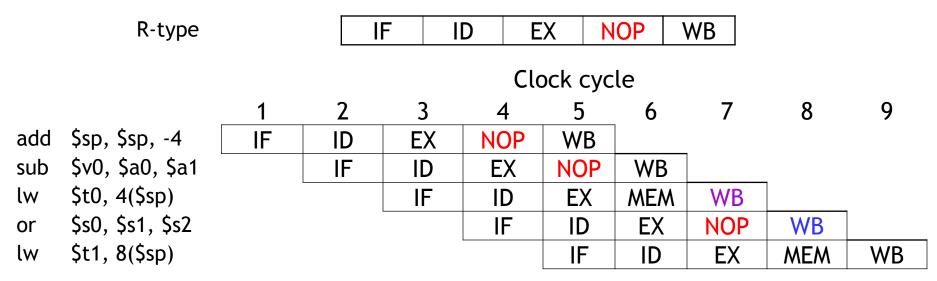
## A solution: Insert NOP stages

- Enforce uniformity
  - Make all instructions take 5 cycles.
  - Make them have the same stages, in the same order
    - Some stages will do nothing for some instructions



Stores and Branches have NOP stages, too...

store branch

IF	ID	EX	MEM	NOP	
IF	ID	EX	NOP	NOP	

#### Summary

- Pipelining attempts to maximize instruction throughput by overlapping the execution of multiple instructions.
- Pipelining offers amazing speedup.
  - In the best case, one instruction finishes on every cycle, and the speedup is equal to the pipeline depth.
- The pipeline datapath is much like the single-cycle one, but with added pipeline registers
  - Each stage needs is own functional units
- Next time we'll see the datapath and control, and walk through an example execution.